

BITS PILANI , DUBAI CAMPUS
2nd Year, SECOND SEMESTER 2013 – 2014

Comprehensive exam (Closed Book)


Course Code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **3 hours**

Date: **27.05.14 FN**
Maximum Marks: **80 marks**
Weightage: **40%**


Instruction: This paper consists of TWELVE questions. Answer all the questions. Part A , B and C must be answered in separate booklets.

PART A

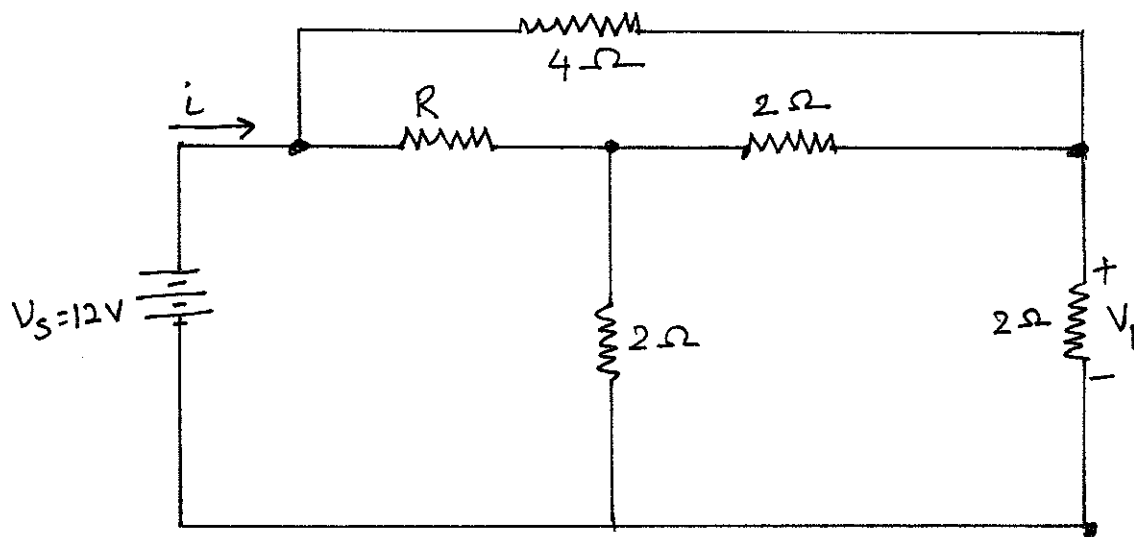Q1. Consider the nonseries – parallel circuit shown below. When $R = \frac{1}{2} \Omega$, then $v_1 = 6$ volts. Determine the resistance $R_{eq} = V_S / i$ loading the battery. **[7M]**



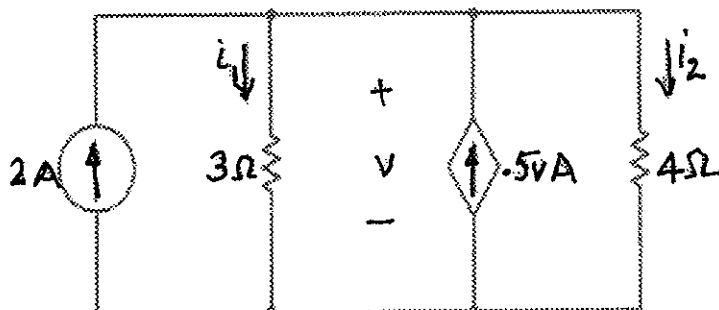
Q2. Consider the following circuit and determine the values of v , i_1 and i_2 . **[5M]**



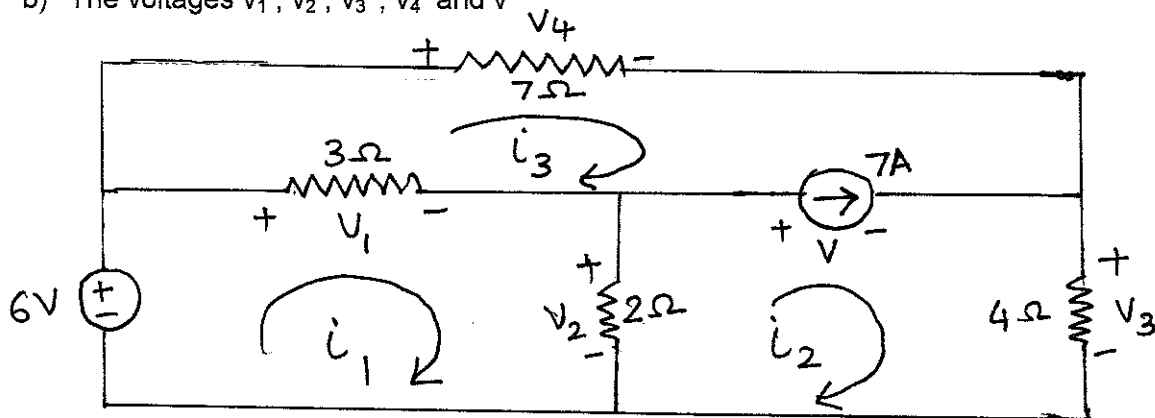Q3. For the circuit shown below, calculate the following using Mesh Analysis.


[8M]

- Mesh currents i_1 , i_2 and i_3
- The voltages v_1 , v_2 , v_3 , v_4 and v



Q4. Determine the natural responses $v(t)$ and $i(t)$ for $t > 0$ for the series RLC circuit shown below. $R = 5\Omega$, $L = \frac{1}{2} \text{ H}$ and $C = \frac{1}{8} \text{ F}$ given that the initial conditions are $v(0) = 2\text{V}$ and $i(0) = 1\text{A}$.


[10M]

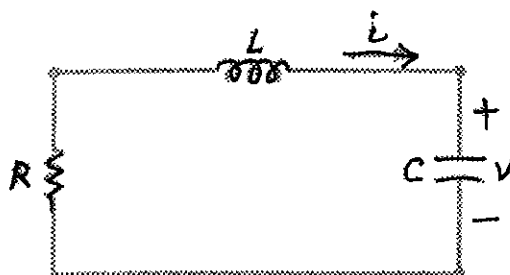

PART B

Q5. What value of ω will cause the forced response v_o in the figure to be zero?

[5M]

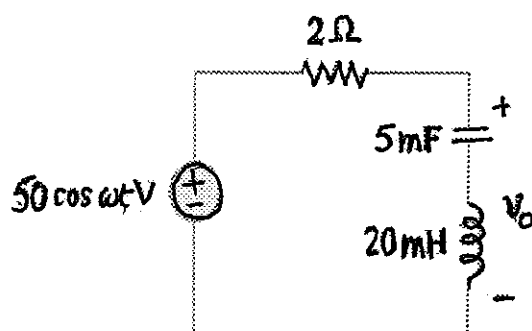


Q6. A coil has an mmf of 600 At, and a reluctance of 3×10^6 At/Wb. Find the total flux Φ .

[4M]

Q7. A balanced three-phase Y-source with $V_{Ph} = 210$ V rms drives a Y-connected three-phase load with phase impedance $Z_A = 80 \Omega$, $Z_B = 60 + j90 \Omega$, and $Z_C = j80 \Omega$. Calculate the line currents and total complex power delivered to the load. Assume that the neutrals are connected as shown.

[8 M]

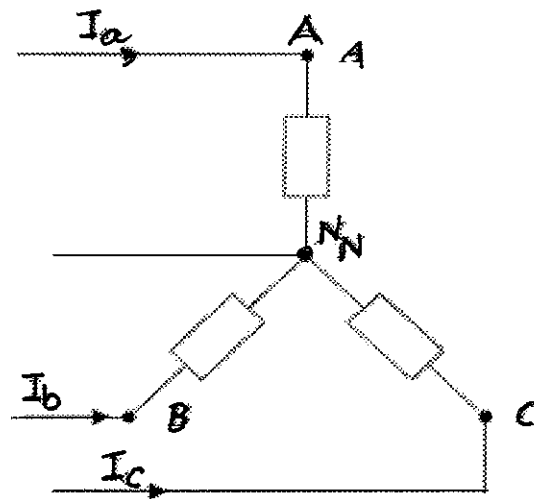


Q8. A germanium diode ($\eta=1$) has saturation current of $10\mu\text{A}$ at 300 K

a) Find the current for the case that the forward bias voltage is 0.3V

b) Find the forward bias voltage that results in a current of 0.5A


c) In the circuit given, if v_1 is 12V, what value of R results in a current of 0.5A?

[8 M]

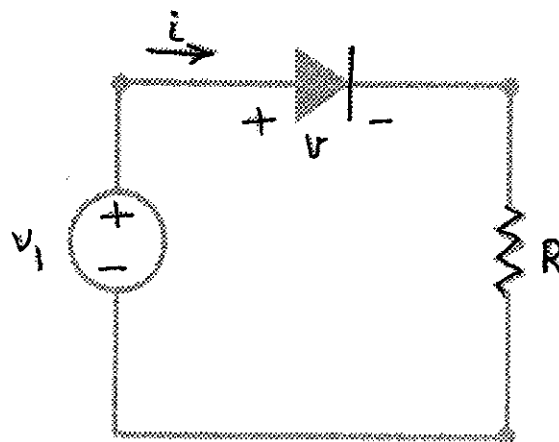


PART C

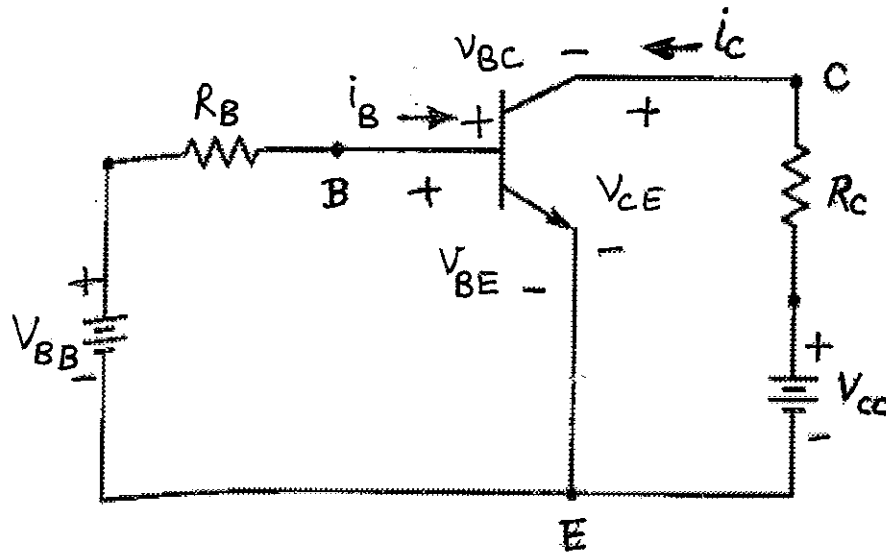
Q9. Consider a silicon npn transistor with $\beta = 100$ in common emitter configuration as shown below, where $R_B = 330 \text{ k}\Omega$, $R_C = 2.7 \text{ k}\Omega$, $V_{BB} = V_{CC} = 10 \text{ V}$. Take $V_{BE} = 0.7 \text{ V}$ and $V_{CE} = 0.5 \text{ V}$. Verify that the transistor is operating in the active region. [10M]



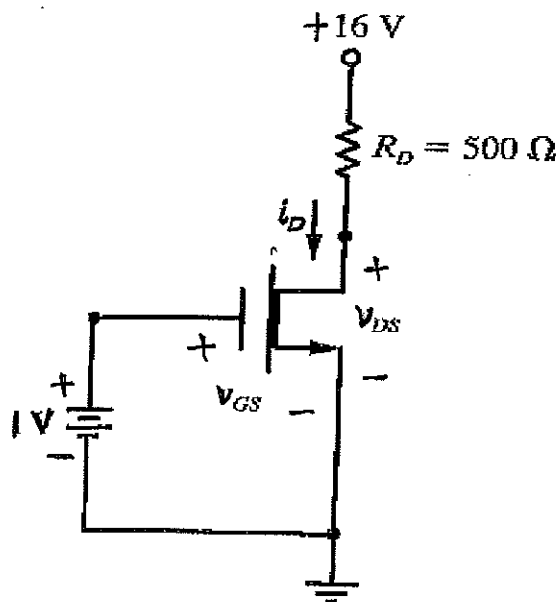Q10. Consider the MOSFET circuit shown below where the depletion NMOS transistor has $I_{DSS} = 8 \text{ mA}$ and $V_P = -2 \text{ V}$. Obtain the values for V_{GS} , I_D and V_{DS} . [6M]




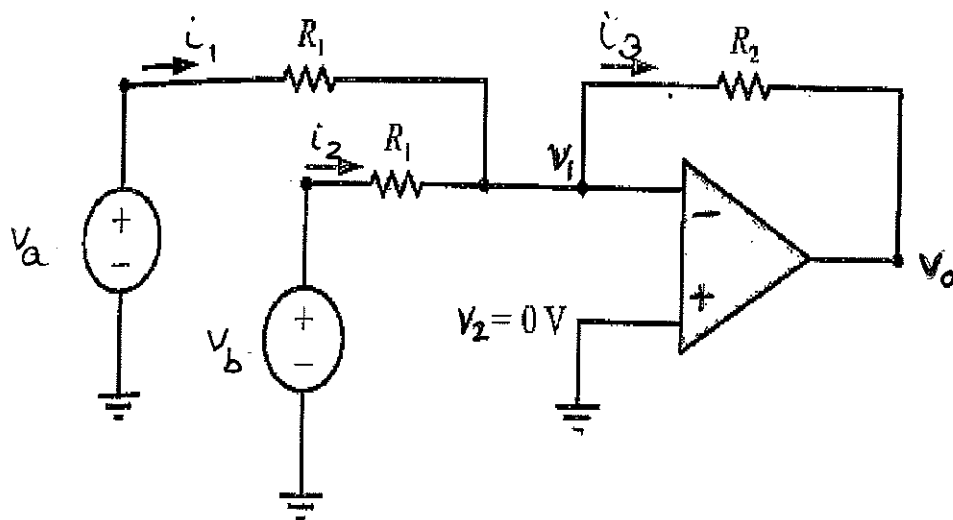- Q11. Calculate the values of V_o , i_1 , i_2 and i_3 for the following op amp when $R_1 = 2\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $v_a = -0.5 \cos(1000\pi t)$ and $v_b = 0.3 \cos(2000\pi t)$. [5M]



- Q12. Consider the logic circuit where the output is characterized by the following binary function. Draw the corresponding truth table. [4M]

$$F = \overline{A + B + AB}$$

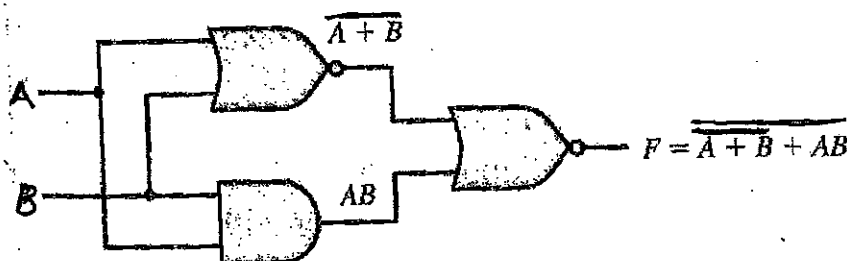

END OF PAPER

BITS PILANI, DUBAI CAMPUS
1st Year, SECOND SEMESTER 2013 – 2014


TEST – 2 (Open Book)

Course Code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **50 minutes**


Date: **27.4.2014**
Maximum Marks: **40**
Weightage: **20%**

Instruction: Answer all the questions.

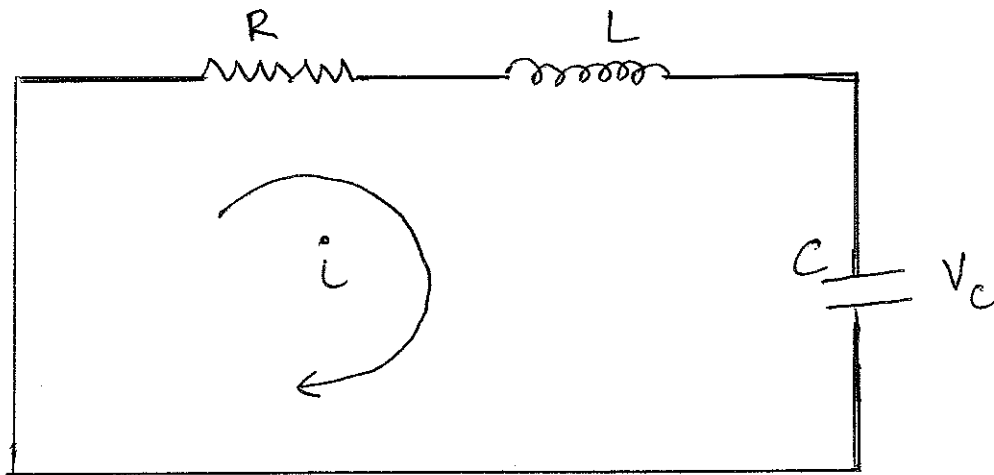Q1. Consider the following RLC series circuit in which $R = 10\Omega$, $L = 5H$, $C = 2mF$, $i(0) = 3mA$ and $v_C(0) = 4V$. Find $i(t)$ at $t > 0$. [13M]



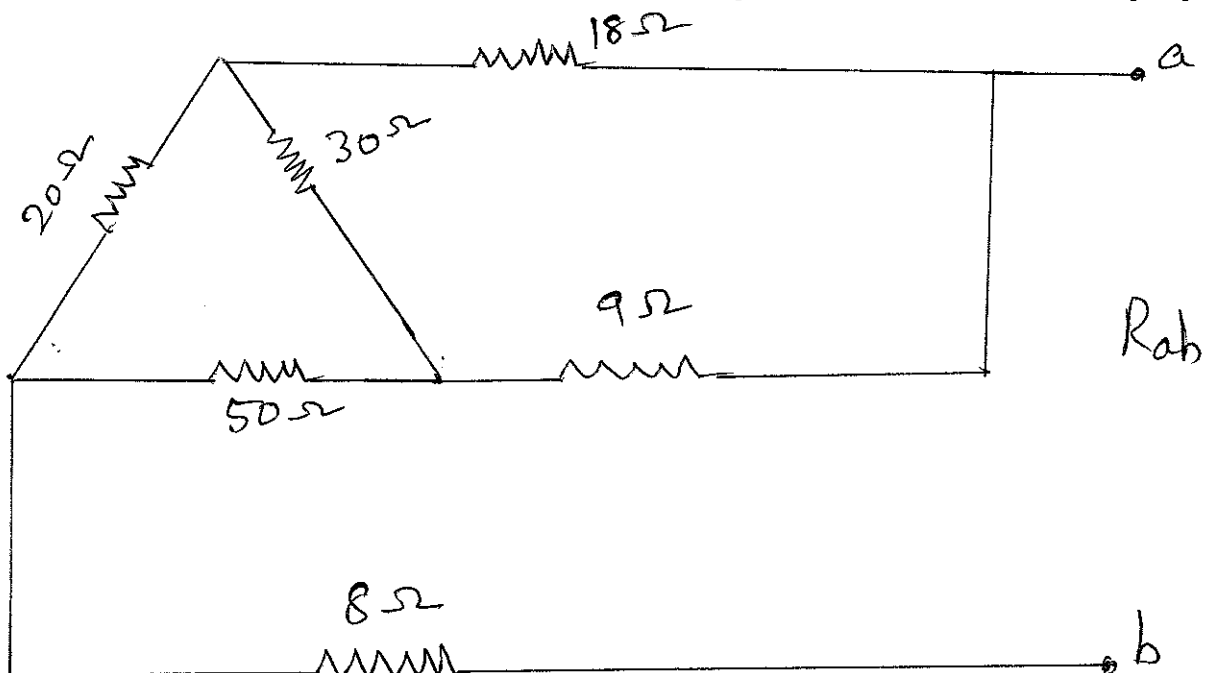
Q2. Find the equivalent resistance R_{ab} for the circuit given below. [8M]




Q3. Determine the equivalent impedance of the network shown in the circuit below if the frequency is 60Hz. Compute the current $i(t)$ if the voltage source is

$$v(t) = 50 \cos(\omega t + 30^\circ) \text{ volts}$$


[6M]

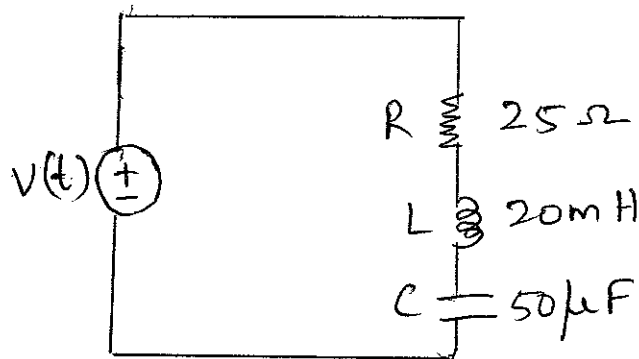

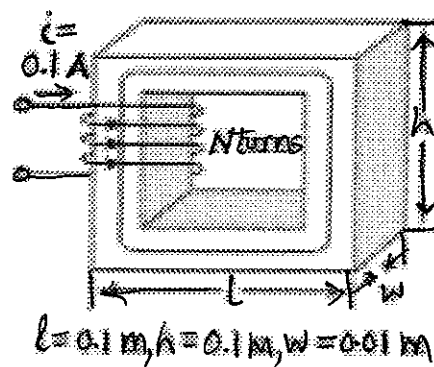Q4. Calculate mmf, reluctance, flux, flux density and the field intensity on the magnetic structure shown below. Assume $N = 500$ turns and relative permeability of 1000. [5M]



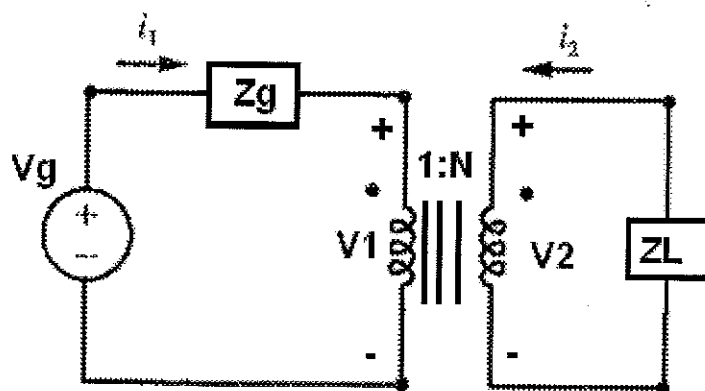Q 5. For the ideal transformer circuit shown below, find (a) $i_1(t)$, (b) $i_2(t)$, (c) $v_1(t)$ and (d) $v_2(t)$. Assume $N = 2$, Z_g is a 2 H inductor, Z_L is a $\frac{1}{2}$ F capacitor and $V_g(t) = 15 \cos 2t$. [8M]



BITS PILANI, DUBAI CAMPUS
1st Year, SECOND SEMESTER 2013 – 2014


TEST – 1 (Closed Book)

Course Code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **50 minutes**


Date: **09 .03.2014**
Maximum Marks: **50**
Weightage: **25%**

Instruction: Answer all the questions.

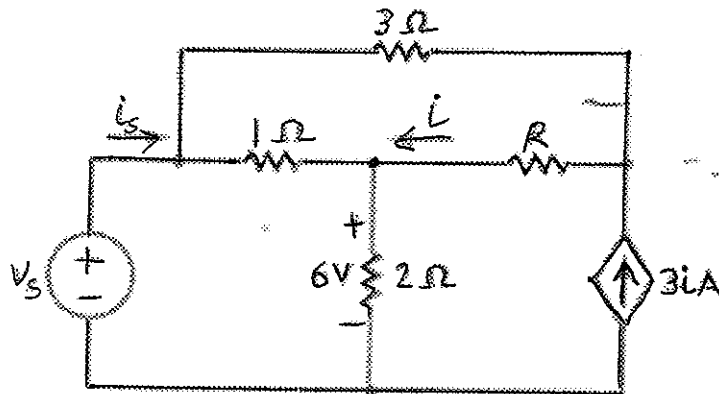
Q1. For the circuit shown below, suppose $R = 10\Omega$. Determine the source voltage v_s , and the equivalent resistance R_{eq} . [12 M]



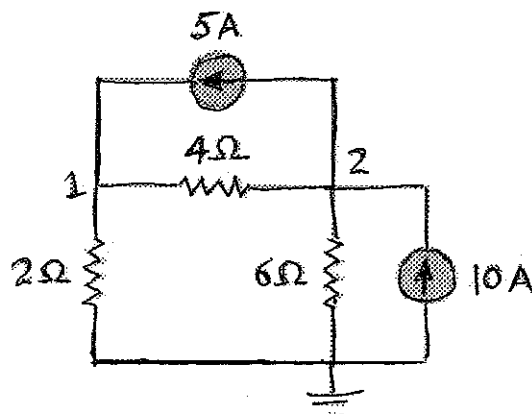Q2. Calculate the node voltages and the current through the 4Ω and the 2Ω resistors in the following circuit. [12 M]




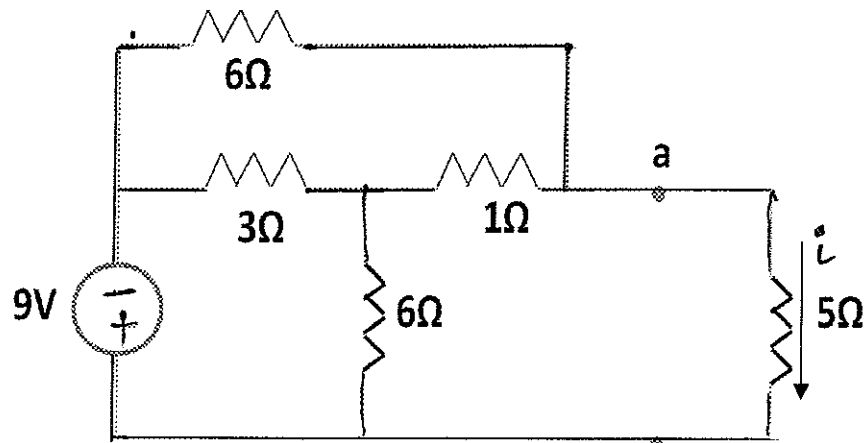
- Q3. Find and draw the Norton equivalent of the circuit to the left of terminal a and b. Use this result to find the current i through the 5Ω resistor. [12 M]



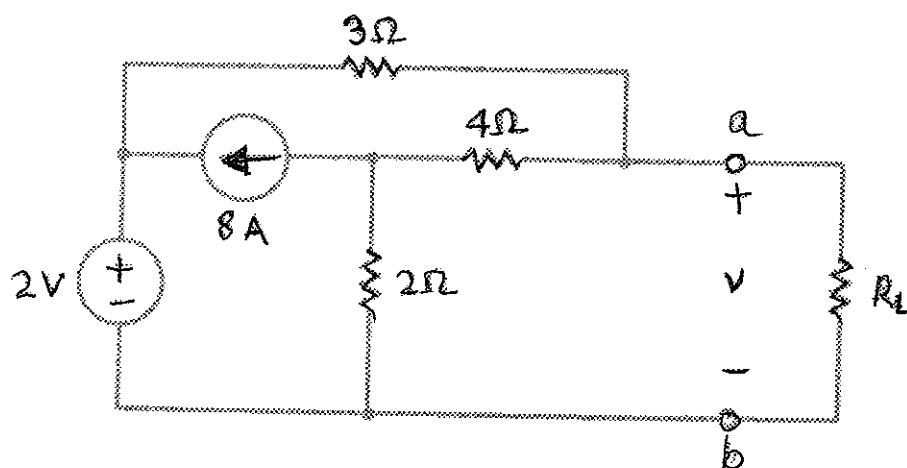Q4.. Consider the circuit shown below.

- Find and draw the Thevenin equivalent of the circuit to the left of terminals a and b.
- Use the Thevenin equivalent circuit to find v and the power absorbed by R_L when $R_L = 3\Omega$.
- Determine the value of R_L , which absorbs the maximum amount of power and find this power. [14M]



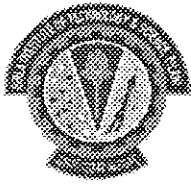

BITS Pilani, Dubai Campus
Dubai International Academic City, Dubai, UAE

I Year, SECOND SEMESTER, 2013 – 14

QUIZ – 2

Course code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **20 minutes**


Date: **11.5.14**
Maximum Marks : **14**
Weightage: **7%**

Name of the student		ID No.
Name of the faculty		Section:

Answer all questions

1. Calculate β for $I_C = 15 \text{ mA}$ and $V_{CE} = 5 \text{ V}$.

[2M]

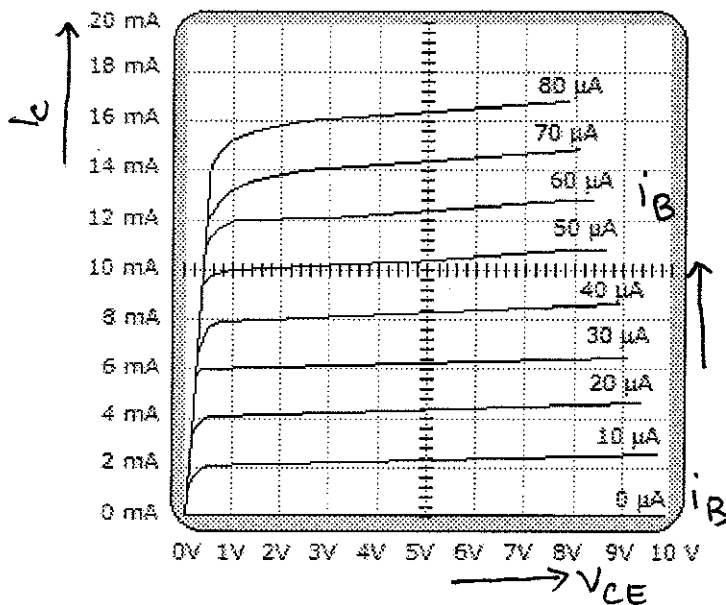

2. A transistor has a β of 250 and a base current, I_B , of $20 \mu\text{A}$. The collector current, I_C , equals _____

[1 M]

3. Which of the following is true for a bipolar transistor?

[1 M]

- (a) Both base and emitter are heavily doped.
- (b) Collector is moderately doped and the emitter is heavily doped.
- (c) The collector is heavily doped and emitter is lightly doped.
- (d) Both the collector and emitter are heavily doped.

4. Draw the circuit symbol for n-channel and p-channel JFET.

[1 M]

5. Write the conditions for v_{DS} and v_{GS} for the JFET to operate in the active region.

[2M]

6. Draw the circuit diagram showing currents and the polarities of the voltages, when npn BJT is in active region in common emitter configuration by using the circuit symbol.

[2M]

7. When a junction transistor is operated under saturated conditions, both the _____ and _____ junction are _____ [1 M]


8. A current ratio of i_C / i_E is usually less than one and is denoted as _____ [1 M]


9. In which region does the JFET behave as a resistor?

[1 M]

10.. Mark I_{DSS} , V_P , and active region in the following graph.

[2 M]

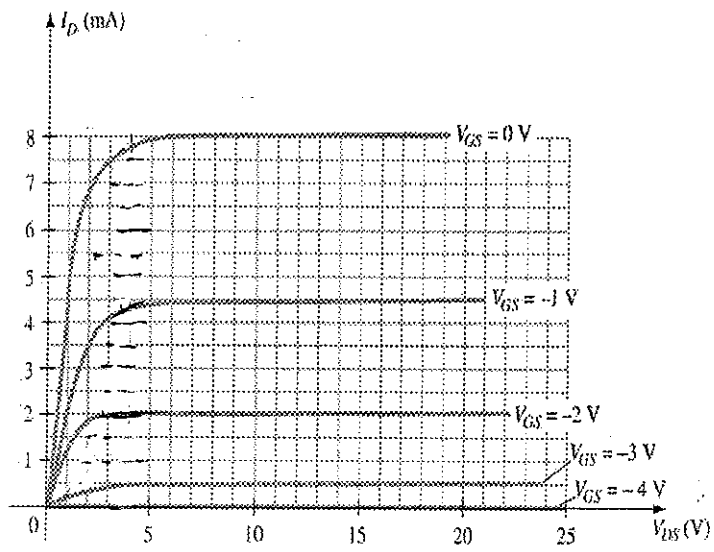

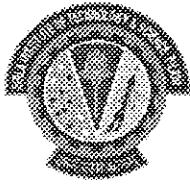

BITS Pilani, Dubai Campus
Dubai International Academic City, Dubai, UAE

I Year, SECOND SEMESTER, 2013 – 14

QUIZ – 2

Course code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **20 minutes**

Date: **11.5.14**
Maximum Marks : **14**
Weightage: **7%**

Name of the student		ID No.
Name of the faculty		Section:


Answer ALL questions

1. A transistor has a β of 250 and a base current, i_B , of $20 \mu A$. The collector current, i_C , equals _____ [1 M]
2. A current ratio of i_C / i_E is usually less than one and is denoted as _____ [1 M]
3. When a junction transistor is operated under saturated conditions, both the _____ and _____ junction are _____ [1 M]
4. Which of the following is true for a bipolar transistor? [1 M]
 - (a) Both base and emitter are heavily doped.
 - (b) Collector is moderately doped and the emitter is heavily doped.
 - (c) The collector is heavily doped and emitter is lightly doped.
 - (d) Both the collector and emitter are heavily doped.
5. Write the conditions for v_{DS} and v_{GS} for the JFET to operate in the active region. [2M]

6. In which region does the JFET behave as a resistor? [1 M]

7. Draw the circuit symbol for n-channel and p-channel JFET. [1 M]

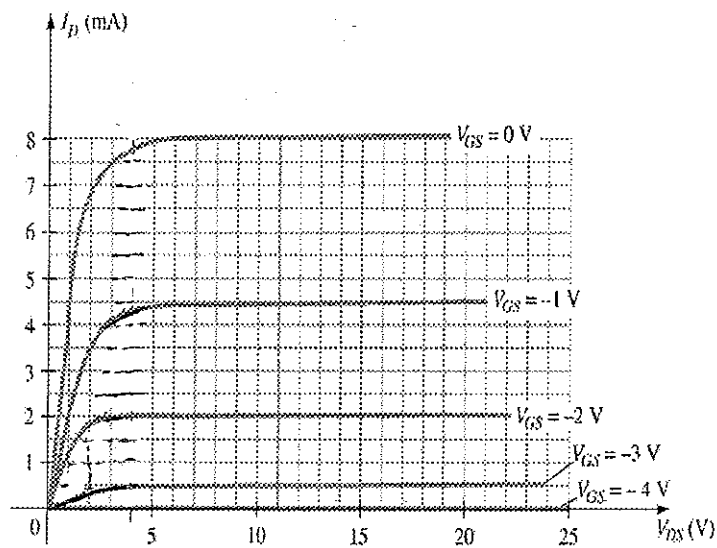
8. Mark I_{DSS} , V_P , and active region in the following graph. [2 M]




9. Draw the circuit diagram showing currents and the polarities of the voltages, when npn BJT is in active region in common emitter configuration by using the circuit symbol. [2M]

10. Calculate β for $I_C = 15 \text{ mA}$ and $V_{CE} = 5 \text{ V}$.

[2M]

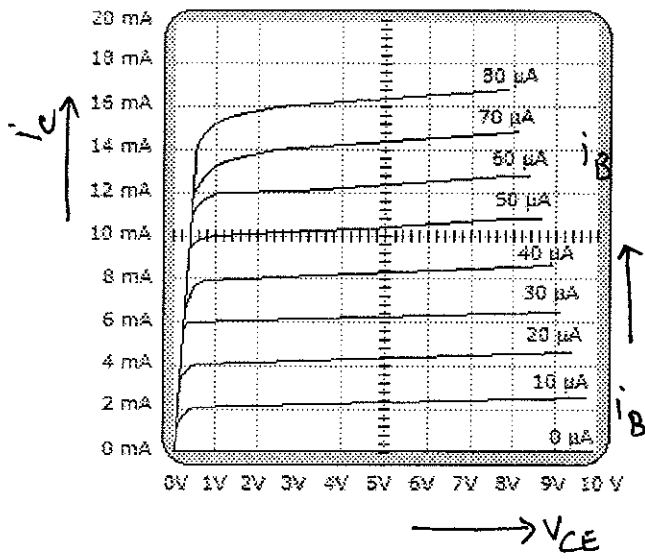

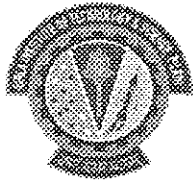

BITS Pilani, Dubai Campus
Dubai International Academic City, Dubai, UAE

I Year, SECOND SEMESTER, 2013 – 14

QUIZ – 1

Course code: **EEE F111**
 Course Title: **Electrical Sciences**
 Duration: **20 minutes**

Date: **23.3.14**
 Maximum Marks : **16**
 Weightage: **8%**


Name of the student		ID No.
Name of the faculty		Section:

Answer ALL questions

- Find the capacitance of a capacitor that stores 8 C of charge at 4 V. [1M]
- Find the total capacitance of two capacitors in series, when both have a value of 150 μF [1M]
- Find the time constant of a 100 μF capacitor in series with a 100 Ω resistor [1M]
- A 4-henry inductor is in series with a variable resistor. The resistance is increased so that the current drops from 6 amps to 2 amps in 2 seconds. What is the voltage induced? [1M]

5. Find the time constant of a 4 H inductor in series with a 100Ω resistor. [1M]

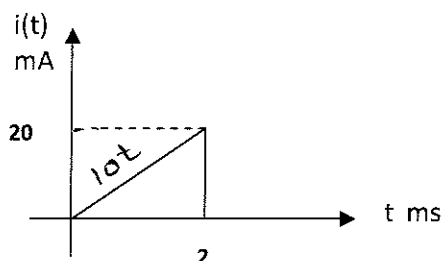6. The current in a 10 mH inductor has the waveform shown in the figure below. Determine the voltage waveform.




Given :

$$i = 10t ; 0 \leq t < 2 \text{ ms}$$
$$i = 20 \text{ mA} ; t \geq 2 \text{ ms}$$

[3M]


7. The voltage across a $25\mu\text{F}$ capacitor is given as $v(t) = 980\sin 377t$. Determine the energy stored by it. [1M]

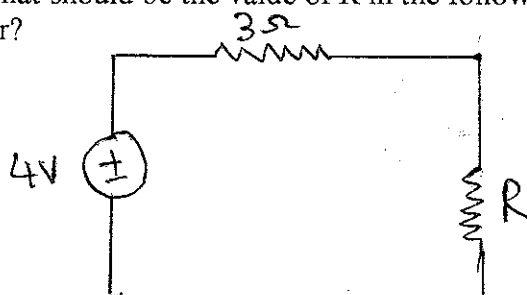8. A) What should be the value of R in the following circuit, for it to absorb the maximum power? [1M]





B) Calculate the maximum power absorbed by R in the circuit shown above. [2M]

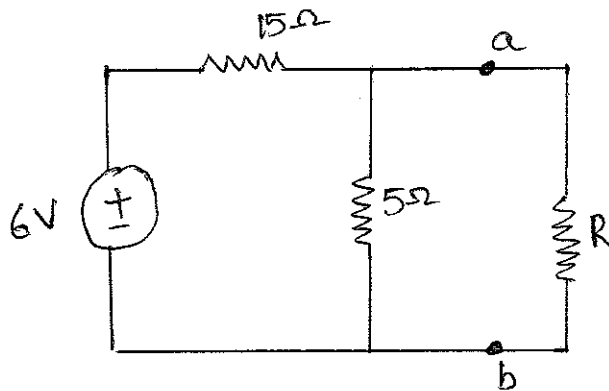9. Draw the Thevenin's equivalent to the left of **a and b** in the circuit shown below. [2M]



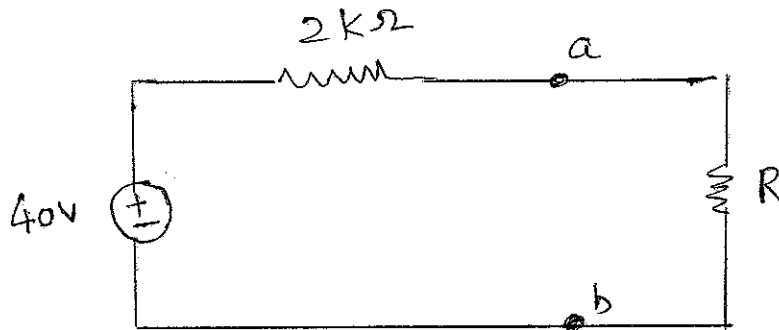10. Draw the Norton's equivalent to the left of **a and b** for the Thevenin's circuit shown below. [2M]



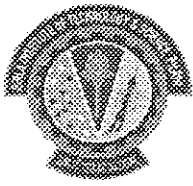

BITS Pilani, Dubai Campus
Dubai International Academic City, Dubai, UAE

I Year, SECOND SEMESTER, 2013 – 14

QUIZ – 1

Course code: **EEE F111**
Course Title: **Electrical Sciences**
Duration: **20 minutes**

Date: **23.3.14**
Maximum Marks : **16**
Weightage: **8%**

Name of the student		ID No.
Name of the faculty		Section:

Answer ALL questions

1. Find the capacitance of a capacitor that stores 8 C of charge at 4 V. [1M]

2. The voltage across a $25\mu\text{F}$ capacitor is given as $v(t) = 980\sin 377t$. Determine the energy stored by it. [1M]

3. Find the time constant of a $100\mu\text{F}$ capacitor in series with a 100Ω resistor [1M]

4. A) What should be the value of R in the following circuit, for it to absorb the maximum power. [1M]


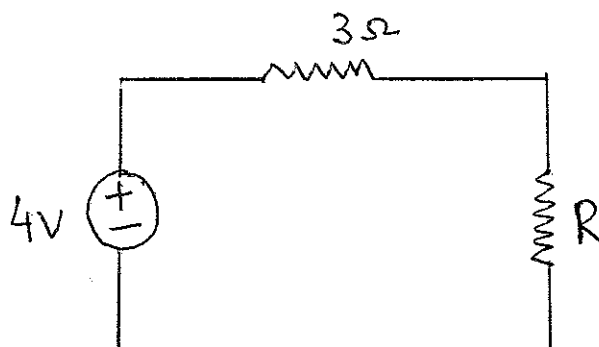



Fig 1.

B) Calculate the maximum power absorbed by R in the circuit shown above. (fig 1) [2M]

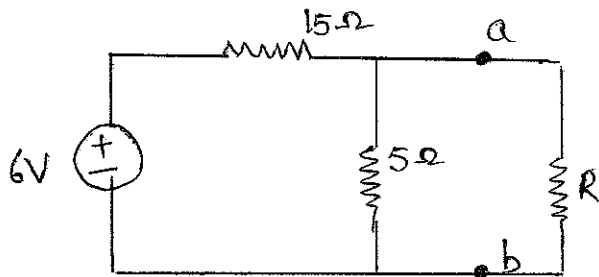5. Draw the Thevenin's equivalent to the left of **a and b** in the circuit shown below. [2M]




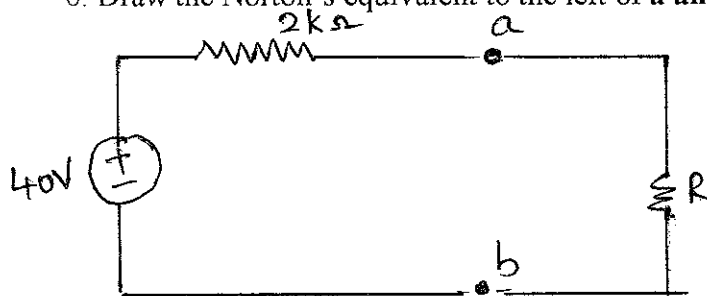6. Draw the Norton's equivalent to the left of **a and b** for the Thevenin's circuit shown below. [2M]



7. Find the total capacitance of two capacitors in series, when both have a value of $150 \mu\text{F}$ [1M]

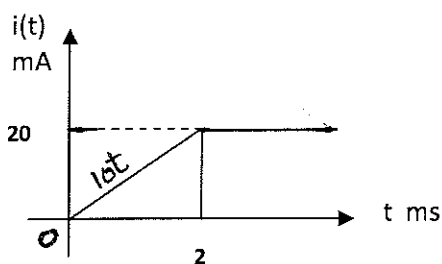8. The current in a 10 mH inductor has the waveform shown in the figure below. Determine the voltage waveform. [3M]



Given: $i = 10t$; $0 \leq t < 2 \text{ ms}$
 $i = 20 \text{ mA}$; $t \geq 2 \text{ ms}$

9. Find the time constant of a 4 H inductor in series with a 100Ω resistor. [1M]

10 A 4-henry inductor is in series with a variable resistor. The resistance is increased so that the current drops from 6 amps to 2 amps in 2 seconds. What is the voltage induced? [1M]