

Write PART A & B & C & D in separate answer sheets.

**PART A**

1. Use mesh analysis to evaluate the three unknown currents  $i_1$ ,  $i_2$  &  $i_3$  in the circuit shown in Figure 1 [5 marks]

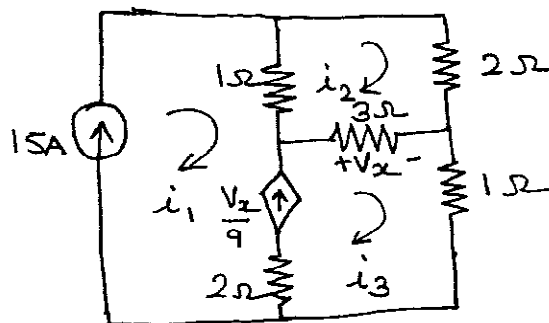


Figure 1

2. For the circuit shown in Figure 2 using thevenin's theorem calculate the current in the  $2\Omega$  resistor [5marks]

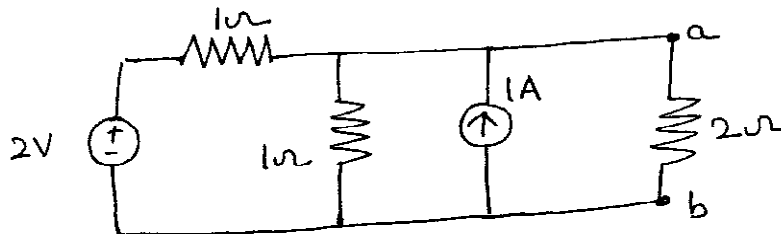


Figure 2

3. Use the principle of superposition to determine the value of  $i_x$  for the circuit shown in Figure 3 [6marks]

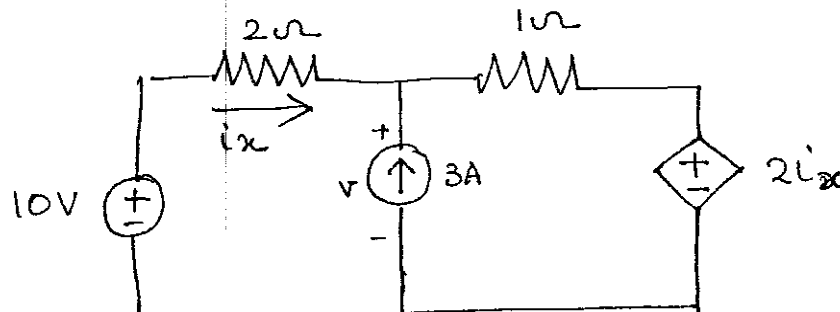


Figure 3

4. Find the value of the adjustable resistance  $R$  which results in maximum power transfer across the terminals  $a$  &  $b$  of the circuit shown in Figure 4. [5marks]

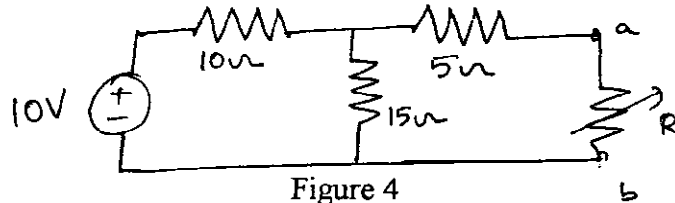


Figure 4

**PART B**

5. Derive the output expression  $V_o$  for the OP -Amp circuit given in Figure 5. [4 marks]

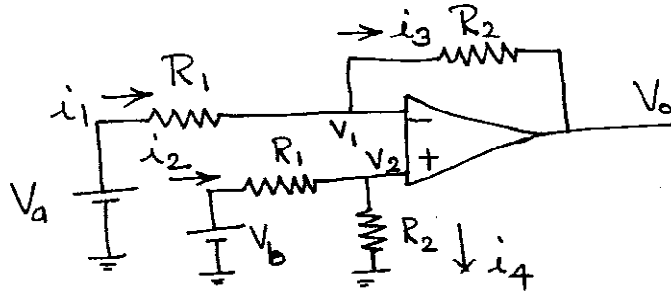


Figure 5

6. For the given circuit shown in Figure 6 find  $V_o$  &  $I$ ,  $V_c$  at  $t < 0$ ,  $t > 0$ ,  $t = 1.3$  m.sec [10 marks]

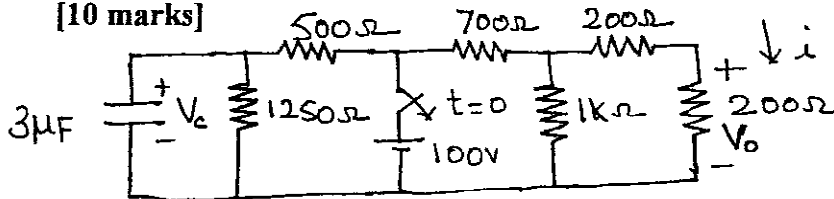


Figure 6

7. For the given circuit shown in Figure 7 the switch  $s$  has been in position 'a' for a long period of time and it is thrown to position 'b' at  $t = 0$ . Determine  $i(t)$  for all  $t$ . [12 marks]

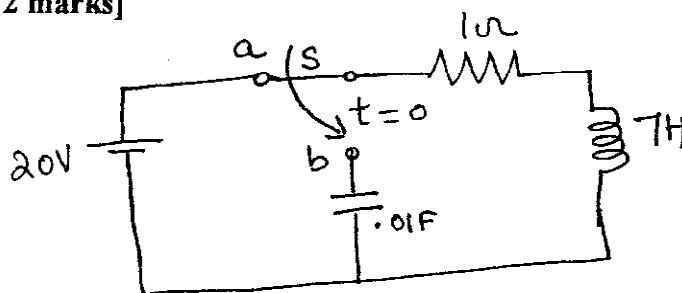


Figure 7

**PART C**

8. Draw the collector static characteristic of a typical P-N-P BJT (made of silicon) in common- base (CB) configuration, clearly indicate boundaries for each region of operation. [6 Marks]

9. For the circuit shown in Figure 8,  $V_{cc} = V_{EE} = 5V$ ;  $R_E = R_C = 2K\Omega$ . Assuming that the transistor is in the active region and that  $\alpha = 1$ , Find  $i_E$ ,  $V_{CB}$  and  $V_{EC}$ . [ 7 marks]

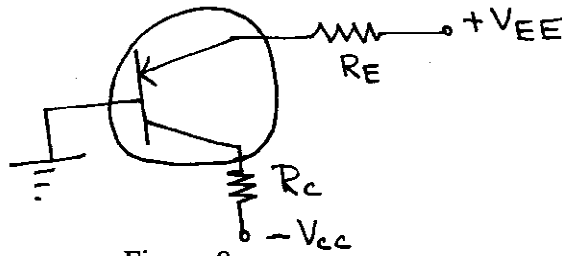


Figure 8

10. For the ideal diode circuit given in Figure 9, the input voltage is  $V_s = 12\text{Sin}\omega t$  V. Determine the output voltage  $V_o$ . [ 7 marks]

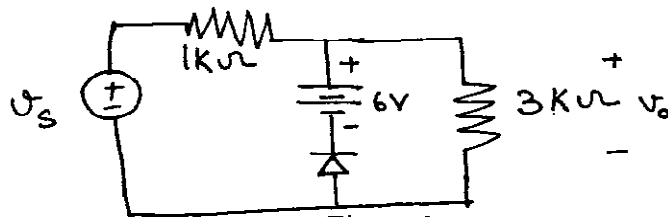


Figure 9

**PART D**

11. For the given circuit in Figure 10, the enhancement MOSFET has  $K = 0.25\text{mA/V}^2$  and  $V_t = 2V$ . Given that  $R_s = 0\Omega$  and  $V_{DD} = 16V$ , determine the value of  $R_D$  for which the enhancement MOSFET will operate on the border between the active and the ohmic regions when  $V_{GG}$  is 4V. [8 marks]

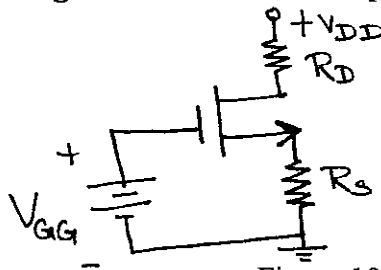


Figure 10

12. Determine the function  $F$  that characteristics the output of the logic circuit shown in Figure 11. Identify the operations performed by writing the truth table. [5 marks]

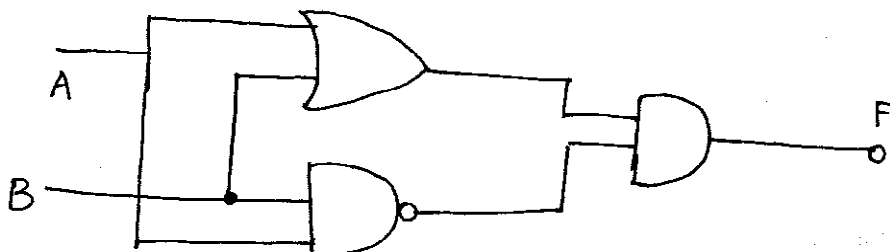


Figure 11

BITS, PILANI - DUBAI ACADEMIC CITY, DUBAI  
 FIRST SEMESTER 2006 - 2007  
 ES UC241 ELECTRICAL SCIENCES - I  
 TEST 2 (OPEN BOOK)

MAXIMUM MARKS: 20

WEIGHTAGE: 20%

DATE: 13/12/07

DURATION: 50 MINUTES

1. For the circuit shown in Figure 1, the switch is open and steady state is reached. If the switch is closed at  $t=0$ ; find  $i(t)$ . [5 marks]

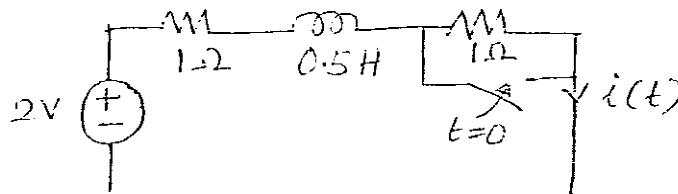


Figure 1

2. For the circuit shown in Figure 2, the switch has been in position 'a' for a long time. At  $t=0$  the switch is thrown to position 'b'. Determine  $i(t)$  for all  $t$ . [5 marks]

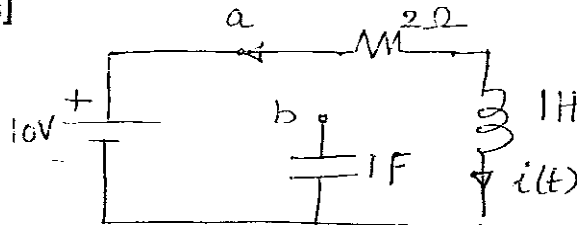


Figure 2

3. For the diode circuit shown in figure 3,  $V_s = 2V$  and the silicon diode has a saturation current of 1 nA at 300K. Given that  $v = 0.7 V$ . Find  $R_2$  when  $R_1 = 1 k\Omega$ . [5 marks]

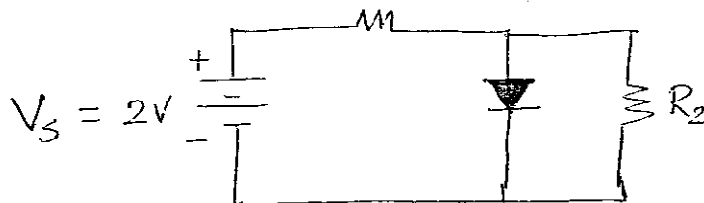


Figure 3

4. Determine the minimum and maximum load currents for which the zener diode in Figure 4 will maintain regulation. What is the minimum value of  $R_L$  that can be used?

$V_z = 12 V$ ,  $I_{z(min)} = 1 mA$ ,  $I_{z(max)} = 50 mA$ . Assume  $V_z$  remains constant at 12 V over the range of current values. [5 marks]

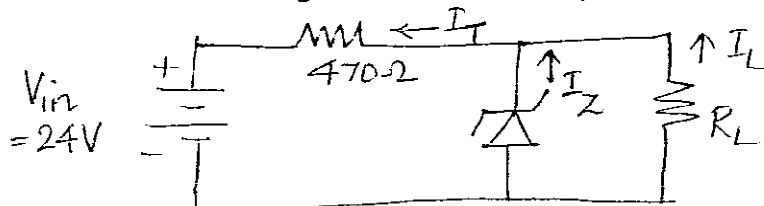


Figure 4

BITS, PILANI – DUBAI, ACADEMIC CITY, DUBAI  
 FIRST SEMESTER 2007 – 2008  
 ES UC241 ELECTRICAL SCIENCES – I  
 TEST 1(CLOSED BOOK)

MAXIMUM MARKS: 25  
 DATE: 28/10/07

WEIGHTAGE: 25%  
 DURATION: 50 MINUTES

1. For the circuit shown in Figure 1, find maximum power absorbed across load resistance  $5\ \Omega$ . [7 marks]

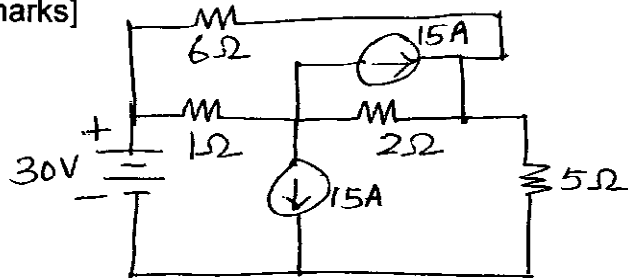


Figure 1

2. For the circuit shown in Figure 2, find current  $I$  to make  $V_1$  to zero. [6 marks] Apply nodal analysis.

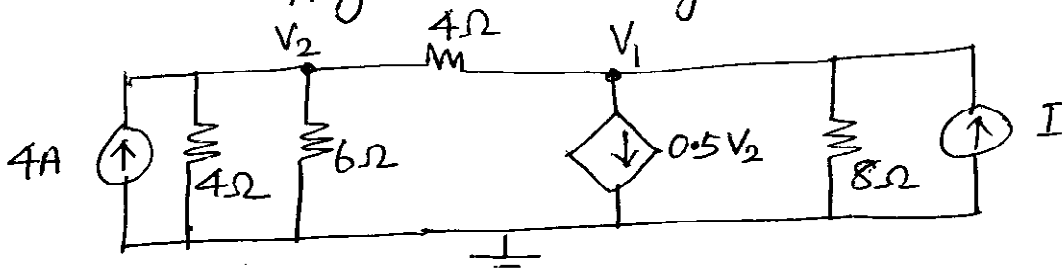


Figure 2

3. Consider the circuit shown in Figure 3, Find the portion of  $I$  and  $V$  that are due to the  $12\text{-V}$  voltage source. (b) Find the portion of  $I$  and  $V$  that are due to the  $6\text{-V}$  voltage source. (c) Find the portion of  $I$  and  $V$  that are due to the  $6\text{-A}$  current source. [7 marks]

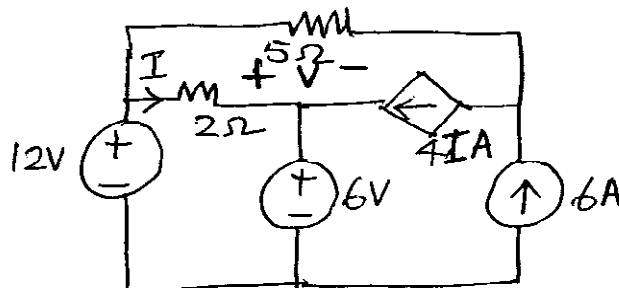


Figure 3

4. Design a non-inverting op-amp circuit for which the gain is 6 and total resistance used is  $120\text{ K}\ \Omega$ . [5 marks]