

Write PART A & B & C in separate answer sheets  
Answer all questions

### PART A

1. Consider the series parallel circuit shown in Figure 1 [12 Marks]
- Find  $V_s$  when  $v_1=2V$
  - Find  $V_s$  when  $i_3=3A$
  - Find  $V_s$  when  $i_5=4A$
  - Find the Power dissipated in  $5\Omega$  resistance when  $v_1=4V$

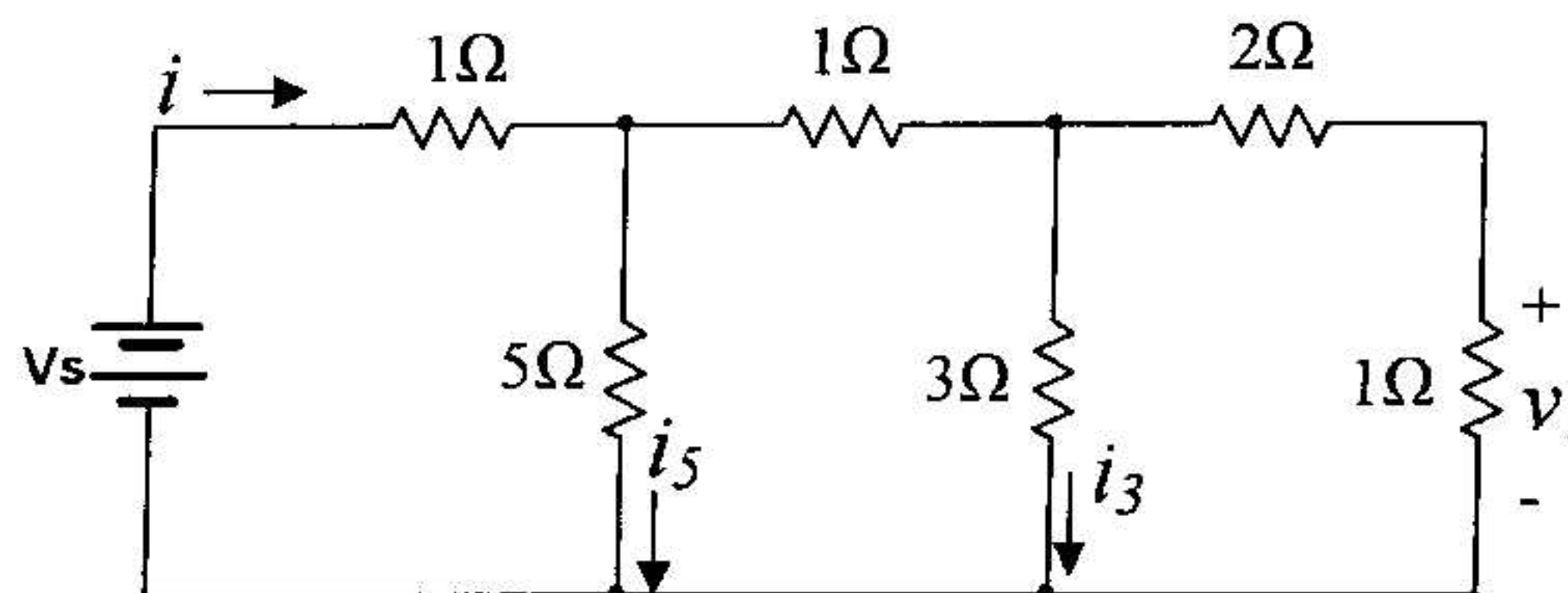


Figure 1

2. Find the node voltages for the circuit shown in Figure 2. [12 marks]

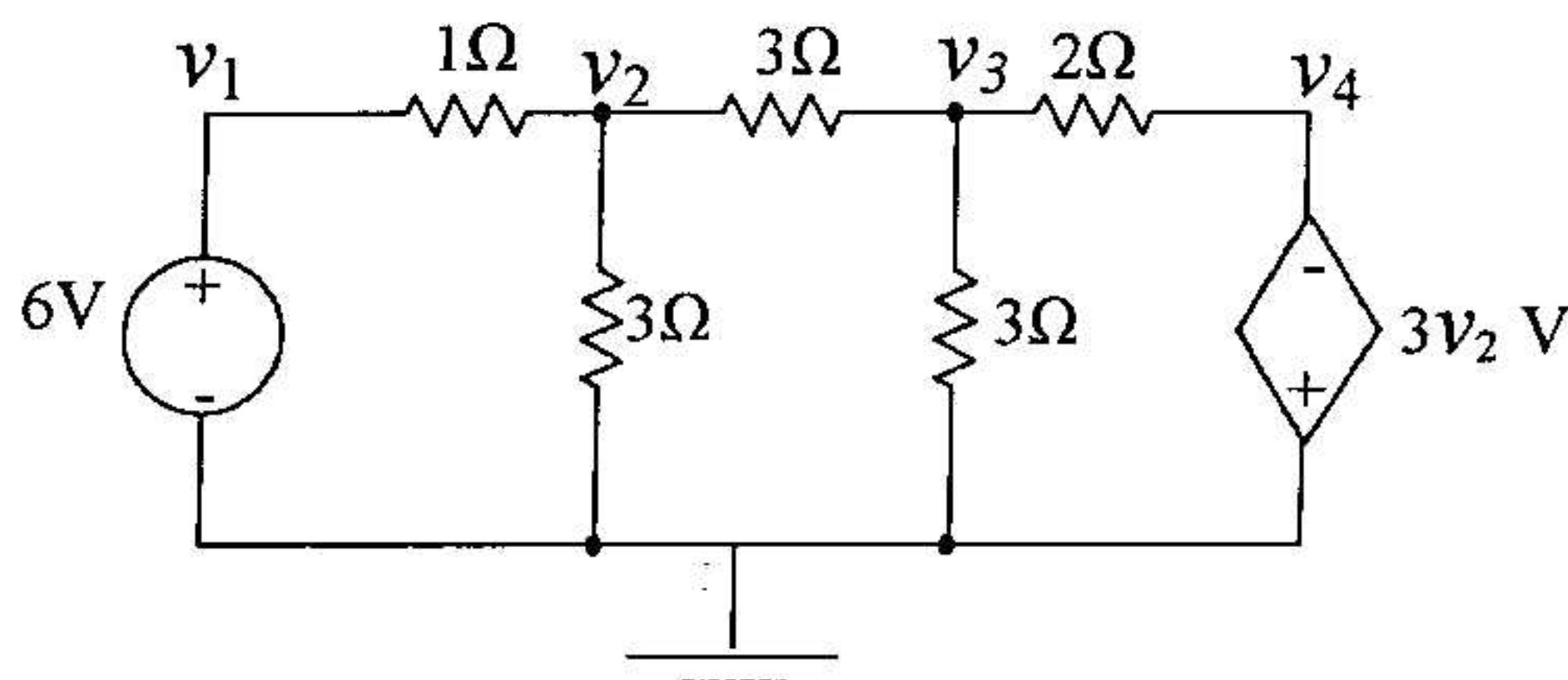


Figure 2

3. For the circuit shown in Figure 3 a) Find the Thevenin equivalent of the resulting circuit to the left of terminals a and b. b) Use the Thevenin's equivalent circuit to find the power absorbed by  $R_L = 2\Omega$ . c) Determine the value of  $R_L$  which absorbs the maximum amount of power and find this power. [12 Marks]

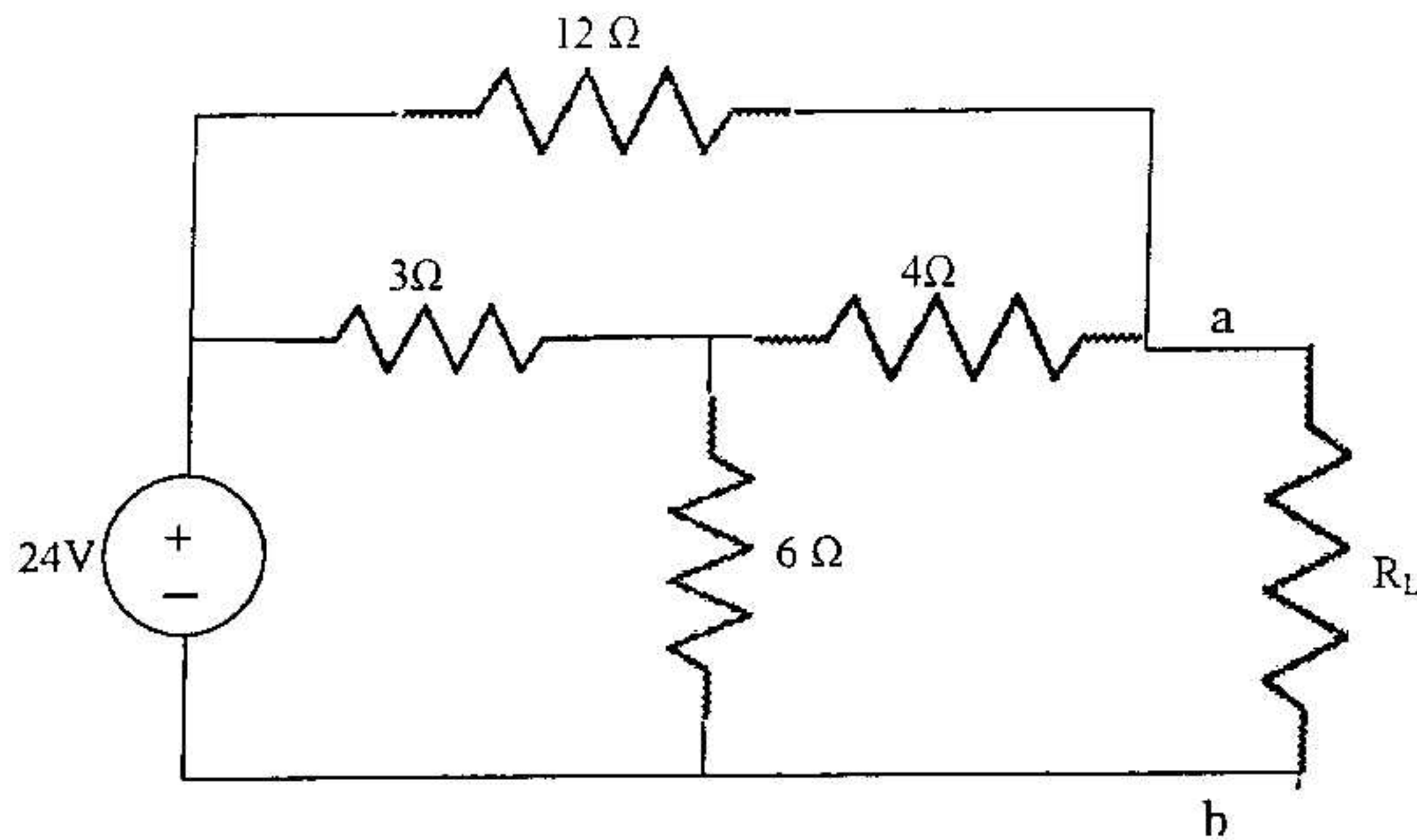


Figure 3

4. Draw the circuit diagram of OPAMP differential amplifier and obtain the expression for the output voltage  $V_o$  [12 Marks]

**PART B**

5. For the circuit shown in Figure 4 find  $V_c$  and  $V_R$  at time  $t < 0$ ,  $t > 0$ ,  $t = 1.5$  m sec. [15 marks]

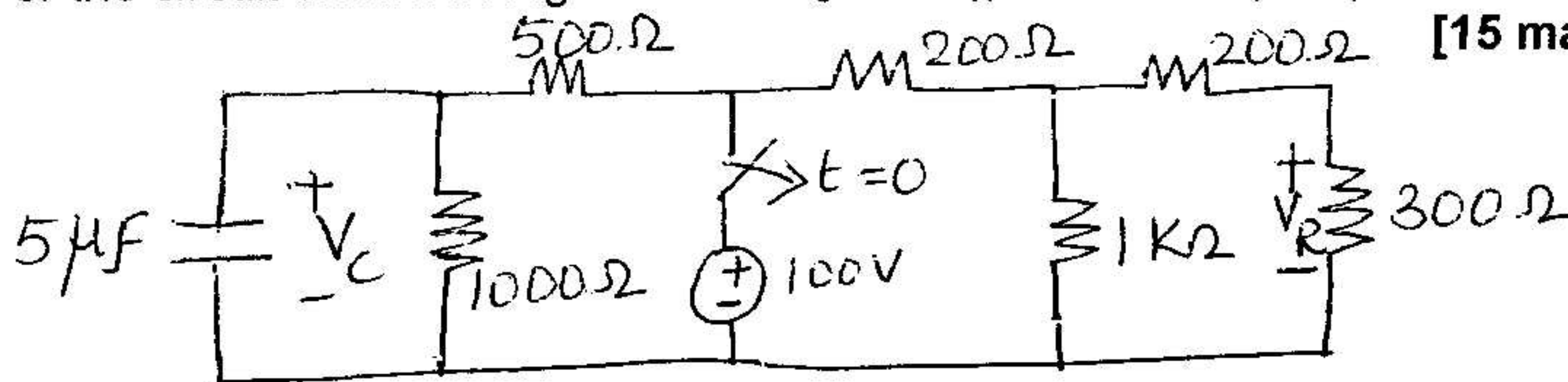


Figure 4

6. For the circuit shown in Figure 5 find the complete response for the current flow through the inductor,  $i_L(0^-)$  and  $i_L(0^+)$  and  $i_L(t)$  for all values of  $t$ . [9 marks]

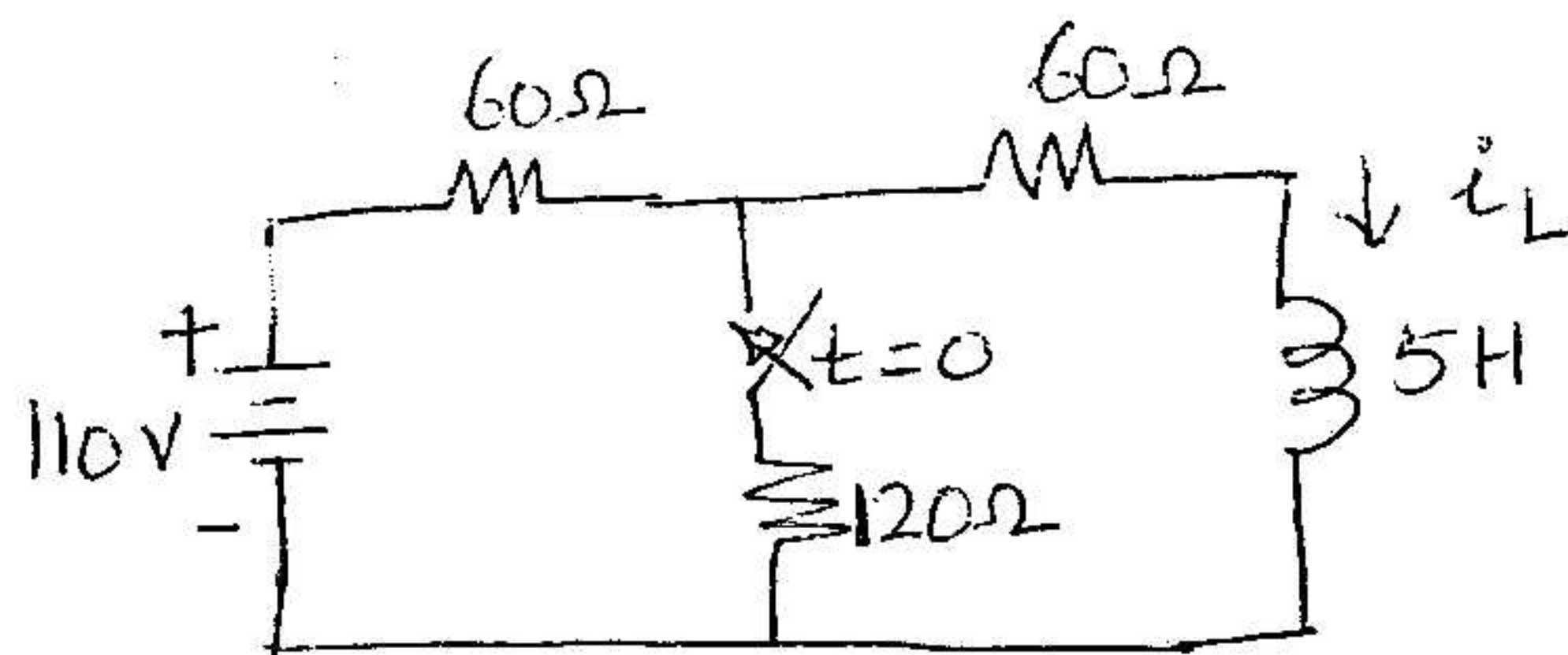


Figure 5



7. For the ideal diode circuit given in Figure 6, determine the output voltage  $V_o$  and Sketch this function. [12 Marks]

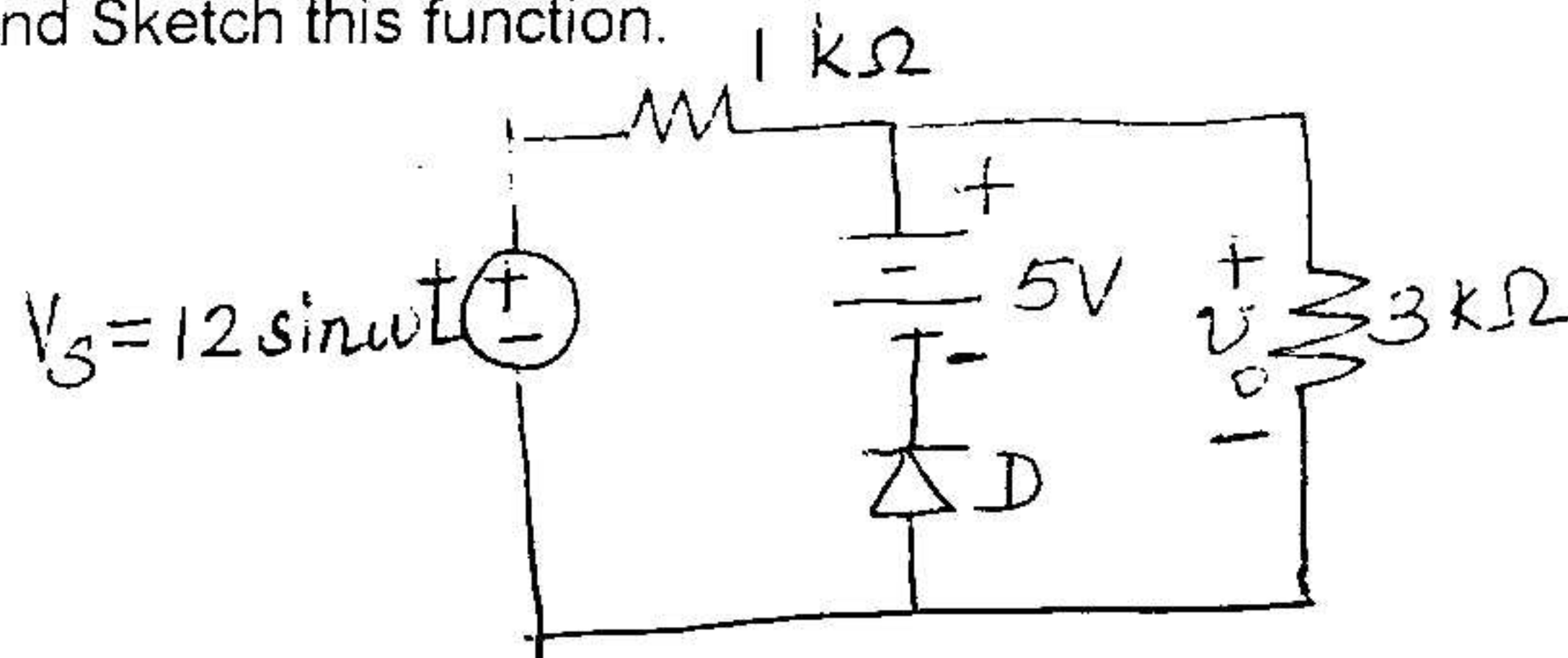


Figure 6

8. The Zener diode in the voltage regulator circuit shown in Figure 7 has a breakdown voltage of 9V and is to operate with a reverse current between 10mA and 100mA. Given that  $R=200\Omega$ , Find

- Range of load resistance ( $R_L$ ) that results in a 9V load voltage when  $V_s=24V$ .
- Range of Supply voltage ( $V_s$ ) that results in a 9 V load voltage when  $R_L=600\Omega$ .

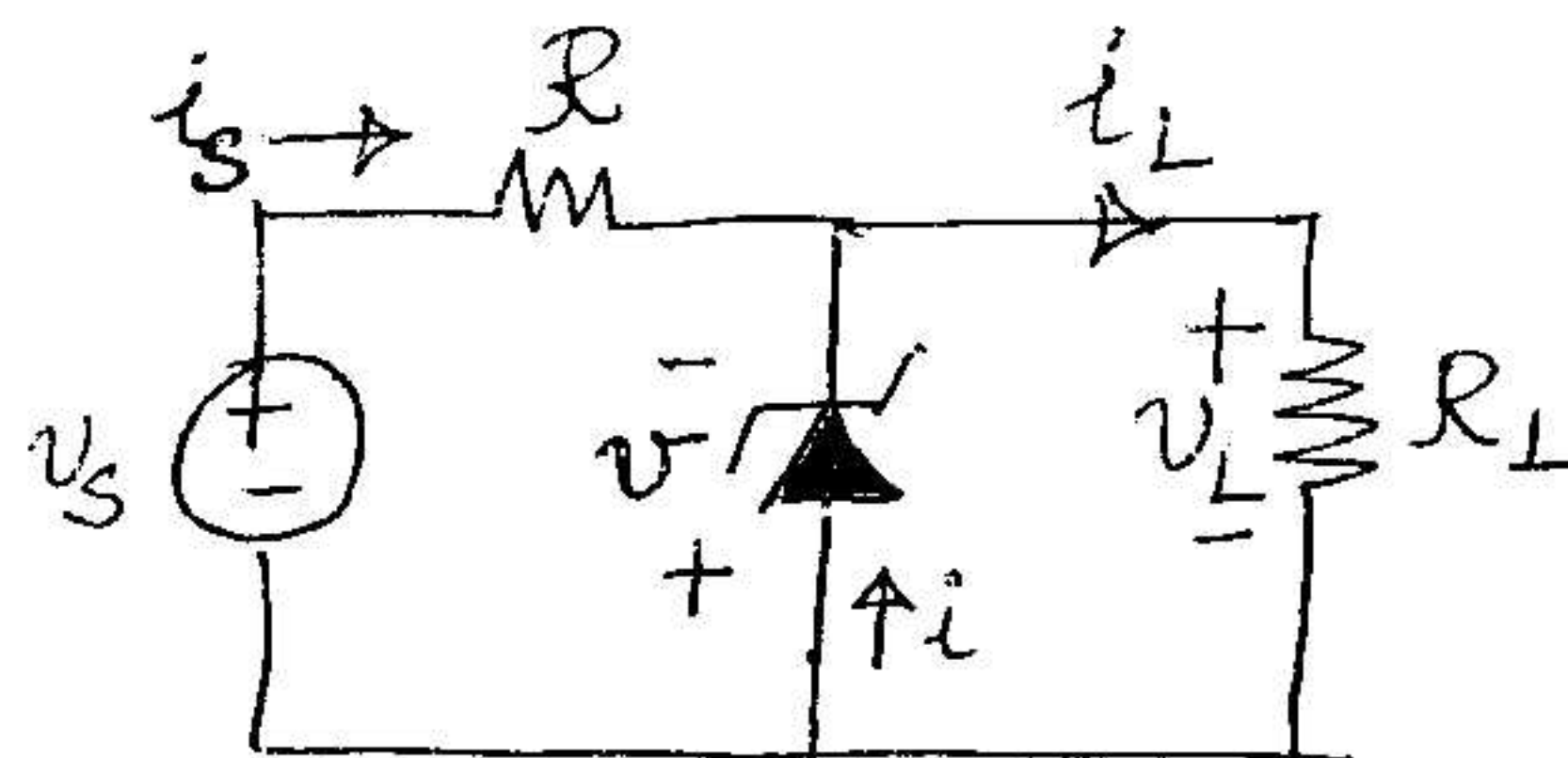


Figure 7

### PART C

9. For the circuit given in Figure 8, suppose that  $R_C=3\text{ k}\Omega$ ,  $R_B=50\text{ k}\Omega$ ,  $V_{BB} = V_{CC}= 5V$  and  $\beta=100$ . Assume that the BJT operates in the active region and find  $i_B$ ,  $i_C$  and  $v_{CE}$ . Comment about the assumption made. [8 marks]

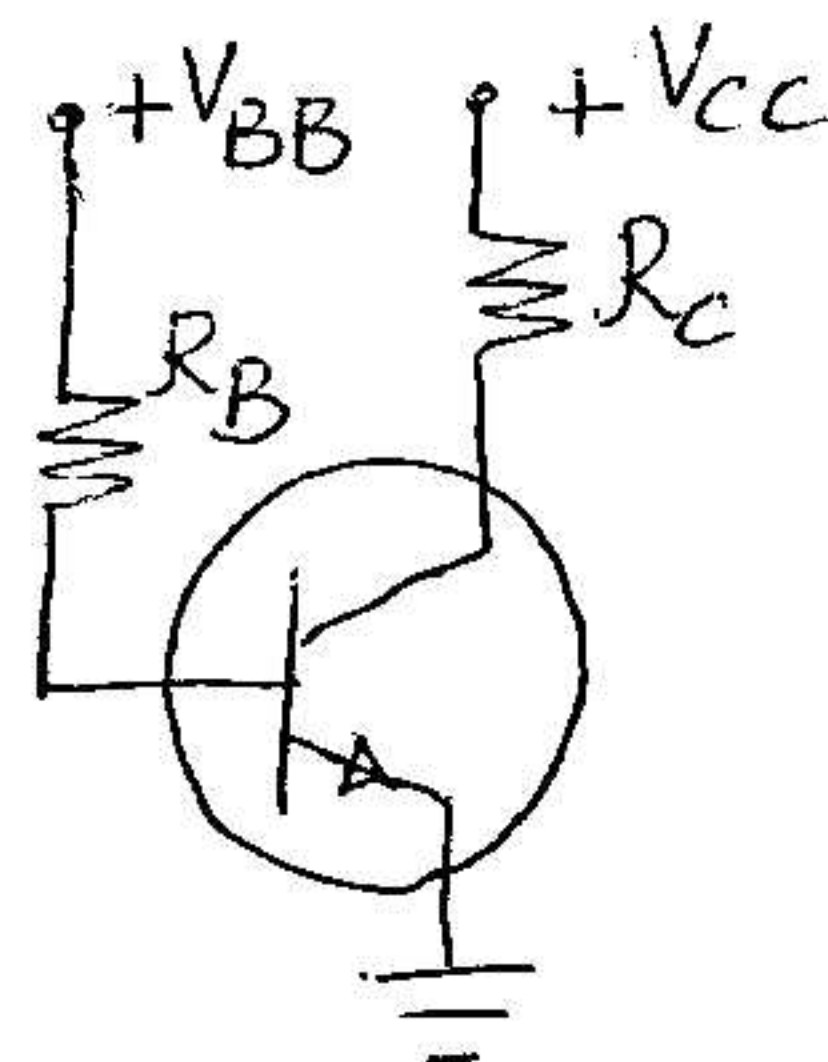


Figure 8

10. For the circuit shown in Figure 9, the enhancement MOSFET has  $K=0.25 \text{ mA/V}^2$  and  $V_t=2 \text{ V}$ . Given that  $R_S=0 \Omega$  and  $V_{DD} = 12 \text{ V}$ , determine the value of  $R_D$  for which the MOSFET will operate on the border between the active and ohmic regions when  $V_{GG}=4 \text{ V}$ . **[8 marks]**

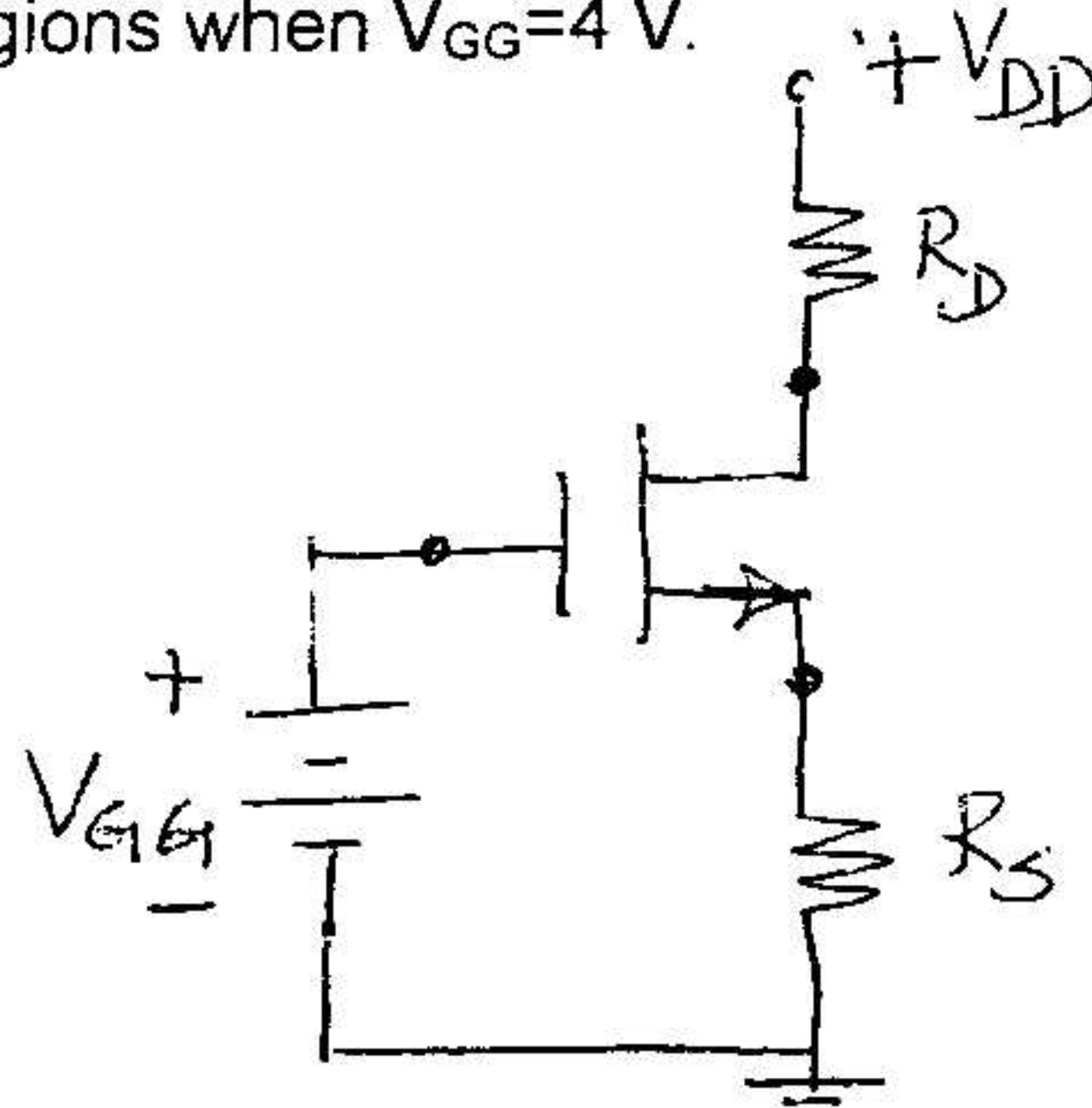


Figure 9

11. Use De Morgan's theorem to obtain a NOR-gate realisation of the expression

$$Y = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C) \quad \text{[4 marks]}$$

12. Draw the drain characteristics of a p-channel JFET, showing typical values.

**[4 marks]**



**BITS, PILANI – DUBAI, ACADEMIC CITY, DUBAI**  
**FIRST SEMESTER 2009 – 2010**  
**ES C241 ELECTRICAL SCIENCES – I**  
**TEST 2(OPEN BOOK)**

**MAXIMUM MARKS: 60**  
**DATE: 15/10/09**

**WEIGHTAGE: 20%**  
**DURATION: 50 MINUTES**

1. For the circuit shown in Figure 1, suppose that  $i_s(t) = 10 \text{ A}$  for  $t < 0 \text{ s}$  and  $i_s(t) = 0 \text{ A}$  for  $t \geq 0 \text{ s}$ . Determine (i) the capacitor voltage  $v(t)$  for all time  $t$  and sketch this function. (ii) Hence find current through the capacitor  $i(t)$  for all time  $t$  and sketch this function. **[12 marks]**

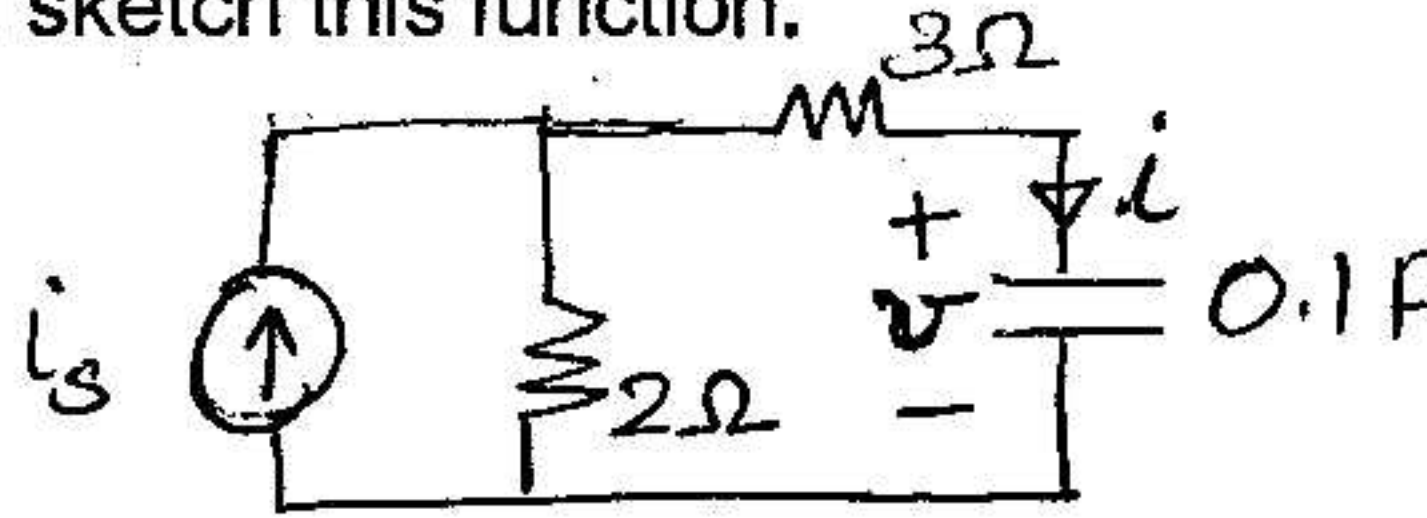


Figure 1

2. The input voltage to a clipper circuit shown in the figure below is  $V_s = 4 \sin \omega t \text{ V}$ . Determine the output voltage  $V_o$  and sketch this function. **[12 marks]**

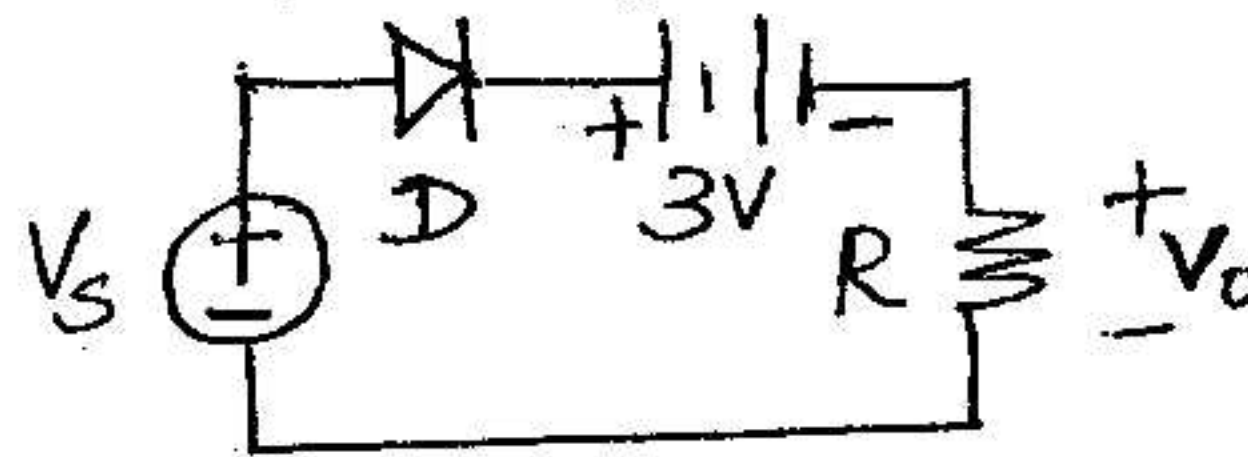


Figure 2

3. For the circuit shown in Figure 3, find the complete response of the current flow through the inductor for all values of  $t$ . **[12 marks]**

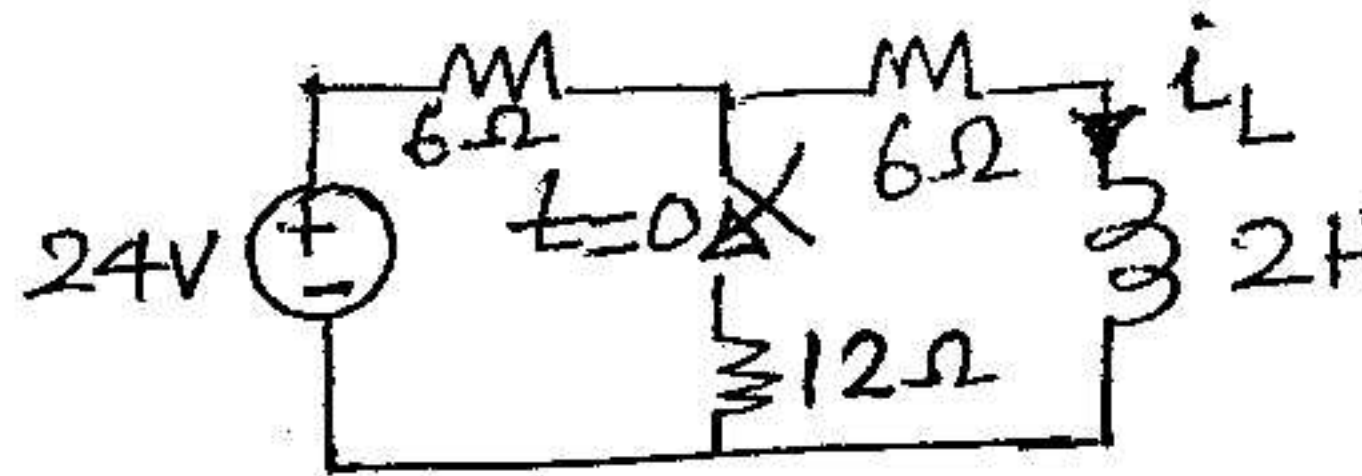


Figure 3

4. The zener diode in the voltage regulator circuit given in Figure no. 4 has a breakdown voltage of 9V. Suppose that a diode has a resistance of  $100 \Omega$  in the breakdown state and the diode is to operate with a reverse current between 10 and 100mA. **[12 marks]**

Find the range of  $v_s$  for the case that  $R=200 \Omega$  and  $R_L=6 \Omega$

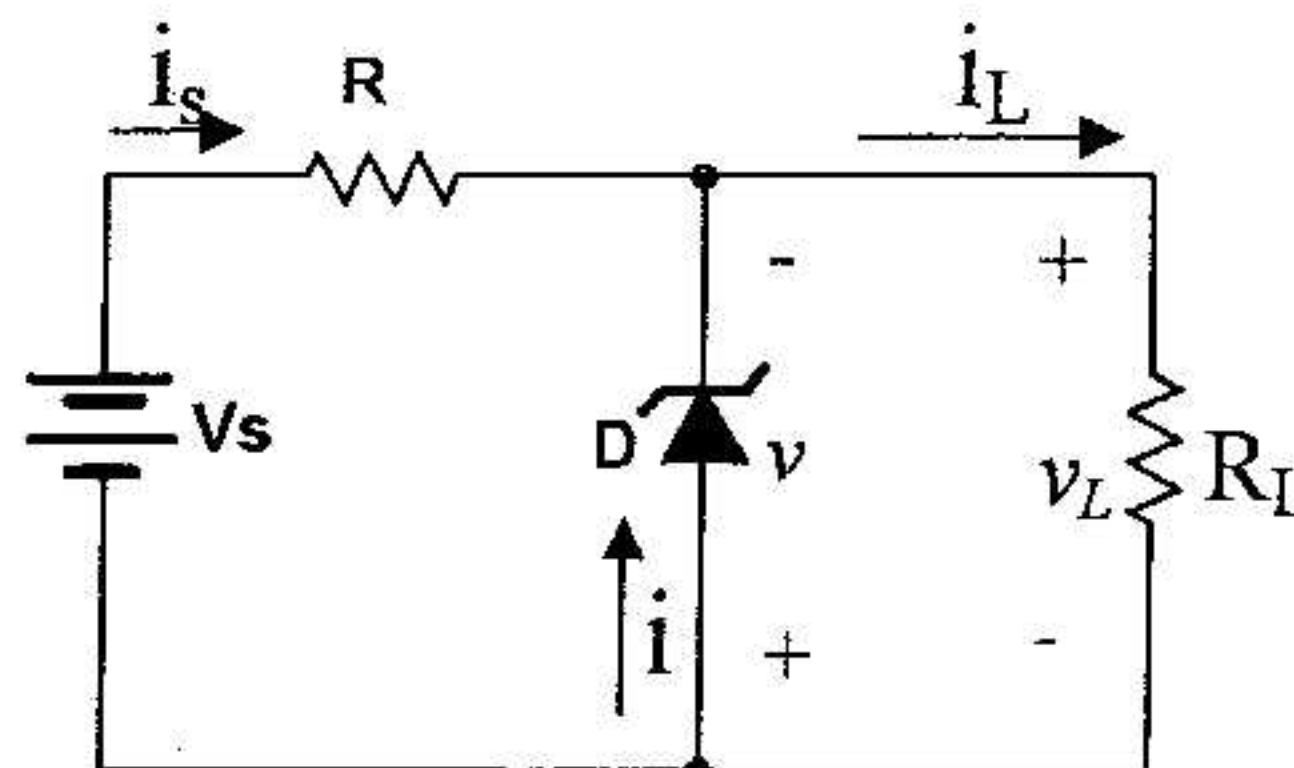


Figure 4

5. Consider a series RLC circuit with  $L = 1.7 \text{ H}$ ,  $R = 2800 \Omega$ ,  $C = 0.001 \mu\text{F}$ ,  $i(0) = 2 \text{ mA}$  and Capacitor voltage  $V_c(0) = 2 \text{ V}$ . Sketch  $i(t)$  **[12 marks]**



**BITS, PILANI – DUBAI, ACADEMIC CITY, DUBAI**  
**FIRST SEMESTER 2009 – 2010**  
**ES C241 ELECTRICAL SCIENCES – I**  
**TEST 1(CLOSED BOOK)**

**MAXIMUM MARKS: 25**  
**DATE: 27/09/09**

**WEIGHTAGE: 25%**  
**DURATION: 50 MINUTES**

1. Consider the circuit shown in Figure 1. Use the current divider formula to find  $i_1, i_2, i_3, i_4, i_5$  and  $i_6$ . [6 marks]

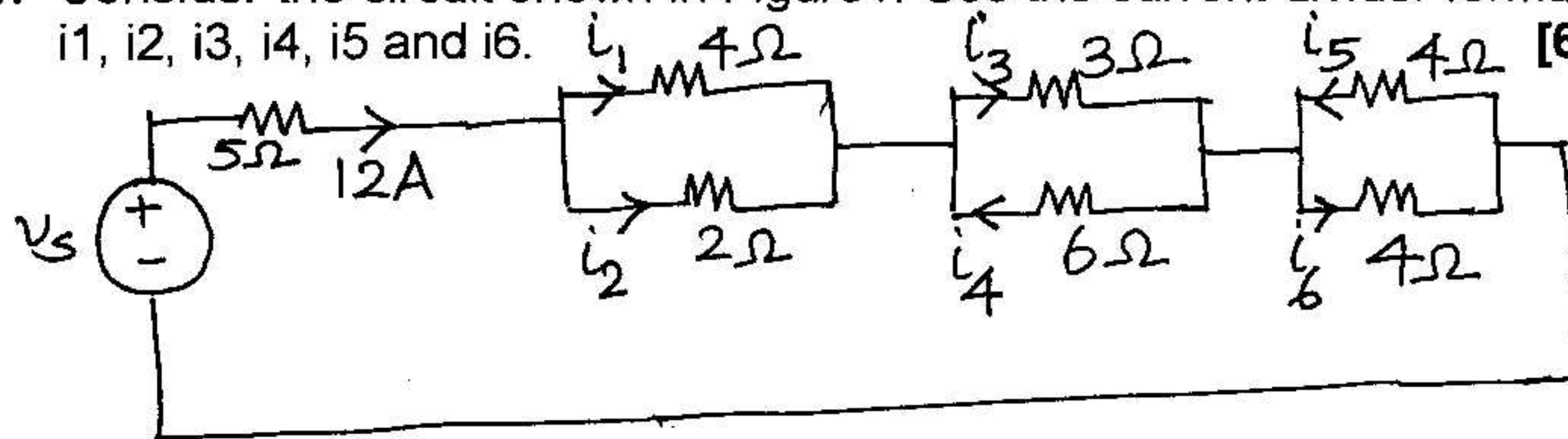


Figure 1

2. For the circuit shown in Figure 2, find current  $I$ . [5 marks]

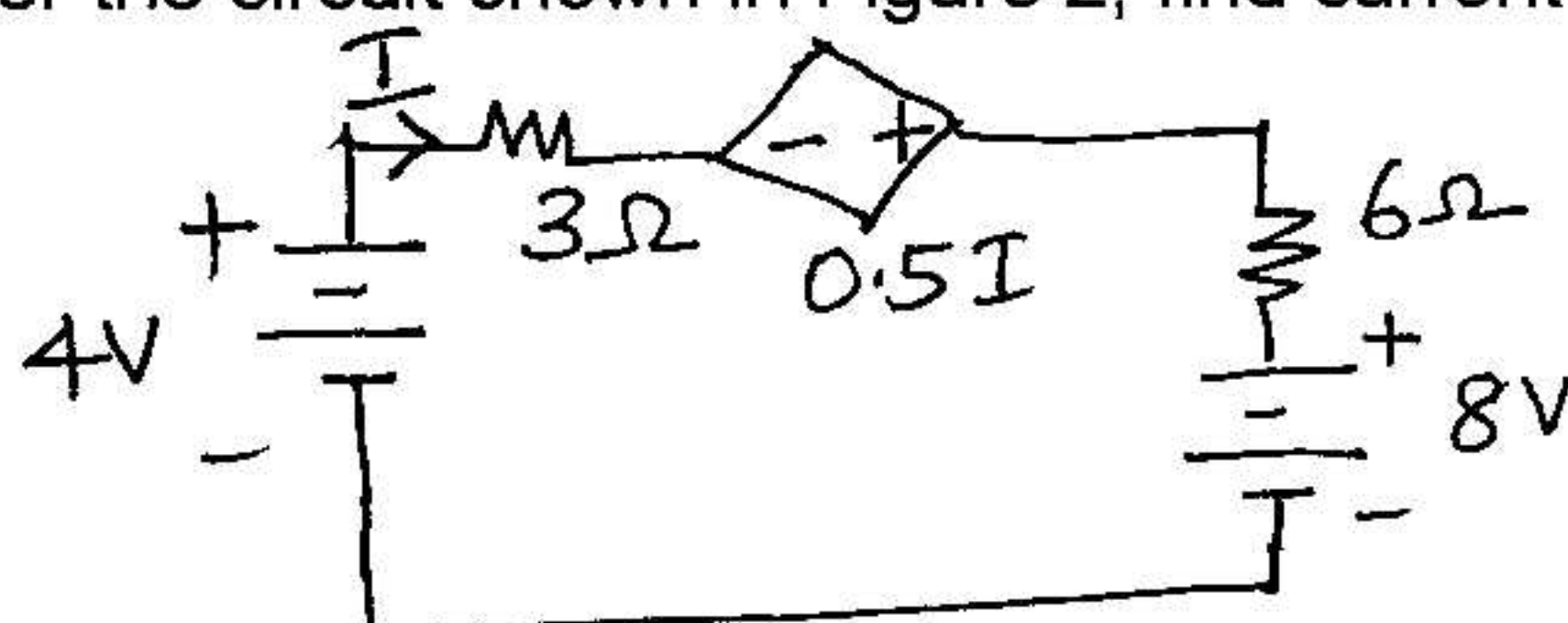


Figure 2

3. For the circuit shown in Figure 3, using nodal analysis find the voltages  $V_1, V_2$  and  $V_3$ . [7 marks]

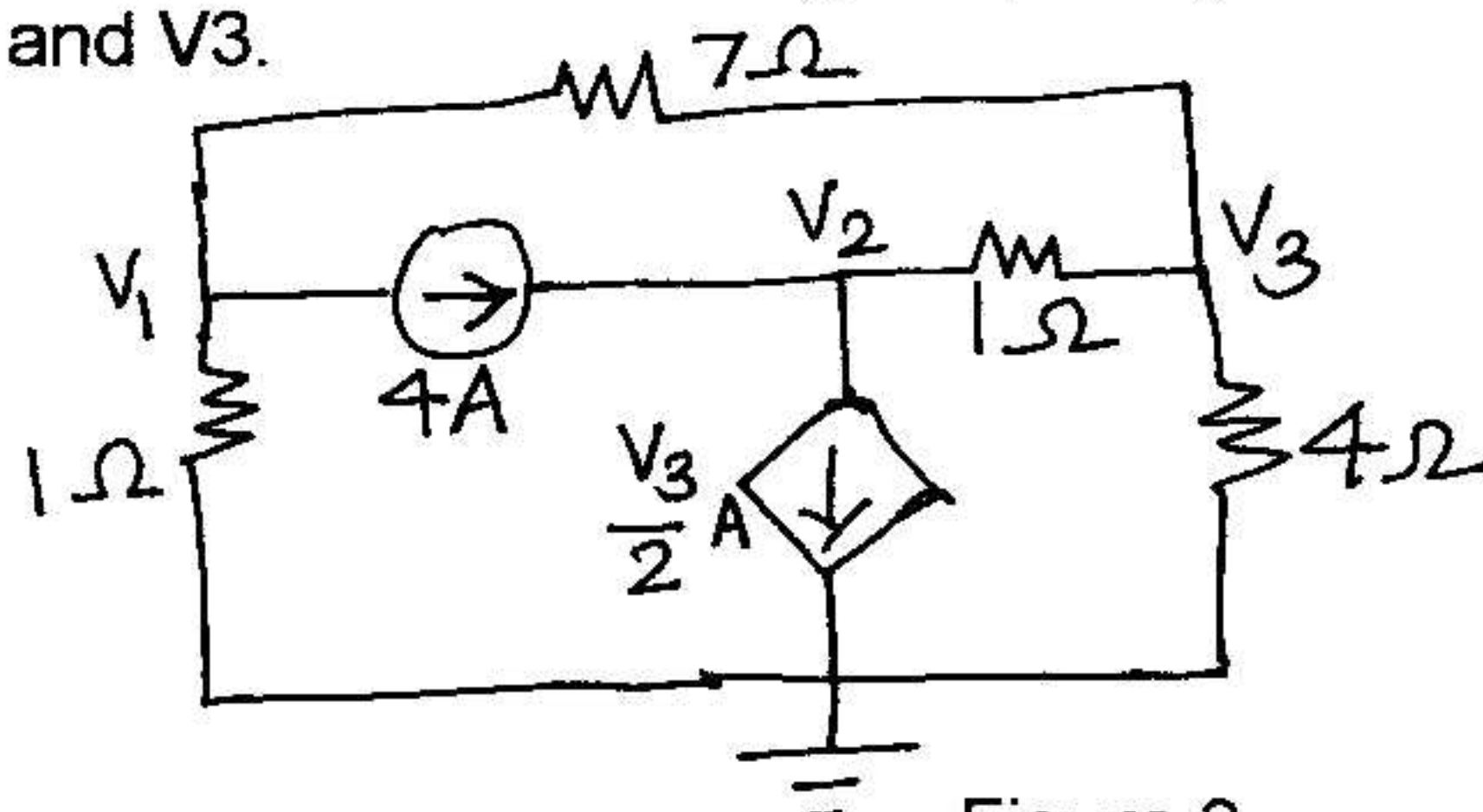


Figure 3

4. For the circuit shown in Figure 4, using mesh analysis find the mesh currents  $i_1, i_2$ , and  $i_3$ . [7 marks]

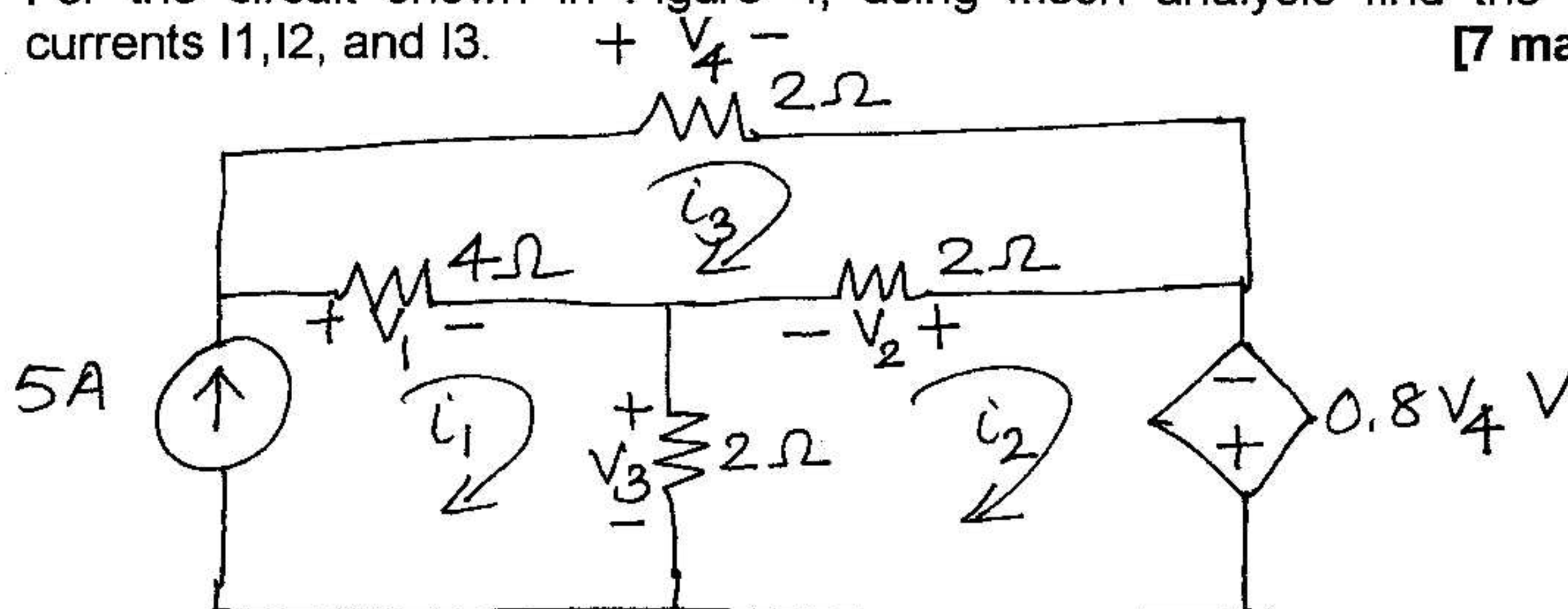


Figure 4

BITS, PILANI – INTERNATIONAL ACADEMIC CITY, DUBAI

FIRST SEMESTER 2009 – 2010

ES UC 241 ELECTRICAL SCIENCES – I

QUIZ 2 (CLOSED BOOK)

MAXIMUM MARKS: 21

DATE: 15.12.09

WEIGHTAGE: 7 %


DURATION: 25 MINUTES

NAME:

Id. No.:

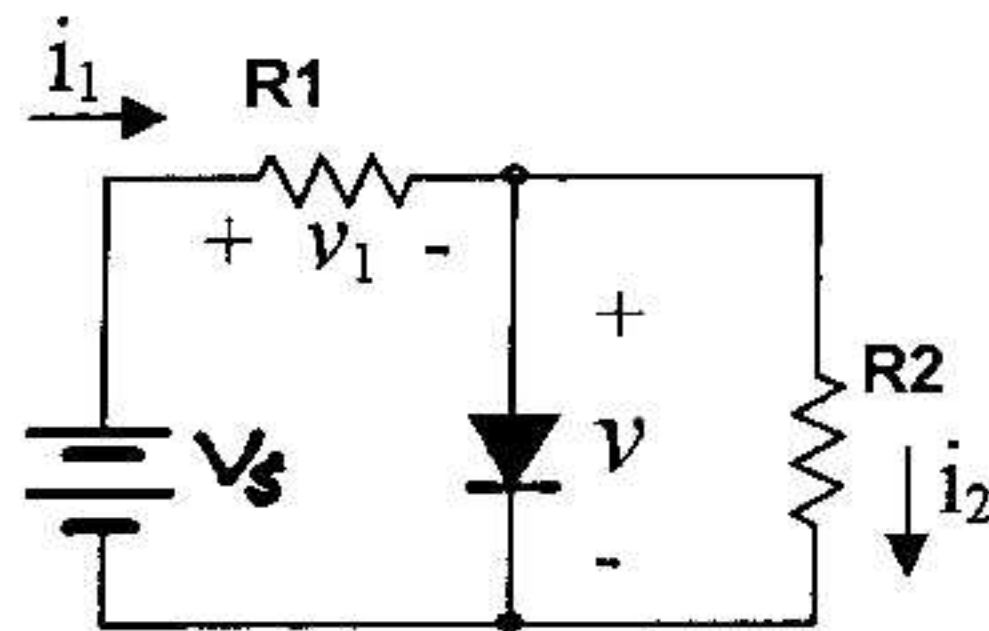1. What kind of a device is a diode? [1 Mark]
  - a) Bilateral
  - b) Linear
  - c) Nonlinear
  - d) Unipolar
2. Which of these is the best description of a Zener diode? [1 Mark]
  - a) It is a rectifier diode
  - b) It is a constant voltage device
  - c) It is a constant current device
  - d) It works in the forward region
3. For a silicon diode the saturation current at 300K is 10 nA. Find the saturation current at temperature 316 K. [2 marks]

**Ans:**
- 4) For the diode circuit shown  $V_s = 2$  volts and the silicon diode has a saturation current of 1 nA at 300 K. Given that  $v = 0.7$  volts,  $\eta = 2$ , find  $R_2$  when  $R_1 = 1 \text{ K}\Omega$ . [4 marks]



**Ans:**  $v_1 =$   $i_1 =$   $i_2 =$   $R_2 =$

- 5) In an npn transistor with Common Emitter configuration, is operating under active region. Its collector current is 4.9 mA, and the emitter current is 5 mA. The value of Alpha ( $\alpha$ ) is \_\_\_\_\_ and beta ( $\beta$ ) is \_\_\_\_\_ [2 marks]

- 6) In a pnp transistor with Common Base configuration, is operated with Emitter-Base junction forward biased and Collector-Base junction reverse biased. Neglecting the total reverse current  $I_{CO}$ , a reasonable approximation relating the collector current to the emitter current is \_\_\_\_\_ [2 marks]



7) In an npn transistor with Common Emitter configuration, the excessive current resulting from transistor breakdown can be due to either \_\_\_\_\_ or to another phenomenon known as \_\_\_\_\_.

[2 marks]

(8) Which of the following relation is correct in the case of BJT

[1 mark]

- (a)  $\alpha = \beta / (1 - \beta)$
- (b)  $\alpha = \beta / (1 + \beta)$
- (c)  $\beta = (\alpha + 1) / \alpha$
- (d)  $\beta = (\alpha - 1) / \alpha$


(9) Draw the circuit diagram for zener voltage regulator

[2 marks]

**Ans:**

10. For the circuit shown below find the voltage across the capacitor  $V_c$  at steady state ( $t = \infty$ ).


[3 marks]

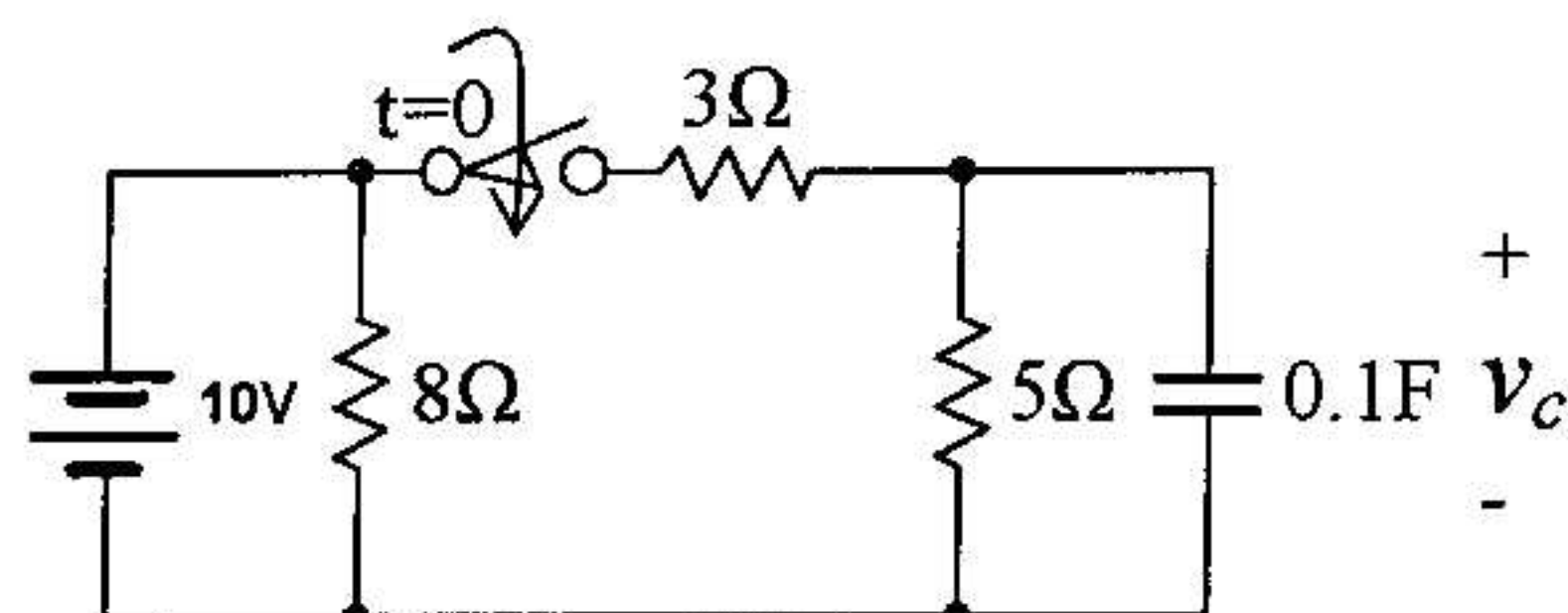

**Ans:.....**

11. In the bipolar transistor output characteristics shown below, what region is represented by the symbol 'x'?

[1 Mark]

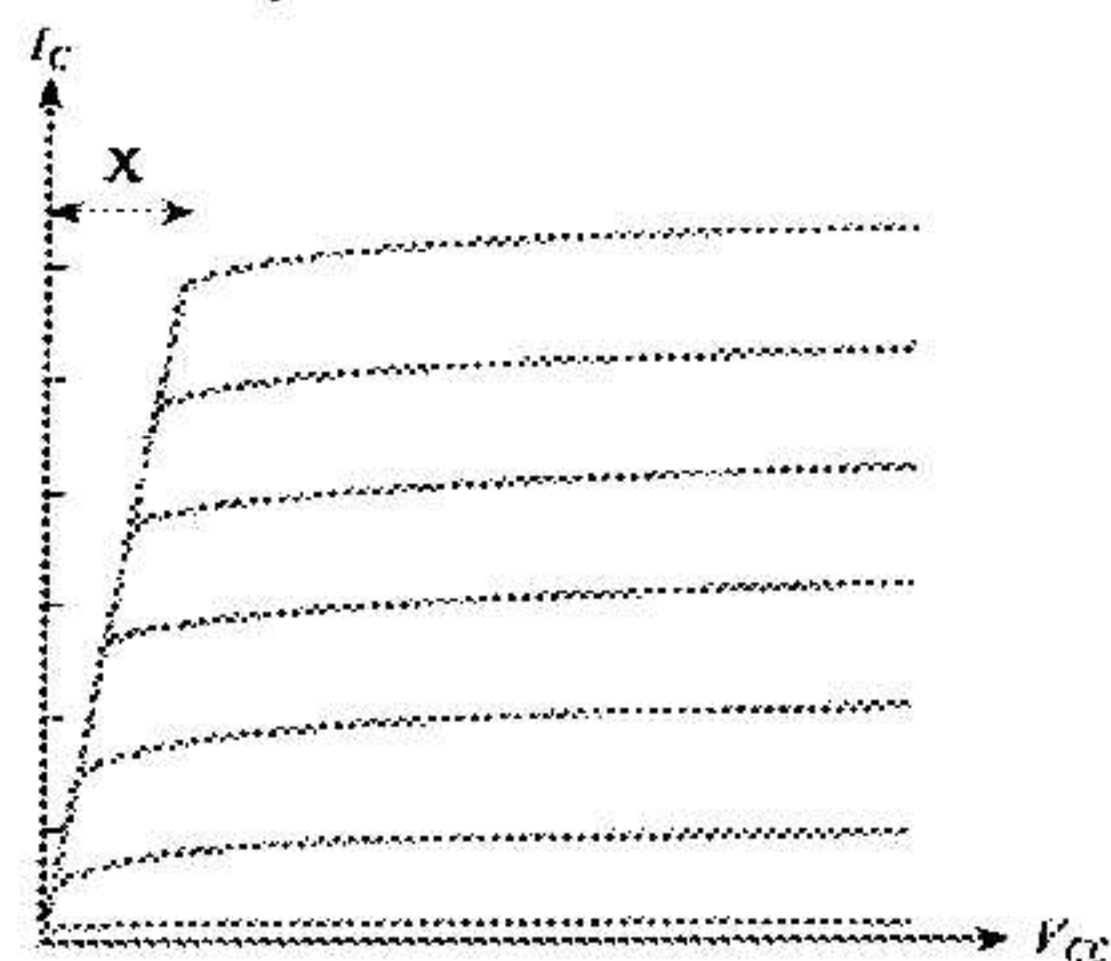

**Ans:**



## Rough Work

BITS, PILANI – INTERNATIONAL ACADEMIC CITY, DUBAI

FIRST SEMESTER 2009 – 2010

ES UC 241 ELECTRICAL SCIENCES – I

QUIZ 1 (CLOSED BOOK)

MAXIMUM MARKS: 24

DATE: 06.10.09

WEIGHTAGE: 8 %


DURATION: 25 MINUTES

NAME:

Id. No.:

1. Two resistors  $R_1$  and  $R_2$  are connected in series to a voltage source  $V_s$ . The voltage across the first resistor is \_\_\_\_\_ [2M]

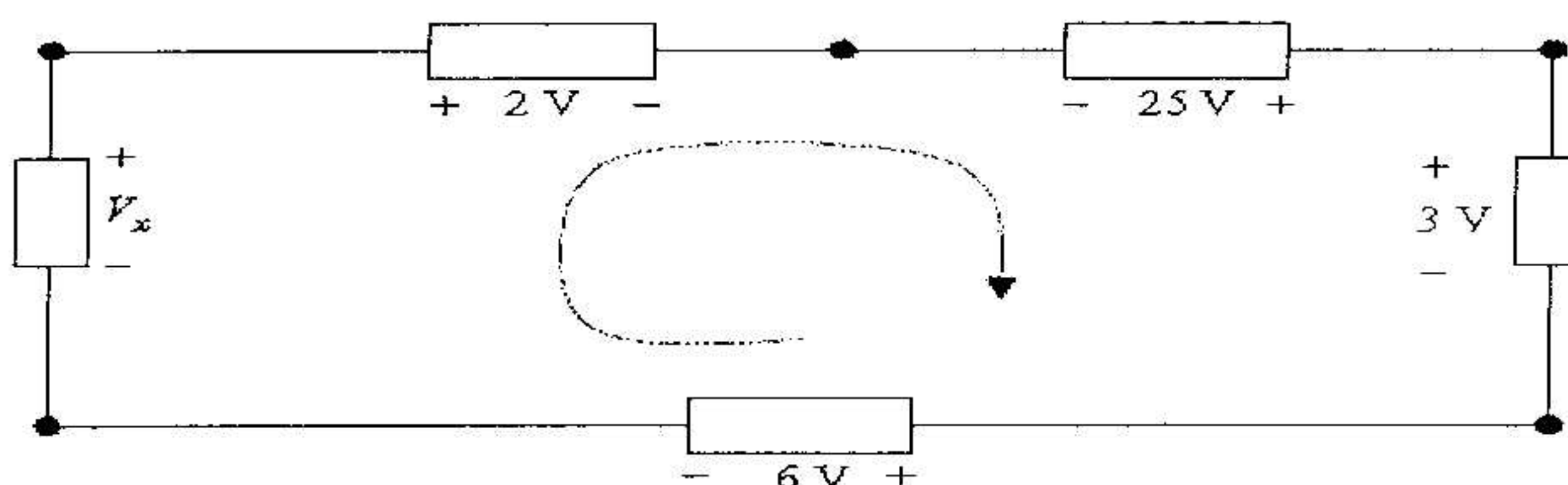2. Find the unknown voltage in the circuit shown below \_\_\_\_\_ V [2M]



3. Identify the incorrect statements with respect to the Thevenin theorem [1M]

- I. Remove the load to find open circuit voltage
- II. Short circuit the load to find the open circuit voltage
- III. Open circuit all voltage sources to find Thevenin's equivalent resistance  $R_0$
- IV. Short all the voltage sources to find Thevenin's equivalent resistance  $R_0$

- A. III, IV
- B. II, III
- C. I, II
- D. All are incorrect

4. If a resistor has 5.5 V across it and 3 mA flowing through it, what is the power \_\_\_\_\_ W [1M]



5. A certain series circuit has a  $100\Omega$ , a  $270\Omega$  and  $330\Omega$  resistors in series if the  $270\Omega$  resistor is short circuited from the circuit, the current \_\_\_\_\_ [1M]  
 (a) Increases (b) decreases (c) exactly doubles (d) becomes zero.

6. If one of the resistors in a parallel circuit is removed, what happens to the total resistance \_\_\_\_\_ [1M]


7. Six light bulbs are connected in parallel across  $110\text{V}$ , each bulb is rated  $75\text{W}$ , Find the current flowing through each bulb \_\_\_\_\_ [2M]

8. For the circuit shown below find out Norton equivalent resistance  $R_N$  \_\_\_\_\_ and the Current Source value \_\_\_\_\_ [2M]

9. In a series circuit, with unequal resistances [1M]  
 A) the lowest resistance has the highest voltage drop  
 B) the highest resistance has the highest voltage drop  
 C) the lowest resistance has the highest current through it  
 D) the highest resistance has the most of the current through it


10. A  $90\text{A}$  current flows into two parallel resistors having resistances of  $12\Omega$  and  $24\Omega$ . The current in the  $24\Omega$  resistor is \_\_\_\_\_ A [1M]

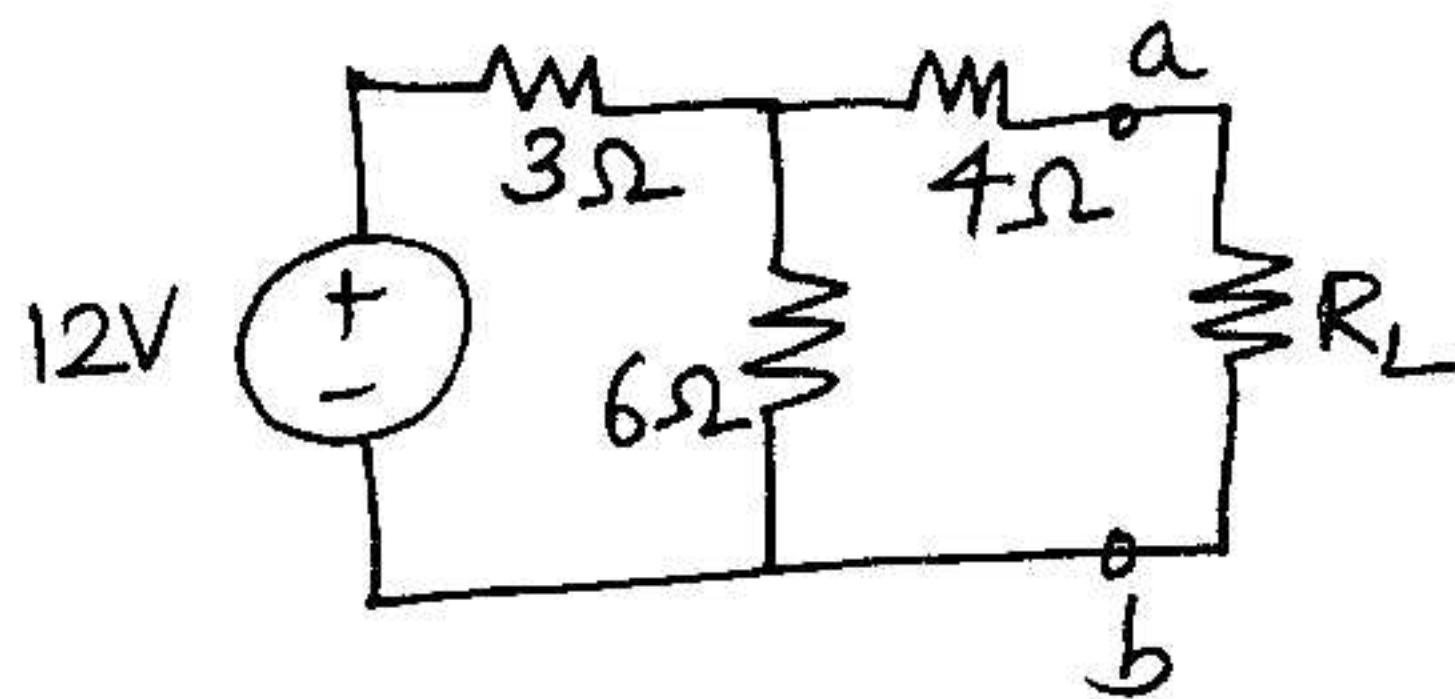11. Refer to the following figure, thevenin's equivalent resistance is \_\_\_\_\_. The value of  $R_L$  that absorbs maximum power is \_\_\_\_\_  $P_{\max} =$  \_\_\_\_\_ [2+1+1M]



12. An ideal voltage source is described by a function  $v(t) = 5 \sin(\omega/2)t$ . The value of this voltage source when  $t = 1$  sec is \_\_\_\_\_ V [1M]

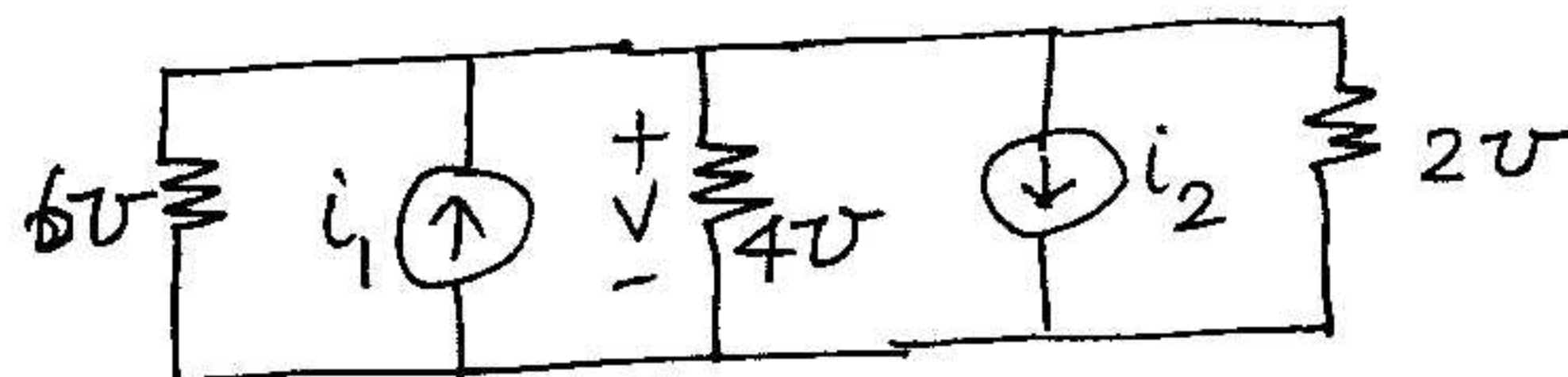13. For the circuit shown below suppose  $i_1$  is  $2\text{A}$ . The value of  $v$  when  $i_2$  is  $3\text{A}$  is \_\_\_\_\_ [2M]



14. For the circuit shown below the values for the current ( $I$ ) \_\_\_\_\_ A, Equivalent Resistance \_\_\_\_\_ and voltage \_\_\_\_\_ v [3M]

