

BITS PILANI DUBAI CAMPUS
DUBAI INTERNATIONAL ACADEMIC CITY, DUBAI
I SEMESTER 2013-2014
COMPREHENSIVE EXAMINATION

COURSE NO : **EEE/ECE/CS/INSTR F 215** DURATION : **3 HOURS**
 COURSE NAME : **Digital Design** **II Years**
 WEIGHTAGE : **40% (80 Marks)**
 Date : **08-01-2014 FN**

Calculators are not allowed.

Answer Part A, Part B and Part C in separate answer sheets.

PART – A

1. Convert (show a complete working of all the steps used during conversions)
 - a. (0.625) to binary. [2]
 - b. (231.3)₄ to base 7. [2]
2. A switching network has: 2 control inputs- C₁ and C₂; 2 data inputs- X₁ and X₂; and 1 output- Z. The network performs one of the logic operations: AND, OR, EQU (Equivalence), or XOR (exclusive-OR) on the two data inputs depending on control inputs as given below:


<u>C₁</u>	<u>C₂</u>	<u>Function performed by network</u>
0	0	AND
0	1	OR
1	0	EQU (Equivalence)
1	1	XOR (exclusive-OR)

 - a. Derive a truth table for Z. [3]
 - b. Use K-map method and find a minimum AND-OR gate network to realize Z;
 - i. Obtain the expression for Z in SOP form. [3]
 - ii. Also draw the logic diagram to realize Z. [3]
3. F(a,b,c,d,e)= $\sum m(0, 3, 4, 5, 6, 7, 8, 12, 13, 14, 16, 21, 23, 24, 29, 31)$
 - a. Find the essential prime implicants using a K-map and indicate why each one of the chosen prime implicants is essential. [4]
 - b. Find all the prime implicants by using the K-map. [5]
4. Realize: F(w,x,y,z)= xy'z + x'yz + w using
 - a. 3-input NAND gates only [5]
 - b. 3-input NOR gates only [5]
5. Design a network of AND & OR gates to convert from excess-3 code (use literals: a b c to 8-4-2-1 BCD Code (use literals: W X Y Z). [4]
6. Show how 16-to-1 and 2-to-1 multiplexers could be connected to form a 32-to-1 MUX with 5 control inputs. [4]

PART B

1. Answer the following questions with respect to the clocked SR latch [2+2+2+2M]
 - a) with the help of a diagram draw and explain the working of an SR latch constructed using Nand gates.
 - b) Give the characteristic table.
 - c) Give the characteristic equation.
 - d) Give the graphic symbol

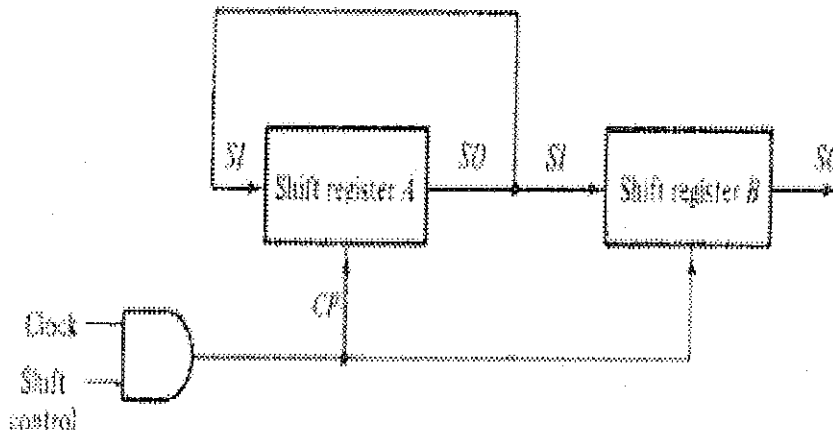2. For the given figure give the states of register A , register B and serial output of register B for four clock cycles. The initial state of register A is 1011 and the initial state of Register B is 0010 [4M]



3. Give answers in one word or in one sentence. [1 X 5 = 5M]
 - a) In a flip flop what does toggle mean ?
 - b) A ring counter with five flip flops has a total of _____ states.
 - c) A four bit synchronous counter use flip flops with a propagation delay of 15ns. The maximum possible time required for change of state is _____.
 - d) How many flip flops are required to construct a mod 30 counter.
 - e) Shifting a register content to the left by one position is equivalent to the _____ arithmetic operation.

4. [6+2M]
 - a. With the help of clocked JK flip flops and timing diagrams, explain the working of a three bit ripple up counter.
 - b. Give the truth table for clock transitions.

5. a. What is meant by a Synchronous counter? [1M]
 b. Design a Mod 5 synchronous counter using JK flip flops. [9M]

6. Explain how a shift register can be used as a ring counter giving the waveforms as the output of the flip flops. [5M]

PART – C

1. Explain the concept of paging with respect to virtual memory. [4 M]
2. Identify the behavior of the IO devices, i.e. specify whether they are input or output device
1. Keyboard 2. Mouse 3. Graphic display 4. Wireless LAN [4M]
3. Draw the logic diagram of the digital circuit specified by the following Verilog description. [6 M]

```
module Circuit(A,B,C,D,F);  
input A,B,C,D;  
output F;  
wire w,x,y,z,a,d;  
and (x,B,C,d);  
and(y,a,C);  
and(w,z,B);  
or (z,y,A);  
or(F,x,w);  
not(a,A);  
not(d,D);  
endmodule
```

4. Multiply 14 by – 5 using Booth's multiplication algorithm. [10 M]
5. Tabulate the PLA programming table for the four Boolean functions listed below, minimize the number of product terms and draw the PLA structure. [10M]
 $A(x, y, z) = \sum (1, 2, 4, 6)$
 $B(x, y, z) = \sum (0, 1, 6, 7)$
 $C(x, y, z) = \sum (2, 4, 5, 6, 7)$
 $D(x, y, z) = \sum (1, 2, 3, 5, 7)$
6. Tabulate the truth table for an 8 X 4 ROM that implements the Boolean functions listed below. [6 M]
 $A(x, y, z) = \sum (1, 2, 4, 6)$
 $B(x, y, z) = \sum (0, 1, 6, 7)$
 $C(x, y, z) = \sum (2, 4, 5, 6, 7)$
 $D(x, y, z) = \sum (1, 2, 3, 5, 7)$

Considering ROM as memory, specify the memory contents of 1 and 5.

BITS PILANI DUBAI CAMPUS

Dubai International Academic City, Dubai

Year II – Semester I 2013– 2014

TEST II (open book)

Course No.: EEE/ECE/CS/INSTR F 215

Course Title: Digital Design

Date: 10.12.13

Time: 50 Minutes

Max. Marks = 45

Weightage (10%)

1. Construct the state diagram for the shift register shown below with X as input and Z as output,

[8M]

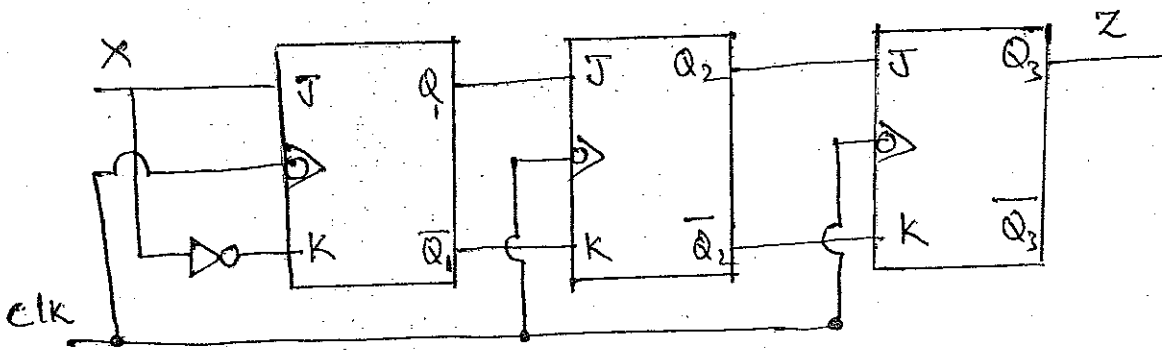


fig. 1

2. i) For the sequential circuit, shown below find the state equation for each flip flop. [6 M]

[6 M]

ii) Also construct state table

iii) What is the output sequence when input sequence is $x = 01100$


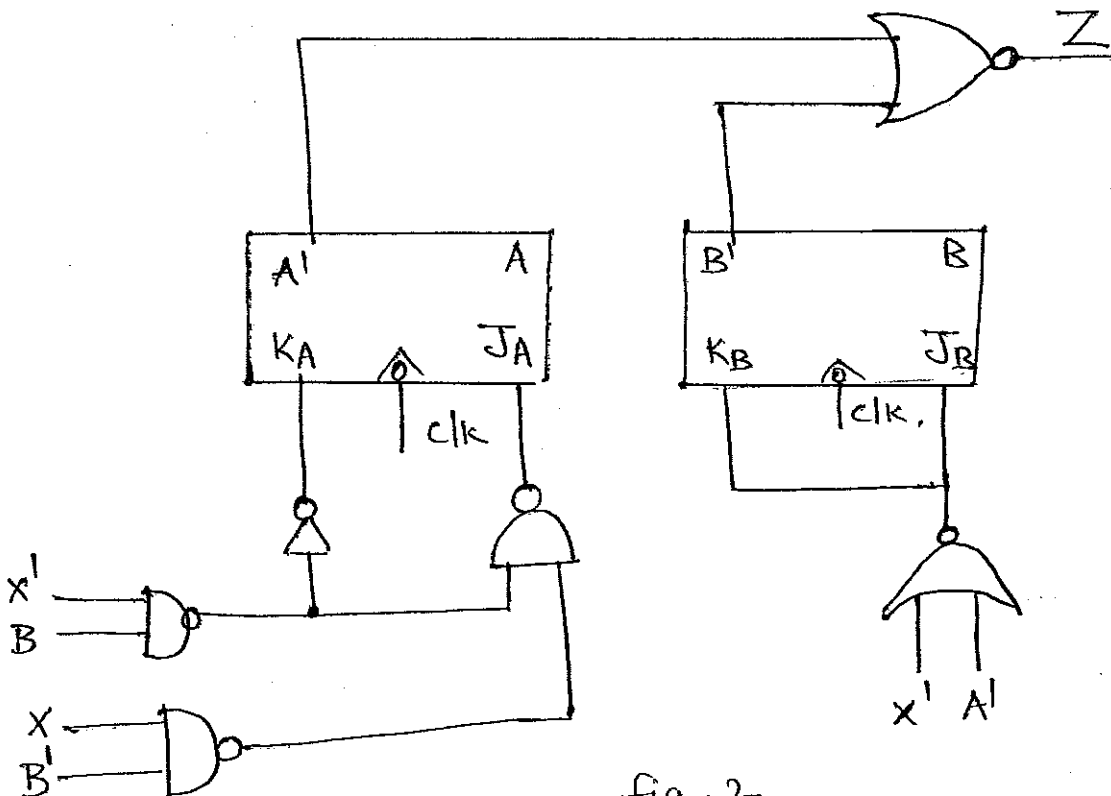



fig. 2

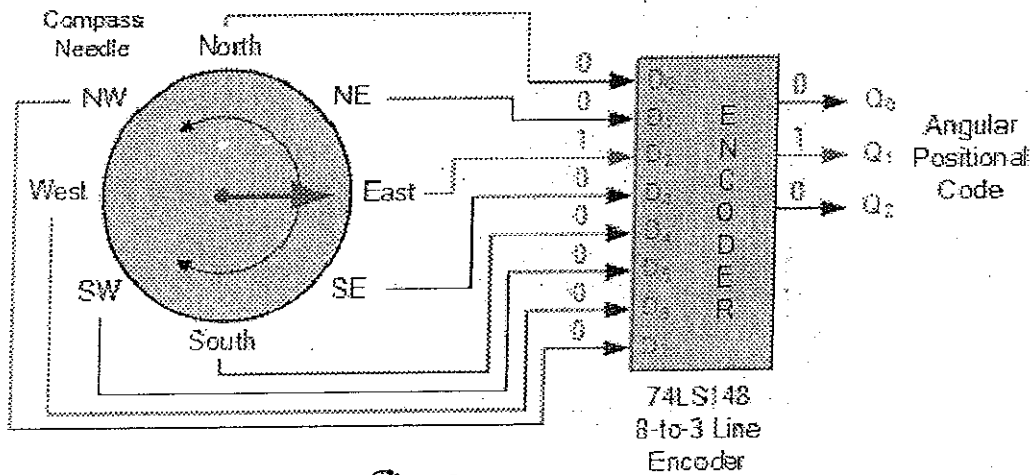3. A Priority Encoder is designed for navigation purpose, here for example, the angular or rotary position of a compass is converted into a digital code by a 74LS148 8-to-3 line priority encoder and inputted to the systems computer to provide navigational data and an example of a simple 8 position to 3-bit output compass encoder is shown in fig 3.

- Draw the truth table
- Give the Boolean expression for the three outputs Q_0, Q_1, Q_2
- Finally draw how this digital encoder can be constructed using logic gates. Assume D_7 has the highest priority and D_0 has the lowest priority. [4 +2+2M]



 4. The given block diagram is of a decimal to BCD encoder. Give the status of the input and the output lines required to generate the number 7. [2M]



Design only the sum function of the full adder using only 2 X 1 MUX. [5 M]

BITS PILANI DUBAI CAMPUS

Dubai International Academic City, Dubai

Year II – Semester I 2013– 2014

TEST I

Course No.: EEE/ECE/CS/INSTR F 215

Course Title: Digital Design

Date: 08.10.13

Time: 50 Minutes

Max. Marks = 45

Weightage (15%)

1. Find all prime implicants for the Boolean function given below and determine which are essential. **(5 Marks)**

$$F(A,B, C, D) = \sum (0,2,3,5,7,8,10,11,14,15)$$

2. Simplify the following Boolean function F together with don't care conditions and then express it in the simplified sum of minterms form **(5 Marks)**

$$F(A, B, C, D) = \sum (4, 5, 6, 7, 12, 13, 14)$$

$$d(A, B, C, D) = \sum (1,9,11,15)$$


3. Draw the logic diagram that implements the **complement** of the following function. **(5 Marks)**

$$F(A,B, C, D) = \sum (0,1,2,3,4,8,9,10,11,12)$$

4. Find the minimum number of gates required to implement the function given below **(2 Marks)**

$$A + AB^1 + AB^1C$$

 5. Draw the truth table for the following logic diagram. **(3 Marks)**



ID NO: -----

Instructor Name:-----

NAME: -----

BITS PILANI DUBAI CAMPUS

Dubai International Academic City, Dubai

Year II – Semester I 2013– 2014

QUIZ II

SET B

Course No.: EEE/ECE/CS/INSTR F 215

Course Title: Digital Design

Date: 13.11.13

Time: 20 Minutes

Max. Marks = 15 Weightage (5%)

1. A 4-bit magnitude comparator has _____ no. of inputs and _____ no. of outputs. [1 M]
2. Complete the missing entries in the Full Subtractor truth table given below. [2 M]


X	Y	Z	D	B
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1		

3. In a typical binary multiplier implementation using AND gates, state how new partial product gets formed? [2 M]

4. In a 4-bit magnitude comparator, "equality" Function can be implemented by just employing _____ logic [1 M]
5. Draw the logic circuit for the function $A (B^1 + C)$ using NOR gates only. Inputs are available in both true and false (high and low) states. [2.5 M]
6. Draw the diagram of a digital circuit for the function $F(X,Y,Z) = Y^1 Z + X Z^1$ using only NAND gates, assume that the inputs are available only in the true (high) state. [2.5 M]

7. _____ No. of AND gates and _____ no. of 4-bit adders would be required to produce a product of seven bits. Assume 2 binary nos.: $B_3B_2B_1B_0$ and $A_2A_1A_0$ are to be multiplied. [1 M]

 8. What should be the value of X, so that we get X_0, X_1, X_2 to be one's complement of A_0, A_1, A_2 [1 M]



X =

9. Write the output of the following circuit. [2 M]

