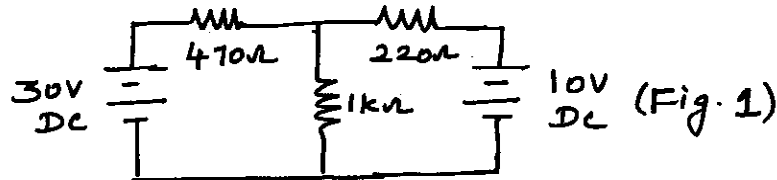



- Answer All the Questions

- 1 Consider the circuit in Fig.1. Find the current through the $1k\Omega$ resistor using superposition theorem.




[10 marks]

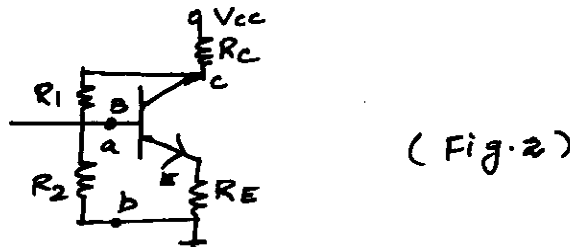- 2(a) A common emitter configuration of a BJT (Bipolar Junction Transistor) with potential divider biasing is given in Fig.2. Draw the Thevenin equivalent of the base circuit and obtain an expressions for Thevenin voltage and Thevenin resistance.



[5 marks]

- 2(b) For the circuit shown in Fig.2, β (Beta) = 70, $V_{CC} = 10V$, $R_c = 2k\Omega$, $V_E = 1.5V$. Fix Q point at the centre of load line $V_{CEQ} = 5V$. Find I_{CQ} and R_E . [5 marks]
- 3(a) List out the characteristics of an ideal operational amplifier. [5 marks]
- 3(b) Draw the transfer characteristics of operational amplifier and explain briefly three regions of operations. [5 marks]
- 4(a) Find the expression for V_o for the circuit shown in Fig.3. consider the op amp as ideal.

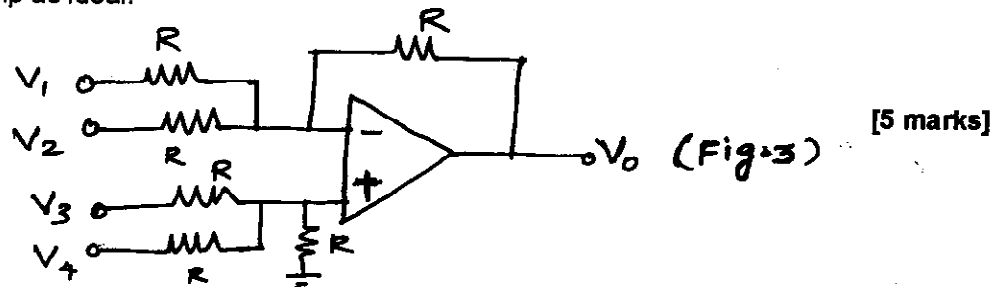

[5 marks]

- 4(b) Draw an inverting operational amplifier to form the weighted sum V_o of two inputs V_1 and V_2 . It is required that $V_o = -(V_1 + 5V_2)$. Choose values for R_1 , R_2 and R_f (feedback resistor) so that for a maximum output voltage of 10V, the current in the feedback resistor will not exceed 1mA. Design the values for R_1 , R_2 and R_f . [5 marks]

-----END-----

**BITS, PILANI-DUBAI
INTERNATIONAL ACADEMIC CITY, DUBAI**

TEST-2(OPEN BOOK)
COURSE NO: EEE C364
DURATION: 50 MINUTES


WEIGHTAGE:15%
DATE: 02.11.08

MAX. MARKS:30
COURSE TITLE: ANALOG ELECTRONICS
INSTRUCTOR: Dr.V.KALAICHELVI


Text books (TB1 and TB2) and hand written class notes are allowed
Photo copy of materials are **not allowed** in the Examination Hall
Semi log sheet is provided along with the question paper.

Answer all questions

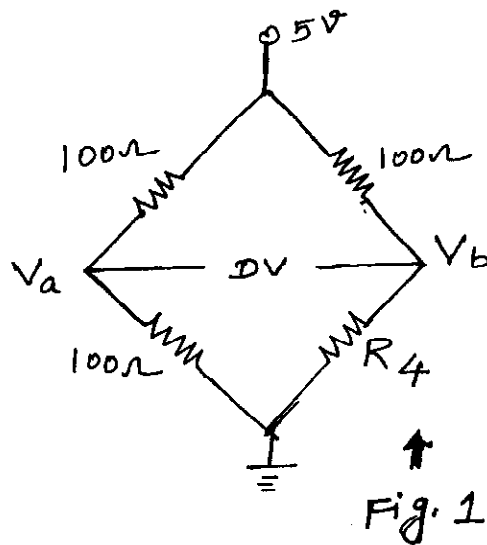1. Fig.1 shows a bridge circuit for which R_4 varies with 100Ω to 102Ω . Show that how an instrumentation amplifier like that in Fig.2 could be used to provide an output of $2.5V$. Assume that $R_2=R_3=1k\Omega$ and that $R_1=100k\Omega$. Draw the circuit diagram that contains bridge circuit and an instrumentation amplifier and find the value of R_G .



DV - Differential Voltage

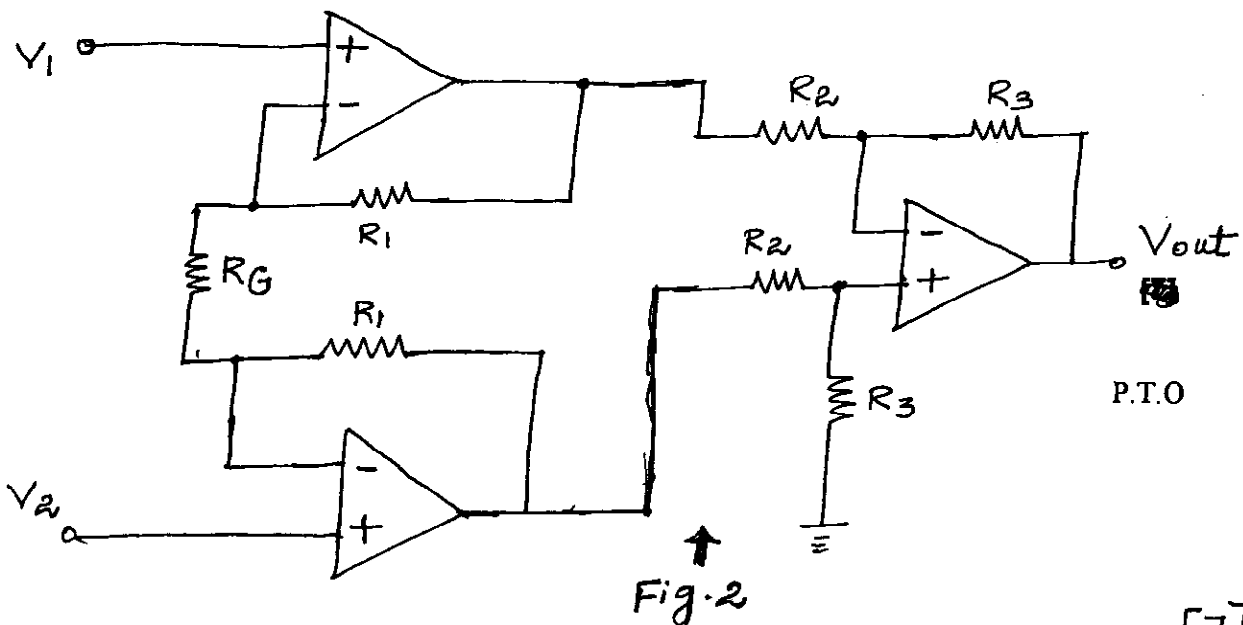

P.T.O

2. Derive the transfer function for the network of Fig.3 using op amp and find the order of the filter. Plot $|G(j\omega)|$ versus frequency in Hertz, on a semi log scale and identify the type of filter from the frequency response.

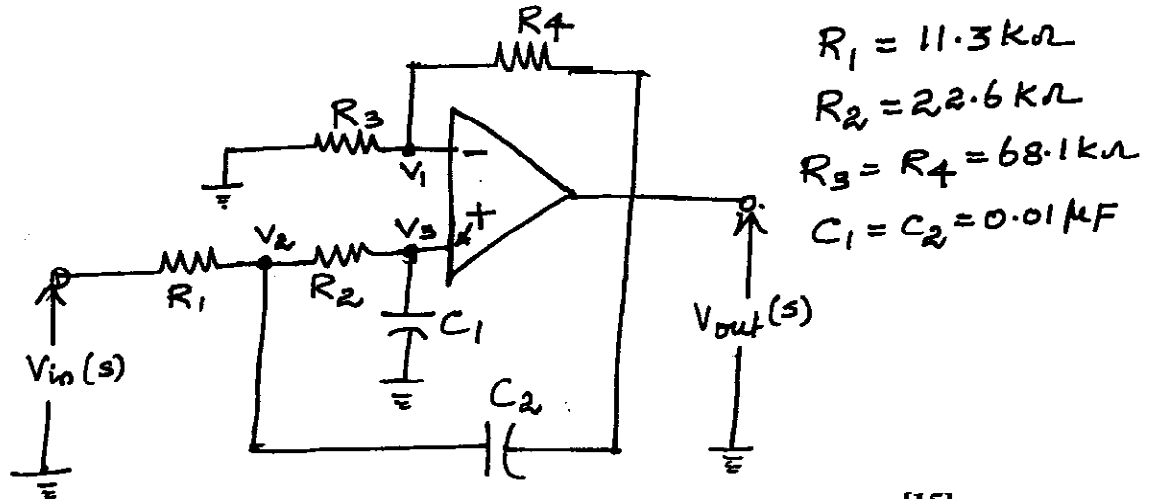


Fig. 3

[15]

3. Use $C_1=C_2=20\text{PF}$ and design the circuit in Fig.4 to realize a band pass function with $f_0=10\text{KHZ}$, $Q=20$ and unity center-frequency gain. Use a clock frequency $f_c = 400 \text{ kHz}$. Find the values of C_3 , C_4 , C_5 and C_6 .


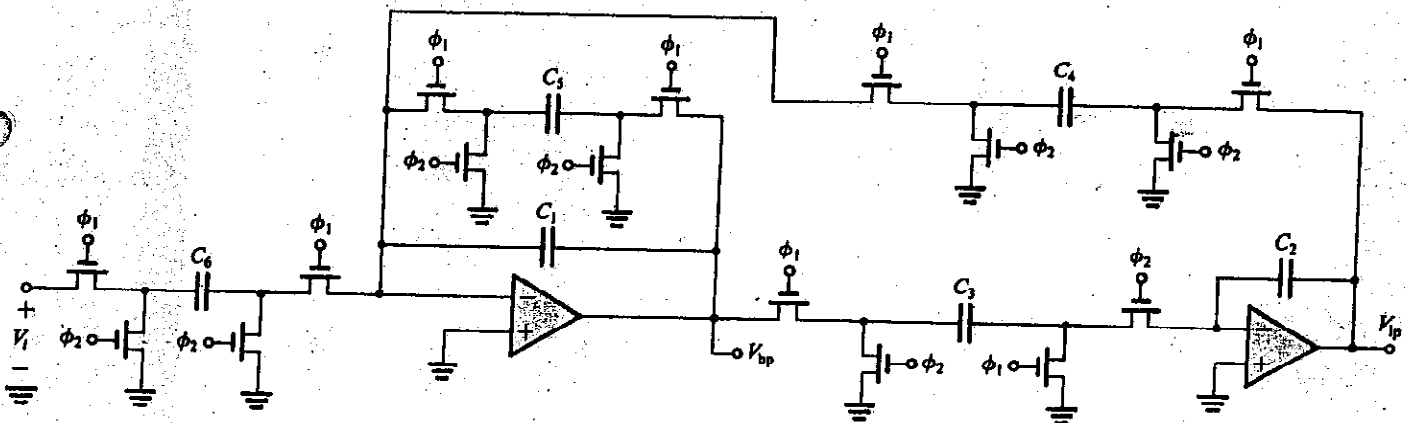


Fig. 4

[8]

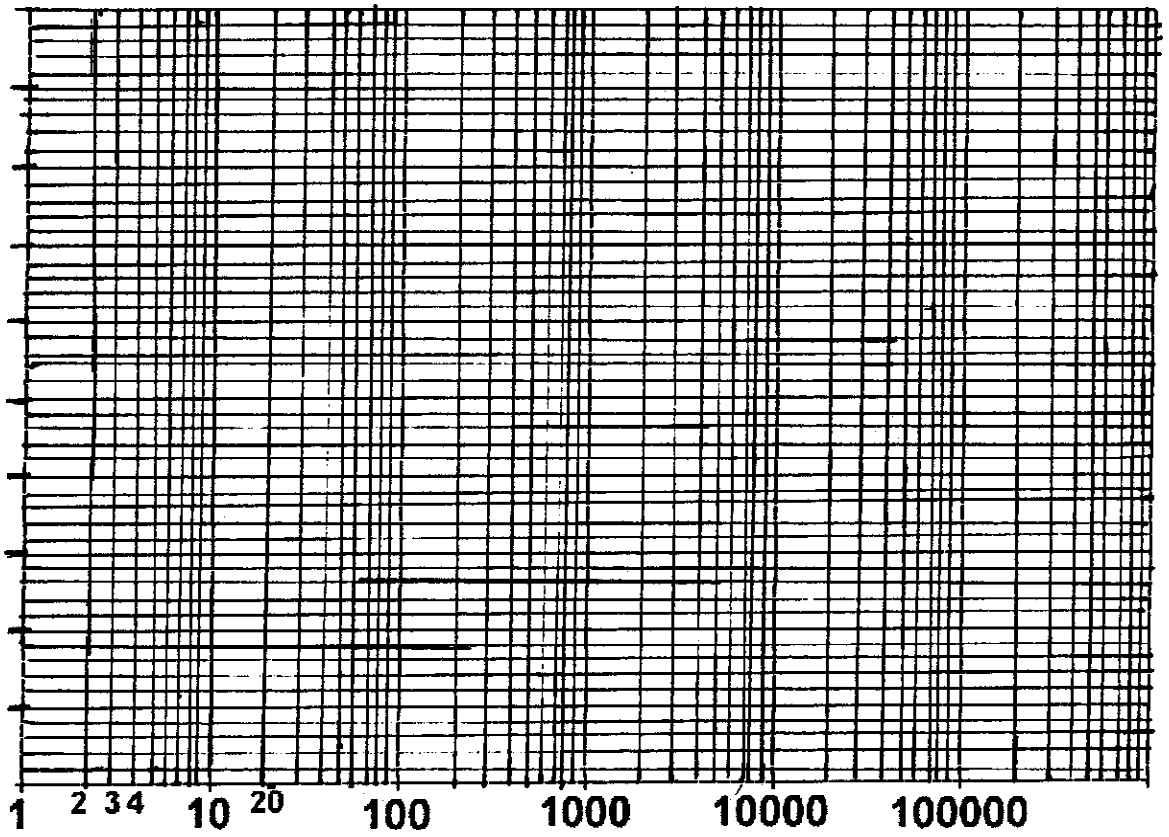


FIRST SEMESTER 2008-2009 QUIZ 1 (CLOSED BOOK)

COURSE NO : EEE C364 DATE:
COURSE NAME: ANALOG ELECTRONICS

MAXIMUM MARKS: 10 (5% wt.)
DURATION: 15 MINUTES

• **Answer All the Questions**

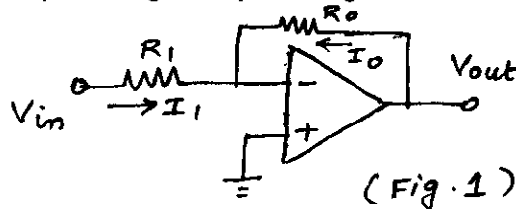- 1 Consider the circuit in Fig.1. What is the expression for the ratio of the output voltage to input voltage?



[1]

- 2 For the circuit shown in Fig.1 gain is -10. If $R_1=5\text{k}\Omega$, what is the value of R_0 ? Give your answer in ohms.

[1]


- 3 An ideal operational amplifier has -----slew rate and -----bandwidth.

[1]

- 4 Draw an inverting amplifier with input resistance of $10\text{k}\Omega$, determine the value of feedback resistance that will produce an amplifier with a gain of 3.3.

[1]

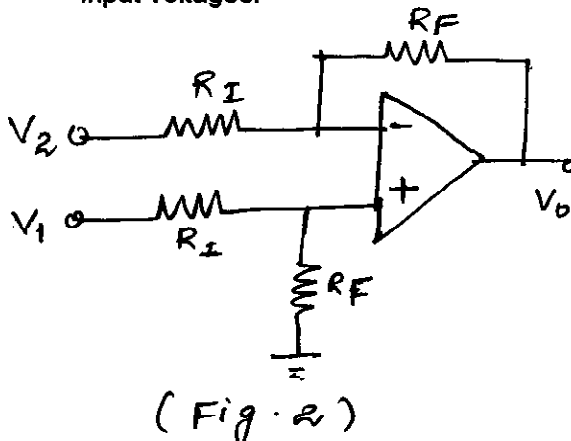- 5 Consider the circuit in Fig.2 An operational amplifier has a gain of 250,000. The output voltage is 3.75V. Calculate the difference of the input voltages.



[1]


6 What kind of an amplifier is an operational amplifier?

[1]

7 What are the typical power supply voltages of a typical 741 op amp?

[1]

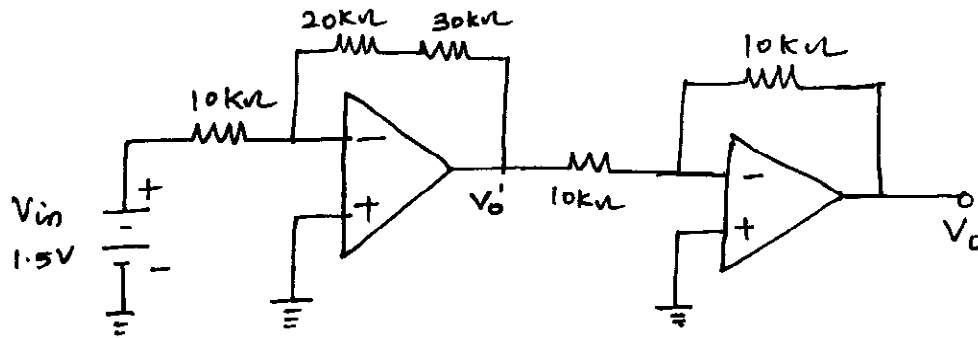8 For the circuit shown below, if $V_{in}=1.5V$, what is V_o in volts?



[1]

9 What is the difference between continuous time signal and discrete time signal?

[1]

10 Draw the output characteristics of a bipolar device.

[1]

END

BITS, PILANI-DUBAI

QUIZ-II(CLOSED BOOK)
 COURSE TITLE: ANALOG ELECTRONICS
 COURSE NO: EEE C364

WEIGHTAGE:5%
 DURATION: 15 MINUTES
 MAX MARKS:10

NAME OF THE STUDENT: _____

ID NO: _____

Answer all questions

1. The following circuit (Fig.1) is a type of difference amplifier, similar in behaviour to the instrumentation amplifier, but only using two operational amplifiers

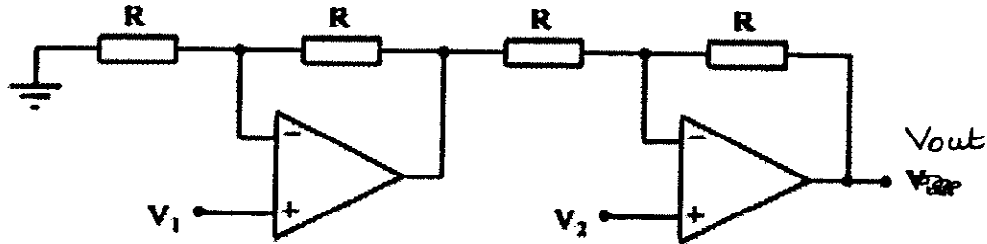


Fig.1


instead of three. Complete the table of values for this op-amp circuit, calculating the output voltage for each combination of input voltages shown.

V_1	V_2	V_{out}
+1 V	0 V	
0 V	+1 V	
+2 V	+1.5 V	
+3.4 V	+1.2 V	
+5 V	+5 V	
-3 V	-3 V	

From the calculated values of output voltage, determine which input of this circuit is inverting, and which is non-inverting, and also how much differential voltage gain this circuit has and express these conclusions in the form of an equation.

[5]

2. The non-inverting op amp configuration is shown in Fig.2

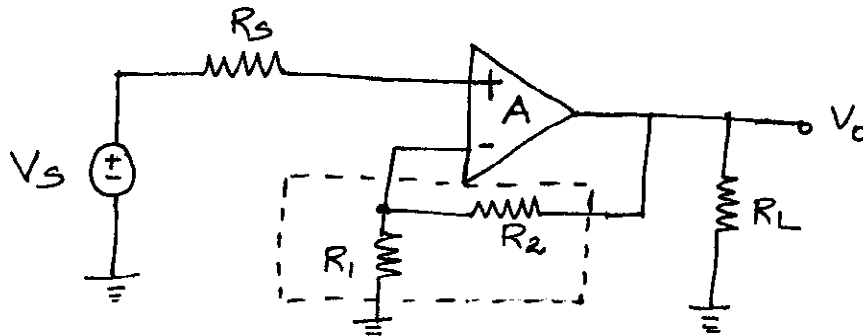

(Fig.2)

- (i) Assume that the op amp has infinite input resistance and zero output resistance. Find an expression for the feedback factor (β)
- (ii) If the open loop voltage gain $A=100$ find R_2/R_1 to obtain a closed loop voltage gain A_f of 10.
- (iii) What is the amount of feedback in decibels?
- (iv) If $V_s=1\text{V}$, find V_o, V_f and V_i
- (v) If A decreases by 20%, what is the corresponding decrease in A_f ?




[5]

Quiz-3

BITS PILANI - DUBAI
INTERNATIONAL ACADEMIC CITY, DUBAI
COURSE NO:EEE C364 COURSE TITLE :ANALOG ELECTRONICS (SET A)
QUIZ-III(CLOSED BOOK) MAX MARKS:10 WEIGHTAGE:5%
INSTRUCTOR:Dr. V.KALAICHELVI DURATION:15 MINUTES
ID NUMBER: NAME OF THE STUDENT:
DATE :

ANSWER ALL QUESTIONS

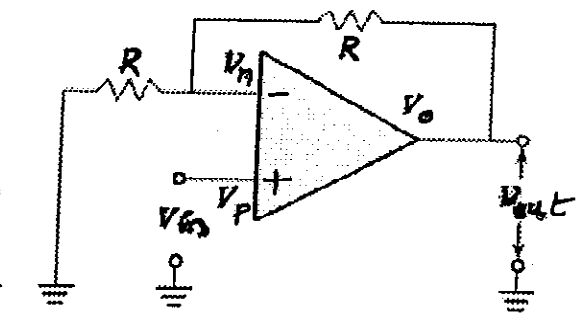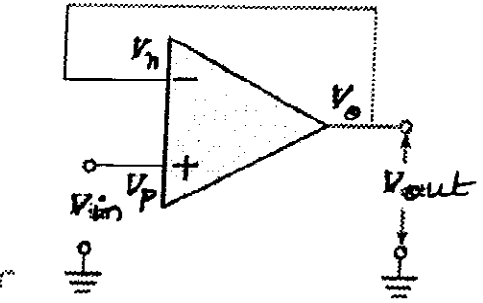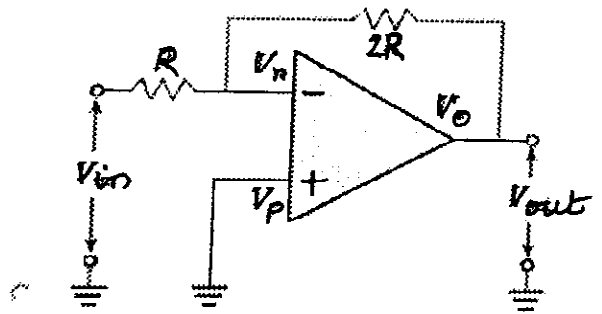
1.. Choose the circuit below that would take a DC input voltage $V_{in} = 1$ V and produce an output voltage $V_{out} = 2$ V.



2. Which choice below best defines the purpose of a buffer (constructed with an op-amp)?

- To invert the input signal.
- To amplify the input signal.
- To invert *and* amplify the input signal.
- To isolate the input signal from the rest of the circuit.
- To effectively increase the input impedance of the op-amp.

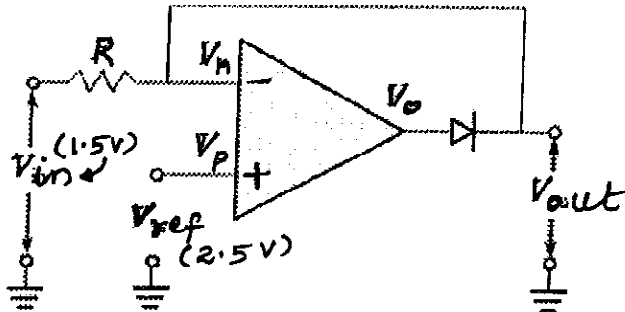3. Consider the following schematic diagram:




If $V_{in} = 1.5\text{ V}$, and $V_{ref} = 2.5\text{ V}$, what is V_{out} (in volts)?

4. In which of the following scenarios can an op-amp running in an open-loop configuration be used to amplify the signal?


- A voltage with a mean of 1.0 V , and with superimposed noise with peak-to-peak amplitude of less than one microvolt.
- A distant radio signal with zero mean, and less than a microvolt peak-to-peak amplitude.
- A voltage with zero mean, and a peak-to-peak amplitude of around 0.2 V .
- A voltage with a mean of -1.0 V , and with superimposed noise with peak-to-peak amplitude of a few millivolts.
- All of the above.

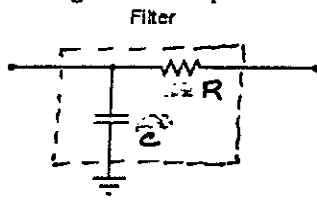5. Identify what type of filter this circuit is, calculate its cut off frequency, and distinguish the input terminal from the output terminal:




$[R = 15k\Omega \quad C = 22\mu f]$


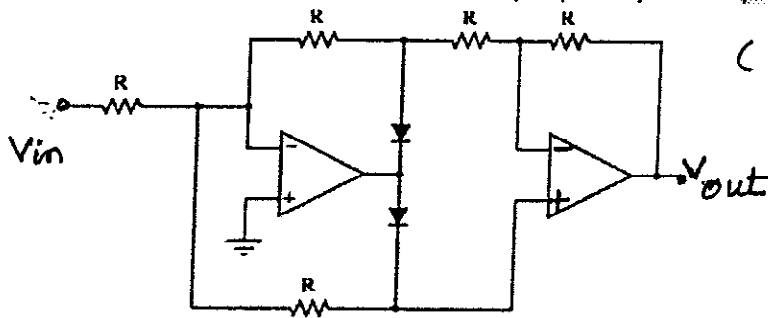
6. Explain how you could reverse the output polarity of this precision rectifier circuit:



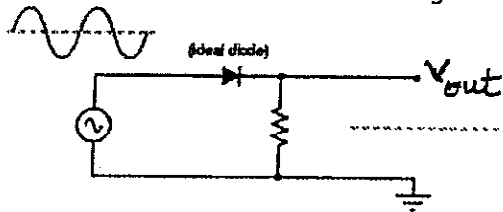7. Sketch the shape of the output voltage waveform for this "clipper" circuit, assuming an ideal diode with no forward voltage drop:




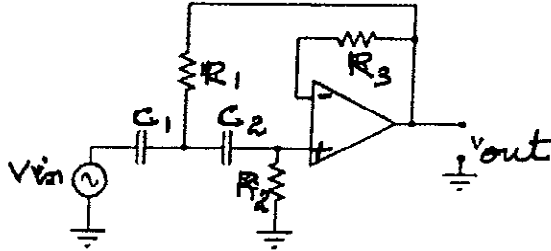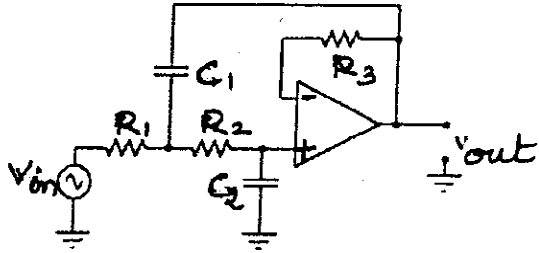8. A very popular active filter topology is called the Sallen-Key. Two examples of Sallen-Key active filter circuits are shown here:



Determine which of these Sallen-Key filters ^{is} low pass _^ and which is high pass. Explain your answers

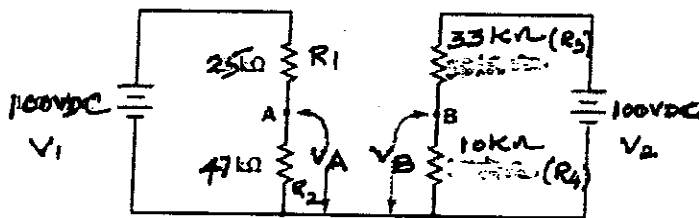
9. Calculate the output voltages of these two voltage divider circuits (V_A and V_B):



- $R_1 = 25\text{ k}\Omega$
- $R_2 = 47\text{ k}\Omega$
- $R_3 = 33\text{ k}\Omega$
- $R_4 = 10\text{ k}\Omega$
- $V_1 = V_2 = 100\text{ VDC}$

Now, calculate the voltage between points A (red lead) and B (black lead) (V_{AB}).

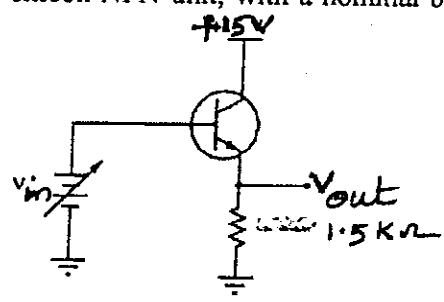10. Complete the table of output voltages for several given values of input voltage in this common-collector amplifier circuit. Assume that the transistor is a standard silicon NPN unit, with a nominal base-emitter junction forward voltage of 0.7 volts:



V_{in}	V_{out}
0.0 V	
0.5 V	
1.0 V	
1.5 V	
5.0 V	

BITS PILANI- DUBAI
INTERNATIONAL ACADEMIC CITY, DUBAI


COURSE NO:EEE C364 COURSE TITLE :ANALOG ELECTRONICS (SET B)
 QUIZ-III(CLOSED BOOK) MAX MARKS:10 WEIGHTAGE:5%
 INSTRUCTOR:Dr.V.KALAICHELVI DURATION:15 MINUTES
 ID NUMBER: NAME OF THE STUDENT:
DATE :

ANSWER ALL QUESTIONS

1. In which of the following scenarios can an op-amp running in an open-loop configuration be used to amplify the signal?


- A voltage with a mean of 1.0 V, and with superimposed noise with peak-to-peak amplitude of less than one microvolt.
- A distant radio signal with zero mean, and less than a microvolt peak-to-peak amplitude.
- A voltage with zero mean, and a peak-to-peak amplitude of around 0.2 V.
- A voltage with a mean of -1.0 V, and with superimposed noise with peak-to-peak amplitude of a few mill volts.
- All of the above.

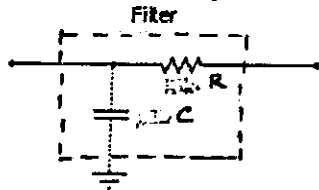2. Identify what type of filter this circuit is, calculate its cut off frequency, and distinguish the input terminal from the output terminal:



$[R = 15k\Omega \text{ \& } C = 22\mu F]$



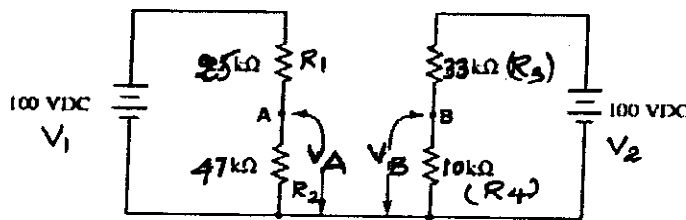
3. Calculate the output voltages of these two voltage divider circuits (V_A and V_B):




$R_1 = 25k\Omega$
 $R_2 = 47k\Omega$
 $R_3 = 33k\Omega$
 $R_4 = 10k\Omega$
 $V_1 = V_2 = 100V DC$

Now, calculate the voltage between points A (red lead) and B (black lead) (V_{AB}).

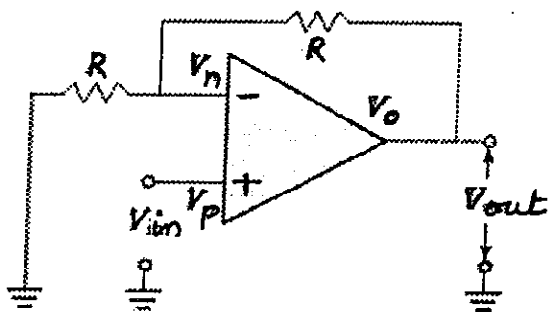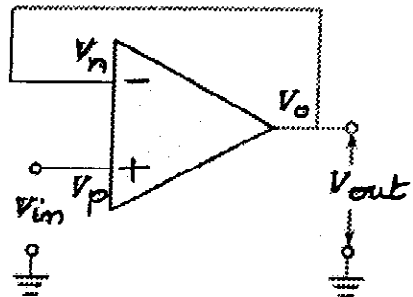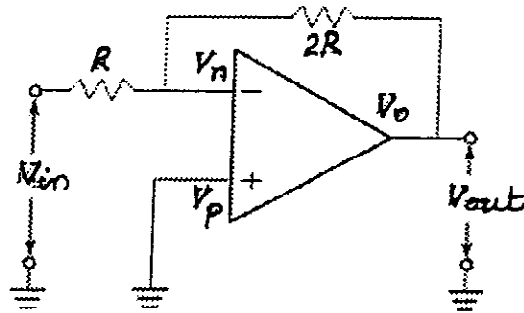4. Choose the circuit below that would take a DC input voltage $V_{in} = 1\text{ V}$ and produce an output voltage $V_{out} = 2\text{ V}$.




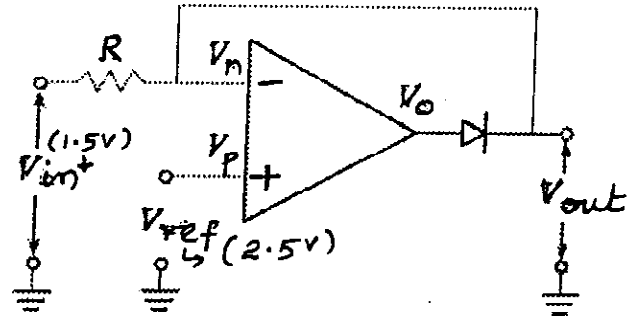5. Consider the following schematic diagram:



If $V_{in} = 1.5V$, and $V_{ref} = 2.5V$, what is V_{out} (in volts)?

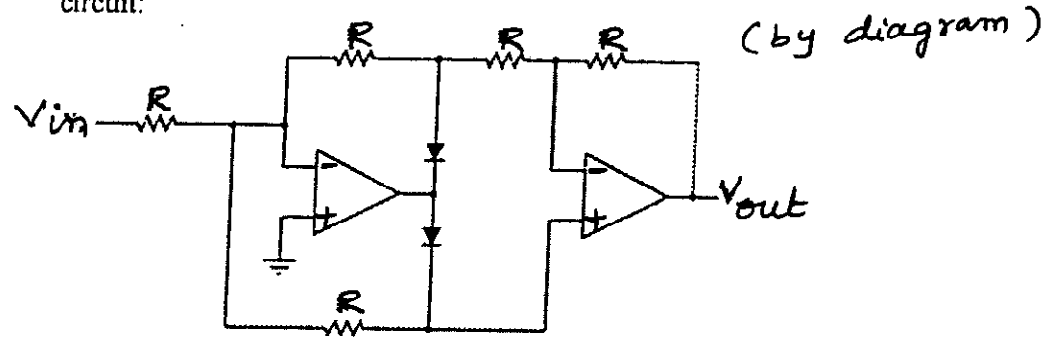
6. Explain how you could reverse the output polarity of this precision rectifier circuit:




7. Which choice below best defines the purpose of a buffer (constructed with an op-amp)?

- To invert the input signal.
- To amplify the input signal.
- To invert and amplify the input signal.
- To isolate the input signal from the rest of the circuit.
- To effectively increase the input impedance of the op-amp.

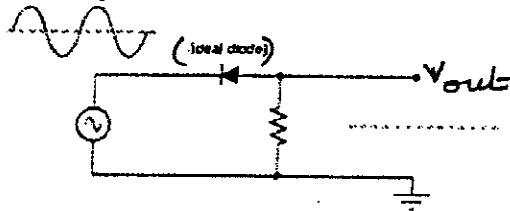8. Sketch the shape of the output voltage waveform for this "clipper" circuit, assuming an ideal diode with no forward voltage drop:





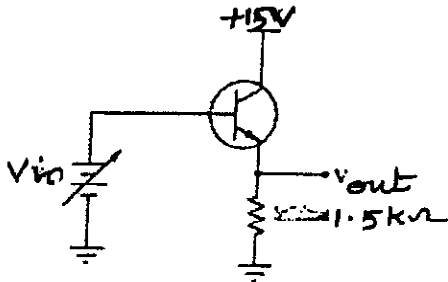9. Complete the table of output voltages for several given values of input voltage in this common-collector amplifier circuit. Assume that the transistor is a standard silicon NPN unit, with a nominal base-emitter junction forward voltage of 0.7 volts:



V_{in}	V_{out}
0.0 V	
0.5 V	
1.0 V	
1.5 V	
5.0 V	

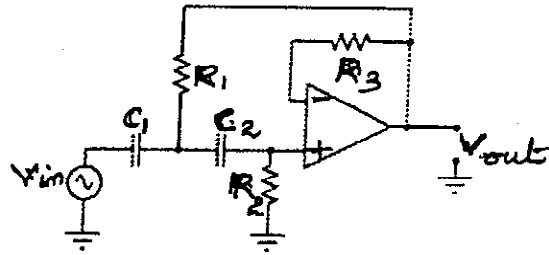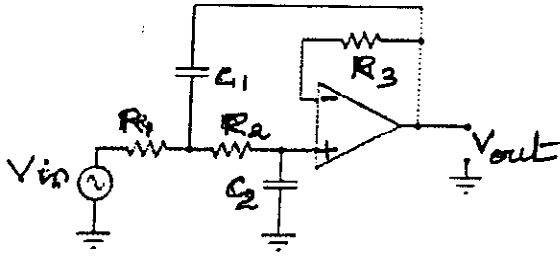10. A very popular active filter topology is called the Sallen-Key. Two examples of Sallen-Key active filter circuits are shown here:



Determine which of these Sallen-Key filters is low pass and which is high pass. Explain your answers

xxxxxx. END xxxxxxxx.

BITS PILANI-DUBAI
DUBAI INTERNATIONAL ACADEMIC CITY, DUBAI
FIRST SEMESTER 2008-2009

CLASS: III YEAR EEE

COMPONENT: COMPREHENSIVE EXAM (CLOSED BOOK)

DATE: 23-12-08

COURSE NO: EEE C364

COURSE TITLE: ANALOG ELECTRONICS

DURATION: 3 Hours

MAX MARKS: 50

WEIGHTAGE: 25% INSTRUCTOR: Dr.KLS

- **Answer All Questions**
- **Any required data not explicitly given, may be suitably assumed and stated.**

- 1(a) Convert the following Thévenin equivalent circuit (Fig.1) into Norton Equivalent circuit: [2Marks]


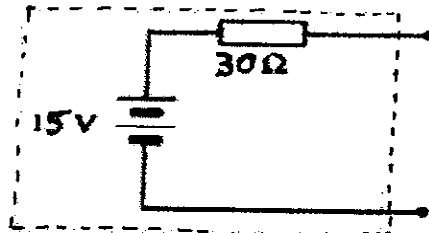


Fig.1

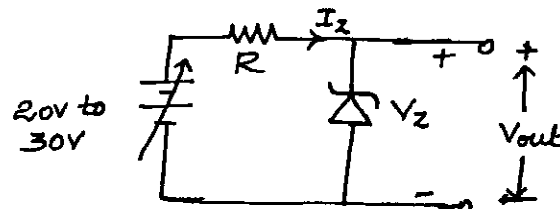- (b) A weighted summer circuit using an ideal op amp has three inputs using $100\text{k}\Omega$ resistors and a feedback resistor of $50\text{k}\Omega$. A signal v_1 is connected to two of the inputs while a signal v_2 is connected to the third. Express v_o in terms of v_1 and v_2 . If $v_1 = 3\text{V}$ and $v_2 = -3\text{V}$, what is v_o ? [5Marks]
- (c) A signal of magnitude 1 to 5V is obtained from a sensor. It is required to transmit the signal to the control room. Design a suitable circuit using operational amplifier to convert the signal into a current signal of range 4 to 20mA. [3Marks]
- 2(a) List the topologies used for realizing active filters. [2Marks]
- (b) Draw the circuit of Schmitt trigger and derive an expression for Hysteresis voltage. Also sketch its input and output waveforms. [5Marks]
- (c) The input to the Zener diode regulator shown in Fig.2 varies from 20V to 30V. Use the ideal characteristic of Zener diode to work out the maximum and minimum Zener current. [3Marks]



$R = 820\Omega$
 $V_Z = 10\text{V}$

Fig.2

P.T.O

3(a) Explain briefly what the **Barkhausen criterion** is for an oscillator circuit. How will the oscillator circuit's performance be affected if the Barkhausen criterion falls below 1, or goes much above 1? [4Marks]

(b) Find the frequency of oscillation of the circuit in Fig.3 for the case $R_1=10k\Omega$, $R_2=16k\Omega$, $C=10nF$ and $R=62k\Omega$.

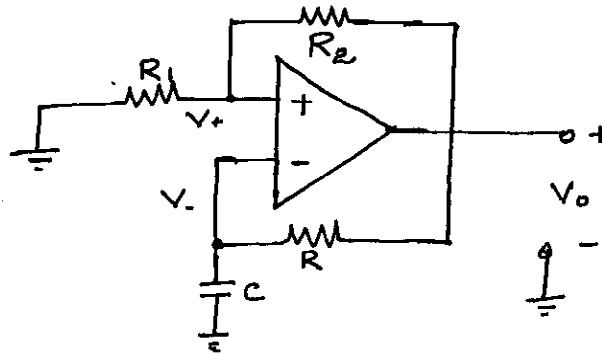


Fig.3

[4Marks]

(c) Sketch the transfer characteristics of the circuit in Fig.4

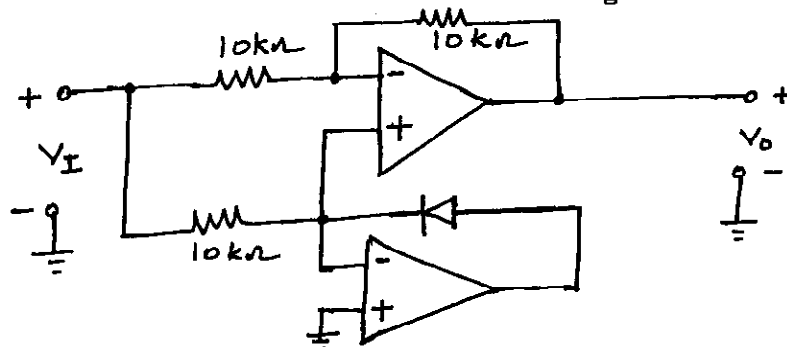


Fig.4

[2Marks]

4(a) Draw the circuit of Class A output stage of an amplifier and derive an expression for Power conversion efficiency. Also sketch its transfer characteristics. [6Marks]

(b) An inductance of $30\mu H$ is resonated with a $1000pF$ capacitor. If the inductor is tapped at one-third of its turns and a $1k\Omega$ resistor is connected across the one-third part, find f_0 and Q of the resonator. [4Marks]

5(a) Design a D/A converter using resistive divider network for the following specifications:

Input - 3 bit digital inputs

Output - 0 to 5V analog output

(b) Define sensor and a transducer. [5Marks]

(c) What are MEMS? Mention some applications of MEMS. [2Marks]

[3Marks]

END