

**BITS-Pilani Dubai,  
Dubai International Academic City, Dubai  
I Semester, Academic Year 2008-09**

Evaluation Component : TEST-I (Closed Book)

**EEE C424 / INSTR U313 MICROELECTRONIC CIRCUITS**

**Date : 5<sup>th</sup> Oct. 2008**

**Duration: 50 mts**

**Max. Marks: 25  
Weightage: 25%**

Note:- 1. ANSWER ALL QUESTIONS

2. Make assumptions, if any, but explicitly indicate the assumptions made

1)

a) Define the following terms with reference to a General Purpose Amplifier:

(i) Voltage Gain

(ii) Bandwidth

(iii) Amplifier saturation

(iv) Maximum signal handling capacity

(v) Efficiency

(5.0 M)

b) List any four important considerations in choosing the BIAS POINT while designing of a BJT Amplifier

(2.0 M)

2)

a) Draw the h-parameter model of a BJT and define all the four parameters. Also indicate how they can be obtained from the characteristics of the active device.

(3.0 M)

b) List the five important steps in performing ac analysis of a BJT Amplifier

(3.0 M)

3) A BJT Common Emitter Amplifier with  $R_C=10\text{ k}\Omega$  is connected between a source with  $R_s=5\text{ k}\Omega$ , and a load of  $R_L=5\text{ k}\Omega$ . Assuming that the parameters of the BJT model are:  $r_{\pi}=2.5\text{ k}\Omega$ ,  $g_m=40\text{ mA/V}$ ,  $r_o=100\text{ k}\Omega$ ,

a) Derive an expression for overall voltage gain

b) Find the magnitude of overall voltage gain.

c) Recalculate the magnitude of overall voltage gain neglecting  $r_o$

d) Find short circuit current gain

(6.0 M)

4) Derive an expression for magnitude response of Single Time Constant which do not attenuate low frequency components of the signal fed to its input and deduce an expression for its 3-dB cut-off frequency.

[6.0 M]

\*\*\*


**BITS-Pilani Dubai,**  
**Dubai International Academic City, Dubai**  
**I Semester, Academic Year 2008-09**  
Evaluation Component : TEST-II (Open Book)  
**EEE C424 / INSTR U313 MICROELECTRONIC CIRCUITS**

Date : 16<sup>th</sup> Nov. 2008  
 Duration: 50 mts


Max. Marks: 20  
 Weightage: 20%

- Note:- 1. ANSWER ALL QUESTIONS.  
 2. Make assumptions, if any, but explicitly indicate the assumptions made.  
 3. Only the Prescribed Text: Microelectronic Circuits by Sedra / Smith allowed.

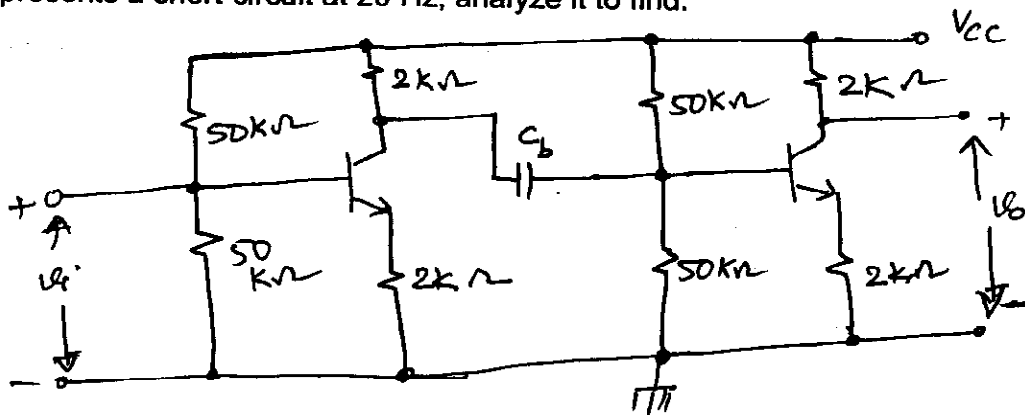- 1) Assuming that (i) transistors are identical with its h-parameter model parameters for each transistor:  $h_{re}=50$ ,  $h_{ie}=1.1K\Omega$ ,  $h_{re} = h_{oe}=0$  and (ii)  $C_z$  in the cascaded stage shown below represents a short-circuit at 20 Hz, analyze it to find:




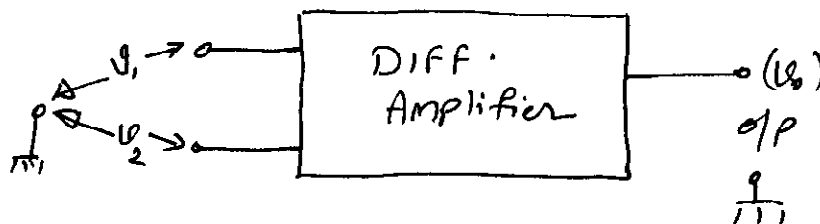- a) The mid band gain (2.0)  
 b) The value of the  $C_b$  necessary to give a lower 3-dB frequency of 20 Hz. (3.0 M)
- 2)
- a) Sketch the idealized bode amplitude and phase plots for if an amplifier's transfer function has one zero at  $f_z$  and one pole at  $f_p$  if (i)  $f_p < f_z$  and (ii)  $f_p > f_z$ . (2.0 M)  
 b) An amplifier with open-loop voltage gain  $A_v = 1,000 \pm 100$  is available. It is necessary to have an amplifier whose voltage gain varies by no more than  $\pm 0.1\%$ . Find (i) the reverse transmission factor,  $b$  of the feedback network used and (ii) gain of this amplifier with feedback. (2.0 M)  
 c) Starting from fundamentals derive an expression for the output voltage of the differential amplifier block shown below in terms of its CMRR( $\rho$ ), differential mode ( $A_d$ ) and common mode gain ( $A_c$ ). (2.0 M)



(Please Turn Over)

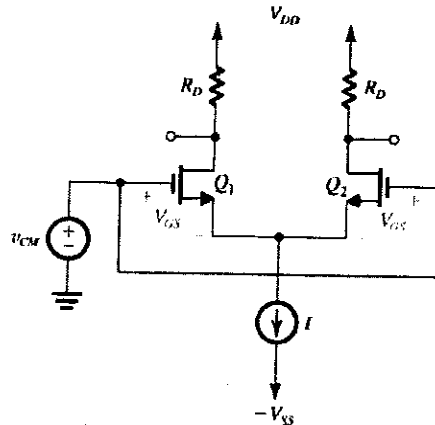- 3) For the MOS differential pair, shown below, a common mode voltage  $v_{CM}$  is applied. Assume  $V_{DD} = V_{SS} = 1.5$  V;  $k'_n(W/L) = 4$  mA/V<sup>2</sup>;  $V_t = 0.5$  V;  $I = 0.4$  mA and  $R_D = 2.5$  k $\Omega$ . Neglect channel length modulation:



- a) Find  $v_{ov}$  and  $V_{GS}$  for each transistor (2.0 M)
  - b) For  $v_{CM} = 0$ , find  $i_{D1}$ ,  $i_{D2}$ ,  $v_{D1}$ ,  $v_{D2}$  (2.0 M)
  - c) What is the highest value of  $v_{CM}$ , for which  $Q_1$  and  $Q_2$  remain in saturation (2.0 M)
- 4) A series-series feedback amplifier employs a basic amplifier with input and output resistances each of 1 k $\Omega$  and gain  $A = 2000$  V/V. The feedback factor  $\beta = 0.1$  V/V. Find the gain,  $A_f$ ; the input resistance,  $R_{if}$ ; and the output resistance,  $R_{of}$ . (3.0 M)

\*\*\*

ALL THE BEST

\*\*\*

*BJTS-Pilani Dubai, International Academic City, Dubai*  
*III YEAR EEE Evaluation Component : QUIZ-1*

**INSTR C 313 MICROELECTRONIC CIRCUIT DESIGN**

Max. Marks: 20

Duration: 20 mts

Weightage: 5%

1. BJT is a \_\_\_\_\_ polar device [1]
2. State the reason for power dissipation in amplifier (1)
3. The operating point is established by \_\_\_\_\_ (1)
4. The gain of buffer amplifier \_\_\_\_\_ (1)
5. The ideal characteristics for transconductance amplifier are  $R_i = \infty$  and  $R_o = \infty$ . Justify them (1)
6. Write the condition required for the cutoff frequency in RC filter (1)
7. Write doping relation among base, emitter and collector of a transistor. (1)
8. Why silicon is preferred for manufacturing semiconductor devices (1)
9. Small signal amplifier is operated in \_\_\_\_\_ region. (1)
10. If  $\alpha = 0.9$  for a transistor, find the value of base current if the emitter current is 25mA (1)
11. A BJT having  $\beta = 100$  is biased at a dc collector current of 1mA. Find the value of  $g_m$ . (1)
12. A BJT having  $\beta = 100$  is biased at a dc collector current of 1mA. Find the value of  $r_e$ . (1)

PTO

ID No:

Name

Date

13. A BJT having  $\beta=100$  is biased at a dc collector current of 1mA. Find the value of  $r_{\pi}$ . (1)

14. Draw the equivalent circuit of current amplifier (1)

15. Draw hybrid model of Voltage amplifier (1)

16. Derive the expression for gain in decibel in terms of current or voltage (1)

17. Write the classification of amplifier with respect to its configuration followed for its connection in the circuit. [1]

18. The value of current gain of CB amplifier is \_\_\_\_\_ [1]

19. Draw hybrid  $\pi$ -model circuit for PNP transistor. [1]

20. The advantage of multi stage amplifier is to have \_\_\_\_\_ gain [1]

ID No:

Name

Date

**BITS-Pilani Dubai, International Academic City, Dubai**

**III YEAR EEE Evaluation Component : QUIZ-2**

**INSTR C 313 MICROELECTRONIC CIRCUIT DESIGN**

**Max. Marks: 20**

**Duration: 20 mts**

**Weightage: 5%**

1. Define differential amplifier [1]
2. write the advantages of differential amplifier (2)
3. Write the various mode of operation of differential amplifier (2)
4. Define CMRR of differential amplifier (1)
5. Write the factors affecting CMRR of differential amplifier (2)
6. The value of CMRR for an ideal differential amplifier is \_\_\_\_\_ (1)
7. If constant DC bias current is  $I=2\text{mA}$  and the overdrive voltage  $V_{ov}=1\text{ V}$  in the differential amplifier, then the value of  $g_m$  is \_\_\_\_\_ (1)
8. The differential gain of differential amplifier with above specifications is \_\_\_\_\_, if the drain resistance is  $1\text{kohm}$  (1)
9. The range of input voltage for differential amplifier to operate in differential mode is \_\_\_\_\_ if the overdrive voltage is  $2\text{V}$  (1)

ID No:

Name

Date

10. At lower frequency, the frequency response of amplifier is \_\_\_\_\_ filter due to \_\_\_\_\_ capacitances. (2)

11. At higher frequency, the frequency response of amplifier is \_\_\_\_\_ filter due to \_\_\_\_\_ capacitances. (2)

12. What is miller effect (2)

13. What is miller multiplier (1)

14. The gain bandwidth product gives the \_\_\_\_\_ of amplifier (1)

Student Name: \_\_\_\_\_

BITS ID No.: \_\_\_\_\_

**BITS-Pilani Dubai, International Academic City, Dubai**

**I – Semester Academic Year 2008-09**

**Evaluation Component : QUIZ - II**

**INSTR UC 313 MICROELECTRONIC CIRCUITS**

**Date : 29<sup>th</sup> October 2008**

**Duration: 15 mts.**

**Maximum Marks:**

**Weightage : 5 %**

- Note:-
1. Respond ALL questions
  2. Fill the blanks, show the working and / or indicate the “most appropriate answer” or “most appropriate combination of Answers” as required for each question.
  2. Make your assumptions, if any, explicit
  3. All questions carry 1 mark unless otherwise indicated

1. Identify the following signals (as either voltage or current) of the generalized signal flow diagram of a Shunt-Series feedback amplifier

Input signal, $X_i$	Output Signal, $X_o$	Feedback Signal, $X_f$	Sampled Signal, $X_s$

2. Upon Application of Shunt-Shunt feedback to an open loop Amplifier, its input resistance will \_\_\_\_\_ (increase / decrease / remain unchanged) (0.5Mark)
3. Match the following configuration of feedback shown under I with the corresponding pair of the way “mixing and sampling” is accomplished as given under II ...by indicating the serial no. of I in the braces: “[ ]” of II.

I

- A. Series Series
- B. Shunt Series
- C. Shunt Shunt
- D. Series Shunt

II

- current mixing and current sampling [     ]
- current mixing and voltage sampling [     ]
- voltage mixing and current sampling [     ]
- voltage mixing and voltage sampling [     ]

4. In determining the loop gain  $A\beta$  through an approach in which conceptual feed back loop is broken and a test signal (as appropriate) is applied, express  $A\beta$  in terms of Open & Short circuit transfer functions ( $T_{oc}$  &  $T_{sc}$  respectively) and also provide expressions to find  $T_{oc}$  and  $T_{sc}$ . (2 Marks)

$A\beta =$  \_\_\_\_\_ ;  $T_{sc} =$  \_\_\_\_\_ ;  $T_{oc} =$  \_\_\_\_\_ where in

\_\_\_\_\_ is \_\_\_\_\_ ; \_\_\_\_\_ is \_\_\_\_\_ ;

\_\_\_\_\_ is \_\_\_\_\_ ; \_\_\_\_\_ is \_\_\_\_\_

5. If the two poles of a feedback amplifier are on the imaginary axis and are complex in nature then they occur as a \_\_\_\_\_ pair and the amplifier is said to have \_\_\_\_\_ response
6. The Phase margin is \_\_\_\_\_ degrees minus \_\_\_\_\_ at the frequency at which \_\_\_\_\_ is unity.
7. From the general rule of thumb in ensuring Feedback amplifier's stability, at the intersection of  $20\log [1 / |\beta(j\omega)|]$  and  $20\log |A(j\omega)|$  the \_\_\_\_\_ should not exceed 20 dB / decade.



ID No:

Name

Date

**BITS-Pilani Dubai, International Academic City, Dubai**

**III YEAR EEE Evaluation Component : QUIZ-3**

**EEE C 424 MICROELECTRONIC CIRCUITS**

**Max. Marks: 20**

**Duration: 20 mts**

**Weightage: 5%**

1. Write the reason for selecting active filter. [1]
2. Write the reason choosing inductor less filter. [1]
3. Write the conditioned required for the BPF filter being formed by LPF followed by HPF in series connection . [1]
4. The LPF and the HPF are connected in parallel with a condition that cutoff frequency of LPF is greater than cutoff frequency HPF. What is the kind of filter this connection formed? [1]
5. Draw the frequency response of Low Pass Chebyshev filter. [1]
6. How is the order of filter determined? [1]
7. Write the advantage of higher order filter. [1]

8. Write the disadvantage of higher order filter. [1]
9. Write the transfer function of all poles filter. [1]
10. Determine the order  $N$  of Butterworth filter for which  $A_{\max}=1\text{dB}$ ,  $\omega_s/\omega_p=1.5$  and  $A_{\min}=30\text{dB}$ . What is the minimum stop band attenuation realized? If  $A_{\min}=30\text{dB}$  exactly, to what value can  $A_{\max}$  be reduced? [3]
11. Write the application of tuned Amplifier. [1]
12. Find the frequency of selection of the tuned circuit having  $L=100\text{mh}$  and  $C=0,01\text{ MFD}$ . [2]
13. Draw the frequency response of parallel tuned circuit if the output voltage is taken across  $L$  and  $C$ . [2]
14. Design a RC 2<sup>nd</sup> order HPF active filter having cutoff frequency 4 khz [3]

BITS ID. No.: \_\_\_\_\_

Student Name: \_\_\_\_\_

**BITS, Pilani – Dubai**  
**Dubai International Academic City, Dubai**  
**I-semester, Academic Year:-2008-2009**

Date : 17<sup>th</sup> September, 2008

Maximum Marks: 20

**INSTR C313 MICROELECTRONIC CIRCUITS**

**Surprise Quiz No.1**

**Note:-**Unless explicitly mentioned, each question carries 1 mark **for the most appropriate answer.**

1. The term "Amplifier" is defined as: \_\_\_\_\_
2. An amplifier response is characterized by the equation:  $v_o(t) = Av_i(t)$  where  $v_o(t)$  and  $v_i(t)$  are the output and input signals respectively, and  $A$  is a constant representing the magnitude of amplification. If this relationship between  $v_o(t)$  and  $v_i(t)$  contains \_\_\_\_\_, then the waveform of  $v_o(t)$  will be no longer be identical to that of  $v_i(t)$ ; and the amplifier is said to exhibit nonlinear distortion.
3. Voltage gain  $A_v$  in dB can be expressed as: \_\_\_\_\_
4. Power gain  $A_p$  in dB can be expressed as: \_\_\_\_\_
5. Amplifier efficiency,  $\eta$  is defined as: \_\_\_\_\_
6. Assuming that an amplifier with its voltage gain as  $A_v$  uses two power supplies and its transfer characteristics exhibit the positive and negative saturation levels denoted by  $L_+$  and  $L_-$ , in order to avoid signal distortion in the output waveform, the input signal swing must be kept with the linear range of operation, expressed by the following inequality:  
\_\_\_\_\_
7. A General Purpose Amplifier's frequency response on the low frequency side can be modeled as a \_\_\_\_\_ Single time constant circuit.
8. A General Purpose Amplifier's frequency response on the high frequency side can be modeled as a \_\_\_\_\_ Single time constant circuit.
9. If a BJT is to work as an amplifier, indicate the biasing conditions to be established:  
Emitter Base Junction : \_\_\_\_\_; Collector Base Junction: \_\_\_\_\_.

(please turn over)

10. List the names of any two Biasing schemes for biasing BJT as an Amplifier

- a. \_\_\_\_\_
- b. \_\_\_\_\_

11. List any Five Significant Parameters of a General Purpose Amplifier

[2.5 M]

- a. \_\_\_\_\_
- b. \_\_\_\_\_
- c. \_\_\_\_\_
- d. \_\_\_\_\_
- e. \_\_\_\_\_

12. Indicate the following typical voltages in a BJT when it is appropriately biased: [1.5 M]

- a.  $V_{BE}(\text{cut-in})$  = \_\_\_\_\_
- b.  $V_{CE}(\text{cut-off})$  = \_\_\_\_\_
- c.  $V_{CE}(\text{saturation})$  = \_\_\_\_\_

13. Draw the low frequency model of a Current Amplifier with Source and Load connected to it appropriately(in the space provided below) [2.0 M]

14. On the basis of its loading effect what are the four classifications of an Amplifier [2.0 M]

- a. \_\_\_\_\_
- b. \_\_\_\_\_
- c. \_\_\_\_\_
- d. \_\_\_\_\_

15. Draw the Small Signal AC Equivalent Model of a BJT CE Amplifier

[2.0 M]

BITS ID. No.:\_\_\_\_\_

Student Name:-\_\_\_\_\_

**BITS, Pilani – Dubai**  
**Dubai International Academic City, Dubai**  
**I-semester, Academic Year:-2008-2009**

Date : 27<sup>th</sup> November, 2008

Maximum Marks:\_\_\_\_\_

**INSTR C313 MICROELECTRONIC CIRCUITS**

**Surprise Quiz No.3**

**Note:-**Unless explicitly mentioned, each question carries 2 marks **for the most appropriate answer.**

- 
1. A two stage amplifier is required to have an upper cut off frequency of 2 MHz and a lower cutoff frequency of 30 Hz. The upper and lower cutoff frequencies of the individual, but identical, stages are [      ]
    - A. 4 MHz, 60 Hz
    - B. 3 MHz, 20 Hz
    - C. 3 MHz, 60 Hz
    - D. 4 MHz, 20 Hz
  2. Most of the linear ICs are based on the two transistor differential amplifier because of its [      ]
    - A. Input voltage dependent linear transfer characteristic
    - B. High voltage gain
    - C. High input resistance
    - D. High CMRR .
  3. Class AB operation is often used in power (large signal) amplifiers in order to [      ]
    - A. Get maximum efficiency
    - B. Remove even harmonics
    - C. Overcome a cross-over distortion
    - D. Reduce collector dissipation
  4. In a CE amplifier, the un-bypassed emitter resistance provides [      ]
    - A. Voltage shunt feedback
    - B. Current Series feedback
    - C. Negative-voltage feedback
    - D. Positive-current feedback
  5. Most of the linear ICs are based on the two transistor differential amplifier because of its [      ]
    - A. Input voltage dependent linear transfer characteristic
    - B. High voltage gain
    - C. High input resistance
    - D. High CMRR
  6. A Class-A transformer coupled transistor power amplifier is required to deliver a power output of 10 watts. The maximum power rating of the transistor should be not less than [      ]
    - A. 5 W
    - B. 10 W
    - C. 20 W
    - D. 40 W

7. A differential amplifier is invariably employed as the input (very first) stage of all OPAMPs. This is done basically to provide the OPAMPs with a very high [      ]
- A. CMRR
  - B. Bandwidth
  - C. Slew Rate
  - D. Open Loop Gain
8. A multistage amplifier has a low-pass response with three real poles at  $s=-\omega_1$ ,  $-\omega_2$ , and  $s=-\omega_3$ . The approximate overall bandwidth B of the amplifier is given by [      ]
- A.  $B = \omega_1 + \omega_2 + \omega_3$ .
  - B.  $1/B = (1/\omega_1) + (1/\omega_2) + (1/\omega_3)$ .
  - C.  $B = (\omega_1 \cdot \omega_2 \cdot \omega_3)^{1/3}$
  - D.  $B = \text{Square root of } (\omega_1^2 + \omega_2^2 + \omega_3^2)$
9. An amplifier has an open loop gain of 100, an input resistance of  $1 \text{ K}\Omega$ , and an output resistance of  $100\Omega$ . A feedback network with a feedback factor of 0.99 is connected in a voltage series feedback mode. The new input and output resistances are \_\_\_\_\_ and \_\_\_\_\_ respectively.
10. Amplifier efficiency,  $\eta$  is defined as: \_\_\_\_\_

\* \* \*

BITS ID. No.:- \_\_\_\_\_

Student Name:- \_\_\_\_\_

**BITS, Pilani – Dubai**  
**Dubai International Academic City, Dubai**  
**I-semester, Academic Year:-2008-2009**

Date: 18<sup>th</sup> December, 2008


Max. Marks : 45  
Time : 20 mts

**INSTR C313 / EEE C424 MICROELECTRONIC CIRCUITS**

**Surprise Quiz No.5**

**Note:-**Unless explicitly mentioned, each question carries 1mark for the most appropriate answer.

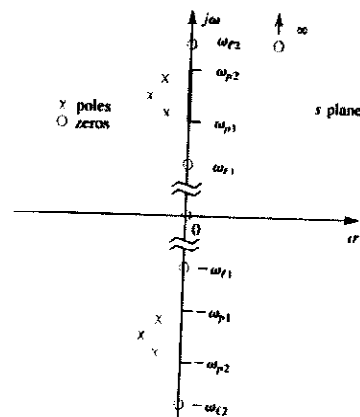- 1) List the four different types of Filters that perform frequency selection function: [ 4 M]
  - a) \_\_\_\_\_
  - b) \_\_\_\_\_
  - c) \_\_\_\_\_
  - d) \_\_\_\_\_
- 2) List the four parameters using which the transmission of a low-pass filter is specified: [ 4 M]
  - a) \_\_\_\_\_
  - b) \_\_\_\_\_
  - c) \_\_\_\_\_
  - d) \_\_\_\_\_
- 3) The process of obtaining filter transfer function that meets given specifications is known as: [ 1 M]  
\_\_\_\_\_
- 4) Identify the order and type of filter from the pole zero plot given below:  
Order is : \_\_\_\_\_; Type of the Filter is: \_\_\_\_\_ [ 2 M]



- 5) The magnitude function for an Nth-order Butterworth filter with a passband edge  $\omega_p$ , is given by:

$$|T(j\omega)| =$$

in which the parameter  $\epsilon$  is given by : \_\_\_\_\_ [ 2 M]

- 6) The expression for  $A_{\max}$ , the maximum variation in passband transmission of a Butterworth low-pass filter is given by :

$$A_{\max} = \text{_____} [ 1 M]$$

- 7) Make a statement that describes the property, as a consequence of which the Butterworth response is termed as Maximally flat response.

\_\_\_\_\_ [ 1 M]

- 8) The magnitude function for an Nth-order Chebyshev filter with a passband edge  $\omega_p$ , is given by:

$$|T(j\omega)| = \text{_____} \quad \text{for } \omega < \omega_p \quad [ 1 M]$$

$$|T(j\omega)| = \text{_____} \quad \text{for } \omega > \omega_p \quad [ 1 M]$$

in which the parameter  $\epsilon$  is given by : \_\_\_\_\_ [ 1 M]

- 9) The expression for  $A_{\max}$ , the maximum variation in passband transmission of a Butterworth low-pass filter is given by :

$$A_{\max} = \text{_____} [ 1 M]$$

- 10) Indicate the four steps using which the transfer function of a Chebyshev lowpass filter can be obtained from the transmission specifications of a lowpass filter. [ 4 M]

- \_\_\_\_\_
- \_\_\_\_\_
- \_\_\_\_\_
- \_\_\_\_\_



11) Indicate in the space provided below the plot of s-plane singularities of a typical 2-pole Notch filter with: center frequency  $\omega_0$ ; and pole quality factor,  $Q$ ; and a high frequency gain of  $a_2$ . [ 2 M]

12) Frequency response of a tuned amplifier is characterized by the following three parameters: [ 3 M]

- a) \_\_\_\_\_
- b) \_\_\_\_\_
- c) \_\_\_\_\_

13) The skirt selectivity of a tuned amplifier is defined as \_\_\_\_\_. [ 1 M]

14) Draw a circuit diagram, in the space provided below, that depicts the basic principle of tuned amplifiers using MOSFET as the active device: [ 2 M]

15) Transformers are employed in Tuned amplifiers mainly because of the following practice problem: \_\_\_\_\_ and the main function of the transformer, thus employed is to have \_\_\_\_\_. [ 2 M]

16) Draw the frequency response of (i) a typical synchronously tuned and (ii) a stagger tuned amplifier depicting both individual and overall responses of employed multiple stages, if any. [ 2 M]

17) An inductance of  $36\ \mu\text{H}$  is resonated with a  $1000\text{-pF}$  capacitor in a tuned amplifier. If the inductor is tapped at one-third of its turns and a  $1\text{k}\Omega$  resistor is connected across the one-third part, find  $f_0$  and  $Q$  of this resonator connected to the tuned amplifier. [ 2 M]

18) A transistor used as a power amplifier supplied  $0.85\text{ W}$  to a  $4\text{ K}\Omega$  load. The zero-signal dc collector current is  $31\text{ mA}$ , and the dc collector current with signal is  $34\text{ mA}$ . Determine the percent second-harmonic distortion. [ 2 M]

19) A single transistor is operating as an ideal class B amplifier with  $1\text{-K}\Omega$  load. A dc meter in the collector circuit reads  $10\text{ mA}$ . How much signal power is delivered to the load? [ 3 M]

20) The effect of the capacitance from collector to base ( $C_{\mu}$ ) can be taken into account during analysis and / or design of double tuned BJT amplifier by using its \_\_\_\_\_ and there \_\_\_\_\_ methods that exist to minimize its effect. [ 2 M]

\* \* \*

**BITS-Pilani Dubai,**  
**Dubai International Academic City, Dubai**  
**III Year, I Semester, Academic Year 2008-09**  
Evaluation Component : Comprehensive Examination (Closed Book)

**EEE C424 / INSTR C313 MICROELECTRONIC CIRCUITS**


Date : 4<sup>th</sup> Jan. 2009  
Duration: 3 hours

Max. Marks: 100  
Weightage: 40%

Note:- 1. ANSWER ALL QUESTIONS

2. Make assumptions, if any, but explicitly indicate the assumptions made

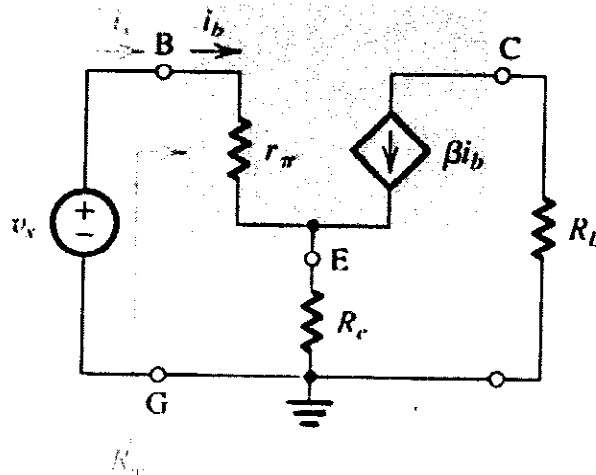
- 1) Define and write briefly (using a couple of sentences) on the following terms with reference to Amplifiers: [1x10=10 M]
  - a) Transfer Characteristics
  - b) Maximum Signal Handling Capacity
  - c) Voltage Gain in dB
  - d) Frequency Response
  - e) Amplifier's Stability
  - f) 'A Circuit' of a Feedback Amplifier
  - g) Common Mode Gain,  $A_c$  of a Differential Amplifier
  - h) Common Mode Rejection Ratio (CMRR) of Differential Amplifiers
  - i) Efficiency of a Power Amplifier
  - j) Skirt Selectivity of a Tuned Amplifiers
- 2)
  - a) List the FIVE important steps in the systematic process of analyzing BJT transistor amplifier circuits employing small signal BJT circuit models [5 M]
  - b) Draw the h-parameter model of a BJT in CE Configuration with voltage source and load resistance connected to BJT. Define all the model parameters and derive expressions this amplifier's mid-band voltage gain. [1+4+2=7.0 M]
  - c) Determine the input impedance,  $R_{in}$ , of the circuit shown below: [3 M]



(Please Turn Over to Page 2)

3)

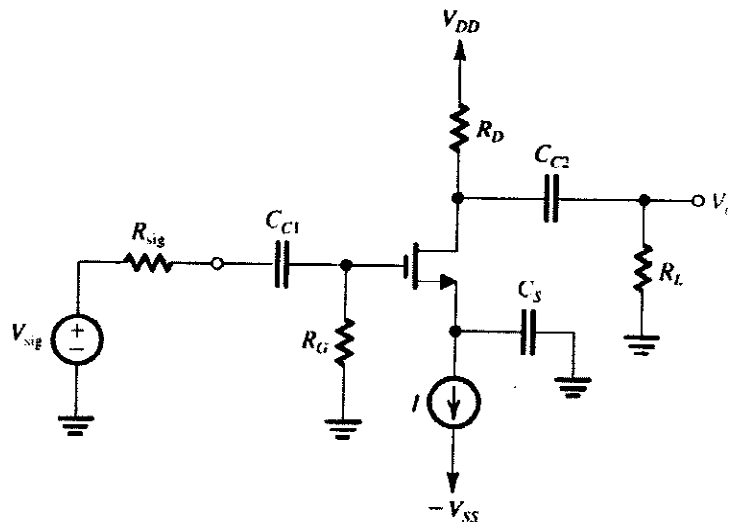- a) Draw the MOSFET high frequency model indicating all its components using standard notation and derive an expression for the figure of merit ( $f_T$ ) of MOSFET's high frequency operation from fundamentals. [2+3=5.0 M]
- b) Consider a CS amplifier, shown below, which is fed with a signal source having an internal resistance  $R_{sig}=100\text{ K}\Omega$ . The amplifier has  $R_G=4.7\text{ M}\Omega$ ;  $R_D=R_L=15\text{ K}\Omega$ ;  $g_m=1\text{ mA/V}$ ;  $r_o=150\text{ K}\Omega$ ,  $C_{gs}=1\text{ pF}$  and  $C_{gd}=0.4\text{ pF}$ .



Find:

- the mid band gain [2 M]
- upper 3-dB frequency  $f_H$  [3 M]
- both (i) and (ii) above if  $R_{sig}$  is reduced to  $10\text{ K}\Omega$  [2+3=5 M]


4)

- a) A series-series feedback amplifier employs a basic amplifier with input and output resistances each of  $1\text{ k}\Omega$  and gain  $A=2000\text{ V/V}$ . The feedback factor  $\beta=0.1\text{ V/V}$ . Find
- the gain,  $A_f$ ; [1 M]
  - the input resistance,  $R_{if}$ ; and [2 M]
  - the output resistance,  $R_{of}$  [2 M]
- b) A feedback amplifier is to be designed using a feedback loop connected around a two stage amplifier. The first stage is direct coupled small signal amplifier with a high upper 3-dB frequency. The second stage is a power output stage with a mid band gain of  $10\text{ V/V}$  with upper and lower 3-dB frequencies of  $8\text{ kHz}$  and  $80\text{ Hz}$  respectively. The feedback amplifier should have a mid band gain of  $100\text{ V/V}$  and upper 3-dB frequency of  $40\text{ kHz}$ .
- What is the required gain of the small-signal amplifier? [2 M]
  - What value of  $\beta$  should be used? [1 M]
  - What does the lower 3-dB frequency of the overall amplifier will become? [2 M]


(Please Turn Over to Page 3)

5)

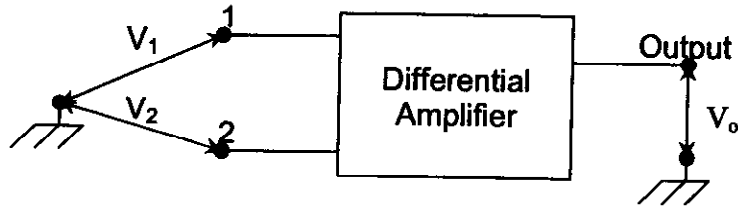- a) Obtain an expression for the output voltage of the following differential amplifier in terms of CMRR ( $\rho$ ), Common-mode voltage ( $V_c$ ) and the Differential voltage ( $V_d$ ) [5 M]




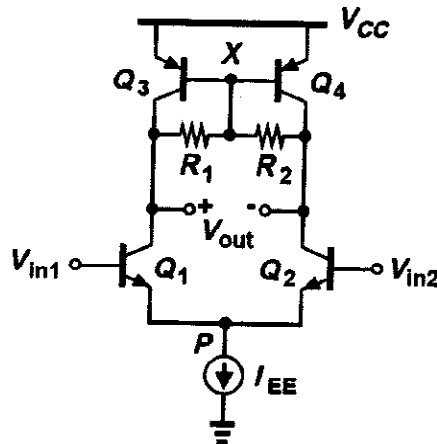- b) Consider the circuit shown below, for which the Early Voltage ( $V_A$ ) for each of the Transistors is given as:  $V_{A,NPN} = 5\text{ V}$  and  $V_{A,PNP} = 4\text{ V}$ .



- i) Explain under what conditions of this circuit, the differential amplifier depicted above "rejects" a common-mode input voltage [1 M]  
 ii) If  $R_1 = R_2 = 5\text{ k}\Omega$ , what value of  $I_{EE}$  is required to achieve a differential voltage gain of 50? [2 M]

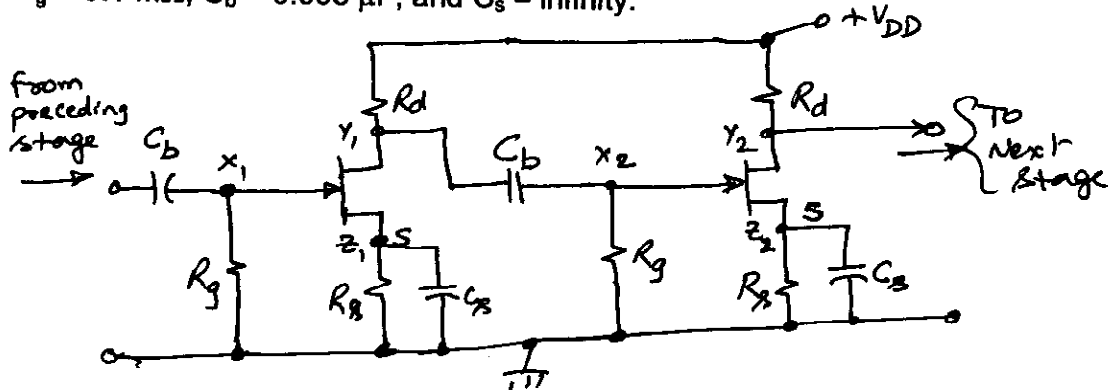- 6) A Three stage RC Coupled amplifier, as in the circuit diagram shown below, uses field-effect transistors with the following parameters  $g_m = 2.6\text{ mA/V}$ ,  $r_d = 7.7\text{ k}\Omega$ ,  $R_d = 10\text{ k}\Omega$ ,  $R_g = 0.1\text{ M}\Omega$ ,  $C_b = 0.005\text{ }\mu\text{F}$ , and  $C_s = \text{infinity}$ .



- a) Evaluate overall mid band voltage gain in decibels [3 M]  
 b)  $f_L$  of each individual stage and [3 M]  
 c) the overall lower 3dB frequency [4 M]

- 7) A three pole feedback amplifier has a dc gain without feedback of  $-10^4$ . All three open-loop poles are at  $f=2$  MHz.
- What is the maximum value of  $\beta$  for which the amplifier is stable? [2 M]
  - Assume that one of the poles is shifted to  $f_1=100$  kHz. Using the value of  $\beta$  found in part (a), what is the gain margin of the modified circuit? [2 M]
- 8) Draw the Circuit of a Class B push-pull output stage and prove, from fundamentals that, it offers a theoretical maximum conversion efficiency of 78.5%. What is crossover distortion in Class B operation and indicate its source. [1+3+0.5+0.5 =5 M]
- 9) Draw a neat sketch to depict the specification of the transmission characteristics of a Butterworth low pass active filter both in terms of magnitude response and pole zero plot and list the four important parameters that aptly specify its magnitude response. Also enumerate the steps in designing the same meeting these specifications. [1+1+2+4=8 M]
- 10) Write Short Notes on any THREE of the following topics: [3x 5 M=15 M]
- Compare and contrast significant features of a BJT with those of an FET, in its use as an amplifying device
  - Circuit diagram and features of Transistor pairs: Cascode, Darlington and Totempole
  - Stagger Tuned Amplifiers
  - Stability analysis of Feedback Amplifiers
  - Current Mirrors and their applications
  - Typical features of the input, output and intermediate stages of a multistage amplifier
  - PSPICE as an Electronic Design Automation (EDA) tool

\*\*\* WISH YOU ALL THE BEST \*\*\*