

**B**

Name:

ID Number:

**BITS PILANI DUBAI CAMPUS  
EEE UC424/INSTR UC313  
MICROELECTRONIC CIRCUITS  
QUIZ 1**

Date: 21/09/06  
Weightage: 10%

Max. Marks: 10  
Time: 30 mts

Answer ALL Questions

- 1) An amplifier has a voltage gain of 100 and a current gain of 1000. The voltage gain is \_\_\_\_\_ dB and current gain is \_\_\_\_\_ dB. The power gain is \_\_\_\_\_ dB.
- 2). Show the circuit model of a voltage amplifier.
- 3 Show the equivalent circuit of trans resistance amplifier.
- 4 Show the frequency response of Direct coupled and Tuned amplifiers
- 5 Define amplifier bandwidth.

- 6 Draw the small signal circuit model for a bipolar junction transistor (BJT).
7. Show the low pass single time constant network.
8. Show the High pass magnitude response of single time constant network.
9. Show the output characteristics of BJT in common emitter configuration.
10. Define h parameters of two port network.

- Note:-
1. ANSWER ALL QUESTIONS
  2. Students are permitted to use their own blank graph sheets after taking signature of invigilator on it just before its usage
  3. Make assumptions, if any, but explicitly indicate the assumptions made

1.

- A. Define the following terms with reference to a general purpose amplifier
- i. Voltage Gain in dB
  - ii. Current Gain in dB
  - iii. Amplifier Efficiency
  - iv. Transfer Characteristics
  - v. Amplifier Saturation


[10 M]

- B. Draw the circuit model for a voltage amplifier. With the input signal source and the load connected to it, derive expressions for (i) the amplifier's output voltage,  $v_o$ ; (ii) voltage gain  $A_v$ ; (iii) amplifier's input voltage,  $v_i$  and (iv) the overall voltage gain,  $v_o/v_s$ . [6 M]

- C. Consider a voltage amplifier having a frequency response of a low pass Single Time Constant type with a dc gain of 60dB and a 3 dB frequency of 1000Hz. Find the gain in dB at  $f =$  (i) 10Hz, (ii) 10 KHz; (iii) 100 KHz, and (iv) 1 MHz. [4 M]

2.

 - A. A BJT having  $\beta = 100$  is biased at a dc collector current of 1 mA. Find, at the bias point, the value of transconductance,  $g_m$ ; and the small signal resistances between base and emitter viz, the one looking into the base,  $r_e$ ; and that looking into the emitter  $r_\pi$ . [4 M]
- B. List the FIVE important steps in the systematic process of analyzing BJT transistor amplifier circuits employing small signal BJT circuit models. [5 M]
- C. The emitter follower shown in figure is used to connect a source with  $R_{sig} = 10 \text{ K}\Omega$  to a load  $R_L = 1 \text{ K}\Omega$ . The transistor is biased at  $I = 5 \text{ mA}$ , utilizes a resistance  $R_B = 40 \text{ K}\Omega$ , and has  $\beta = 100$ , Early Voltage ( $V_A$ ) = 100V.




- i. Find  $R_{ib}$ ,  $R_{in}$ ,  $G_v$ ,  $G_{vo}$  and  $R_{out}$ . [5 M]
- ii. What is the largest peak amplitude of an output sinusoid that can be used without the transistor cutting off? [2 M]
- iii. If in order to limit nonlinear distortion the base-emitter signal voltage is limited to 10mV peak, what is the corresponding amplitude at the output? [2 M]
- iv. What will the overall voltage gain become if  $R_L$  is changed to 2 K $\Omega$  to 500 $\Omega$ ? [2 M]

3.


- A. An amplifier with open-loop gain  $A_v = 1,000 \pm 100$  is available. It is necessary to have an amplifier whose voltage gain varies by no more than  $\pm 0.1\%$ .
- Find the reverse transmission factor  $\beta$  of the feedback network used [2 M]
  - Find the gain with feedback [2 M]
- B. For the circuit shown below, assuming that  $g_m = 5 \text{ mA/V}$  and  $r_d = 100 \text{ K}\Omega$ , find
- the Current gain,  $A_i = I_L / I_s$ ;
  - the Voltage gain  $A_v = V_o / V_s$ ;
  - Transconductance,  $G_M = I_L / V_s$ ;
  - The Transresistance,  $R_M = V_o / I_s$ ;
  - the Input resistance seen by the source,  $R_i$  and
  - the Output resistance seen by the load,  $R_o$ .

[6 M]

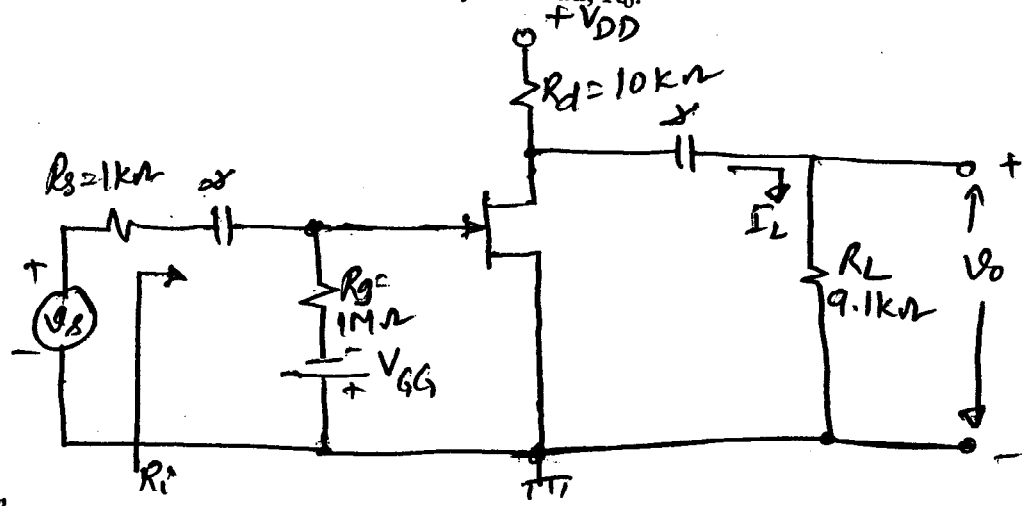


4.

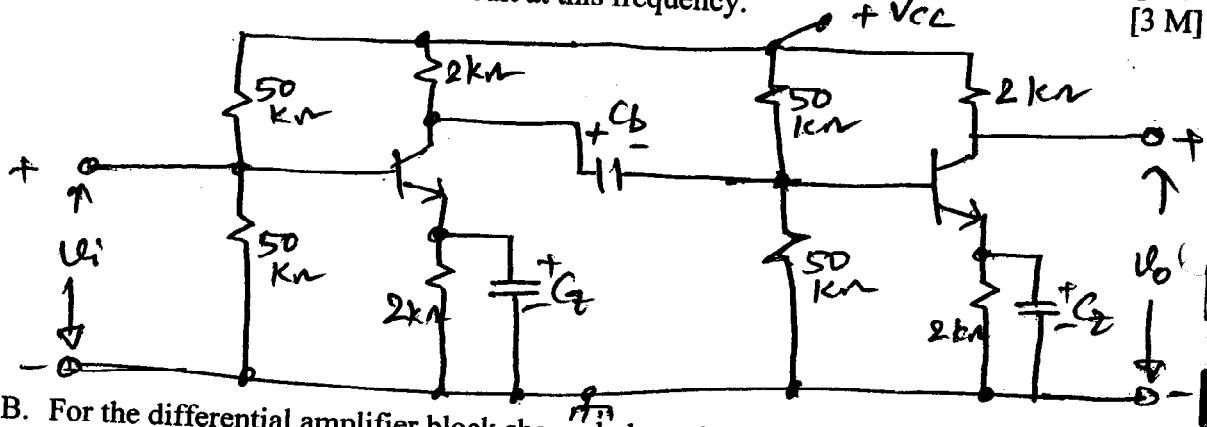- A. The parameters of the transistors in the circuit shown below are  $h_{fe} = 50$ ;  $h_{ie} = 1.1 \text{ K}\Omega$ ,  $h_{re} = h_{oc} = 0$ . Find
- the mid band gain, [2 M]
  - the value of  $C_b$  necessary to give a lower 3-dB frequency of 20 Hz assuming that  $C_z$  represents a short circuit at this frequency. [3 M]




 - B. For the differential amplifier block shown below obtain an expression for the output in terms of its Differential gain  $A_d$ ; differential and common mode voltages ( $v_d$  and  $v_c$ ) and the CMRR,  $\rho$ . [5 M]



5.

 - A. Draw the MOSFET high frequency model indicating all its components using standard notation and derive an expression for the figure of merit ( $f_T$ ) of MOSFET's high frequency operation from fundamentals. [8 M]
- B. Consider a CS amplifier, shown below, which is fed with a signal source having a



- internal resistance  $R_{sig}=100\text{ K}\Omega$ . The amplifier has  $R_G=4.7\text{ M}\Omega$ ;  $R_D=R_L=15\text{ K}\Omega$ ;  $g_m=1\text{ mA/V}$ ;  $r_o=150\text{ K}\Omega$ ,  $C_{gs}=1\text{ pF}$  and  $C_{gd}=0.4\text{ pF}$ . Find
- the mid band gain [3 M]
  - upper 3-dB frequency  $f_H$  [3 M]
  - both (i) and (ii) above if  $R_{sig}$  is reduced to  $10\text{ K}\Omega$ . [6 M]

6.

- A. Draw the Circuit of a Class B push-pull output stage and prove, from fundamentals that, it offers a theoretical maximum conversion efficiency of 78.5%. Indicate the source of crossover distortion in Class B operation. [5 M]
- B. Draw a neat sketch to depict the specification of the transmission characteristics of a Chebyshev low pass active filter both in terms of magnitude response and pole zero plot and list the four important parameters that aptly specify its magnitude response. Also enumerate the steps in designing the same meeting these specifications. [5 M]

7.

- Write Short notes on any TWO of the following: [10 M]
- Issues in the design of Tuned amplifiers
  - Features and importance of multistage amplifiers employing compound devices
  - PSPICE as a tool in Electronic Design Analysis
  - Current Mirrors and Sources employed in IC Biasing

\*\*\*\*\* ) ALL THE BEST (\*\*\*\*\*


Date : 23<sup>rd</sup> Nov. 2006

Duration: 50 mts


Max. Marks: 20  
Weightage: 20%

- Note:-
1. ANSWER ALL QUESTIONS
  2. Students are permitted to use their own blank graph sheets after taking signature of invigilator on it just before its usage
  3. Make assumptions, if any, but explicitly indicate the assumptions made


1. An amplifier consists of three identical stages connected in cascade. The output voltage is sampled and returned to the input in series opposing. If it is specified that the relative change  $dA_f/A_f$  in the closed loop gain  $A_f$  must not exceed  $\psi_f$ , show that the minimum value of the open-loop gain  $A$  of the amplifier is given by  $A = 3.A_f |\psi_f| / |\psi_f|$  where  $|\psi_f| = dA_1/A_1$  is the relative change in the voltage gain of each stage of the amplifier (5 M)
2. For the circuit shown below, Find the (A) Voltage gain and (B) output impedance at the terminals (i) AN and (ii) BN of the circuit assuming that  $g_m = 6 \text{ mA/V}$  and  $r_d = 10 \text{ K}\Omega$ ,  $R_g = 1 \text{ M}\Omega$ ;  $R_d = 50 \text{ K}\Omega$ , neglecting reactances of all capacitors. (2 M + 2 M + 2 M = 6 M)

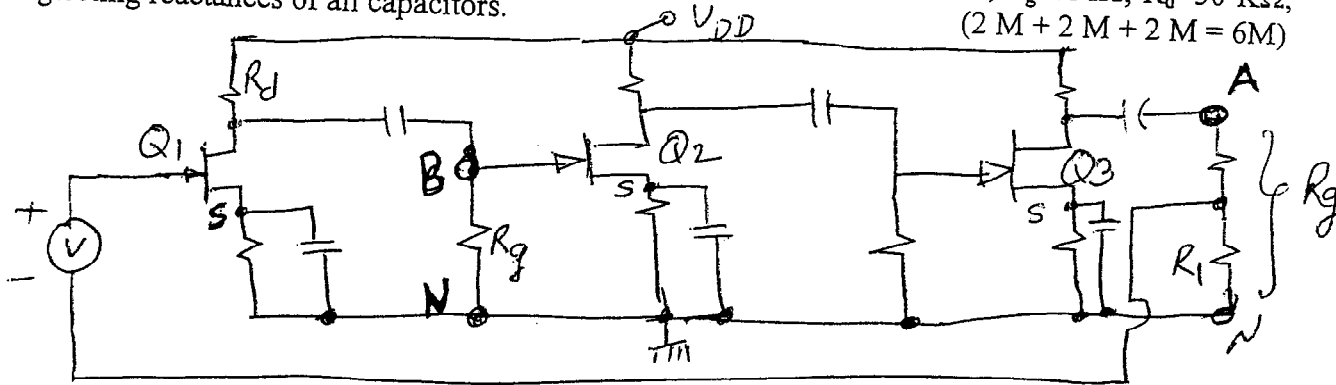

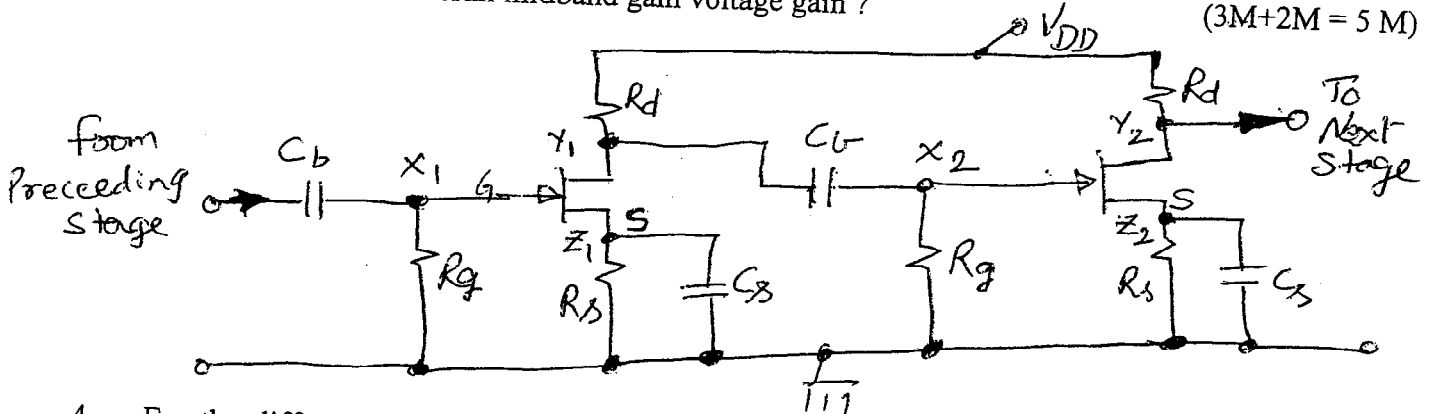3. The FET RC coupled amplifier has the following parameters:  $g_m = 10 \text{ mA/V}$  and  $r_d = 5.5 \text{ K}\Omega$ ,  $R_g = 10 \text{ K}\Omega$ ;  $R_s = 0.5 \text{ K}\Omega$  for each stage. Assume  $C_s$  is arbitrarily large. (a) What must be the value of  $C_b$  in order that the frequency characteristic of each stage be flat within 1 dB down to 10 Hz? (b) What is the overall midband gain voltage gain? (3M+2M = 5 M)



 
4. For the differential amplifier using an ideal OP AMP block shown below (a) find the output voltage  $v_o$ . (b) Show that the output corresponding to the common-mode voltage  $v_c = 0.5 (v_1 + v_2) = 0$  if  $R'/R = R_1/R_2$ . Find  $v_o$  in this case. and (c) the CMRR,  $\rho$  of the amplifier if  $R'/R \neq R_1/R_2$ . (4M)




REST OF LUCK

- Note:-
1. ANSWER ALL QUESTIONS
  2. Students are permitted to use their own blank graph sheets after taking signature of invigilator on it just before its usage
  3. Make assumptions, if any, but explicitly indicate the assumptions made

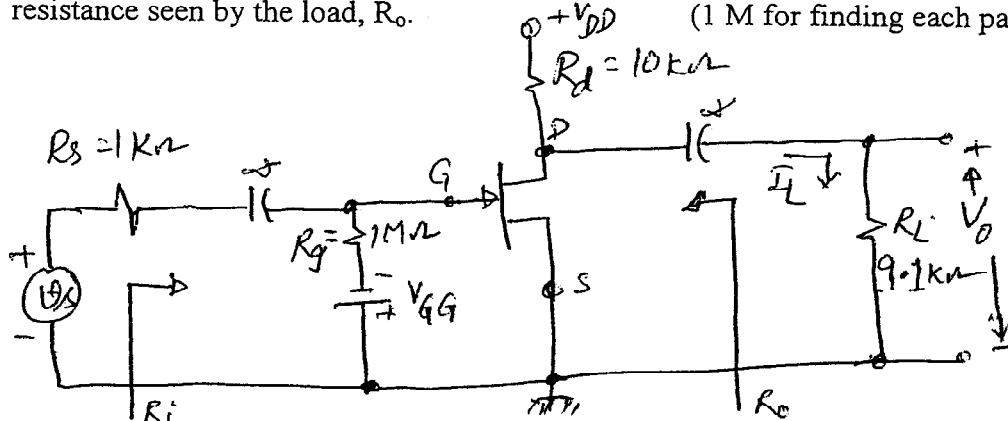
1. An amplifier with open-loop gain  $A_V=1,000 \pm 100$  is available. It is necessary to have an amplifier whose voltage gain varies by no more than  $\pm 0.1\%$ .
  - A. Find the reverse transmission factor  $\beta$  of the feedback network used (2.5M)
  - B. Find the gain with feedback (2.5M)
2. For the circuit shown assuming that  $g_m=5 \text{ mA/V}$  and  $r_d=100 \text{ K}\Omega$ , find the Current gain,  $A_I = I_L/I_S$ ; the Voltage gain  $A_V = V_o/V_s$ ; Transconductance,  $G_M = I_L/V_s$ ; The Transresistance,  $R_M = V_o/I_s$ ; the Input resistance seen by the source,  $R_i$  and the Output resistance seen by the load,  $R_o$ . (1 M for finding each parameter= 6 M)



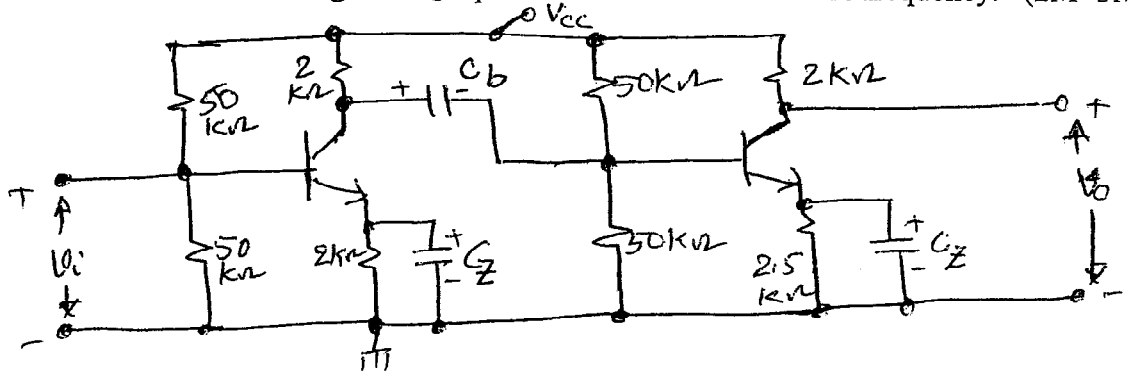3. The parameters of the transistors in the circuit shown below are  $h_{fe}=50$ ;  $h_{ie}=1.1 \text{ K}\Omega$ ,  $h_{re}=h_{oc}=0$ . Find (a) the mid band gain, (b) the value of  $C_b$  necessary to give a lower 3-dB frequency of 20 Hz assuming that  $C_z$  represents a short circuit at this frequency. (2M+3M)



 4. For the differential amplifier block shown below obtain an expression for the output in terms of its Differential gain  $A_d$ ; differential and common mode voltages ( $v_d$  and  $v_c$ ) and the CMRR,  $\rho$ . (4 M)



\*\*\*\*\* ) ALL THE BEST (\*\*\*\*\*

Student Name:



BITS ID No.:

*BITS-Pilani Dubai Campus, Knowledge Village, Dubai*

Evaluation Component : **QUIZ-II**

EEE UC 424 / INSTR UC 313 MICROELECTRONIC CIRCUITS

Date : 02<sup>nd</sup> Nov. 2006

Duration: 30 mts

Max. Marks: 30  
Weightage: 10%

- Note:-
1. Respond ALL questions
  2. Fill the blanks, show the working and / or indicate the "most appropriate answer" or "most appropriate combination of Answers" as required for each question.
  2. Make your assumptions, if any, explicit
- - -

1. Expand the Acronym : IG FET \_\_\_\_\_
2. Consider the statement : "A 0.1  $\mu\text{m}$  CMOS technology is being employed in several applications of consumer electronics." Here "0.1  $\mu\text{m}$ " represents: \_\_\_\_\_
3. The Output characteristics of a FET can broadly be divided into three distinct regions of operation namely :
  1. \_\_\_\_\_
  2. \_\_\_\_\_ and
  3. \_\_\_\_\_
4. In order to obtain linear amplification, the MOSFET is biased to operate somewhere near the \_\_\_\_\_ of the \_\_\_\_\_ region of its characteristics.
5. A good bias design ensures that the parameters of the bias point namely \_\_\_\_\_ , \_\_\_\_\_ and \_\_\_\_\_ are predictable and stable.
6. An Alternate method of biasing instead of "fixing of  $V_{GS}$ " of a FET in amplifier applications is by the use of a Resistance in the Source. This resistance is called \_\_\_\_\_
7. Other than the use of two bias methods namely "fixing of  $V_{GS}$ " OR "use of  $R_S$ " list / indicate two other techniques of BIASING an FET
  1. \_\_\_\_\_
  2. \_\_\_\_\_
8. The Fourth terminal brought out by almost every manufacturer other than Source(S), Drain (D) and Gate(G) of a FET is designated in the manufacturer's data sheets as the \_\_\_\_\_ or the \_\_\_\_\_ terminal.
9. A Depletion type MOSFET can be operated in both "Enhancement Mode" and "Depletion Mode". State whether this statement is TRUE or FALSE. \_\_\_\_\_
10. Process transconductance parameter determined by the process technology used to fabricate an NMOS can be expressed as \_\_\_\_\_ and is designated as \_\_\_\_\_
11. The value of  $V_{GS}$  at which a sufficient number of mobile electrons accumulate in the channel region is called \_\_\_\_\_ and the region is called the \_\_\_\_\_
12. When biased in \_\_\_\_\_ Region of an NMOS device, it can be used as an Amplifier and the Characteristic  $i_D - V_{DS}$  relationship is expressed as :



13. Draw the Large-Signal Equivalent-Circuit Model of an NMOS device operating in saturation region that can be employed to analyze a practical circuit. Indicate all components of the equivalent circuit and the significant voltages and currents with most appropriate symbol notation.

14. The relationship between  $v_{GS}$ ,  $V_t$  and  $v_{DS}$  to operate an NMOS device in saturation region is

15. In Integrated circuits to maintain a constant zero bias in all the substrate to channel junctions, the substrate is usually connected to the most negative Power Supply in an \_\_\_\_\_ (NMOS /PMOS) and the most positive in a \_\_\_\_\_ (NMOS / PMOS) circuit.

16. As the voltage on the drain is increased, a value is reached at which the pn junction between the drain region and the substrate suffers \_\_\_\_\_ Breakdown (known also as Punch through) and it occurs at voltages ranging from \_\_\_\_\_ V to \_\_\_\_\_ V.

17. Draw the circuit symbol of NMOS and PMOS transistors.

(i) Circuit symbol of NMOS:

(ii) Circuit Symbol of PMOS:

18. Match the following process parameters shown under I with their dimensions / units shown under II ...by indicating the serial no. of I in the braces: “[ ]” of II.

I	II
A. $C_{ox}$	$V^{-1/2}$ [     ]
B. $K'_n$	$V/m$ [     ]
C. $V'_A$	$F/m^2$ [     ]
D. $\lambda$	$A/m^2$ [     ]
E. $\gamma$	$V^{-1}$ [     ]

19. The characteristic equation representing the “load line” of a CS Amplifier can be mathematically expressed as a relationship between  $i_D$ ,  $V_{DD}$ ,  $R_D$  and  $v_{DS}$  and it is given by:


20. In the following two non-linear transistor biasing circuits, the resistors  $R_A$  and  $R_B$  are suitably employed to provide appropriate compensation against Bias Point drift, then, choose and indicate the most appropriate choice of the nature of resistors : [     ]
- $R_A$  and  $R_B$ , both have negative temperature coefficient
  - $R_A$  and  $R_B$ , both have positive temperature coefficient
  - $R_A$  has negative temperature coefficient and  $R_B$  has positive temperature coefficient
  - $R_A$  has positive temperature coefficient and  $R_B$  has negative temperature coefficient
21. The Gain Bandwidth product of an FET amplifier is \_\_\_\_\_
22. In the MOSFET shown below, the signal outputs  $V_1$  and  $V_2$  obey the relationship [     ]
- $V_1 = V_2/2$
  - $V_1 = -(V_2/2)$
  - $V_1 = 2V_2$
  - $V_1 = -2V_2$
23. A two stage amplifier is required to have an upper cut off frequency of 2 MHz and a lower cutoff frequency of 30 Hz. The upper and lower cutoff frequencies of the individual, but identical, stages are [     ]
- 4 MHz, 60 Hz
  - 3 MHz, 20 Hz
  - 3 MHz, 60 Hz
  - 4 MHz, 20 Hz
24. The threshold voltage of an n-channel MOSFET can be increased by [     ]
- Increasing the channel doping concentration
  - Reducing the channel length
  - Reducing the gate oxide thickness
  - Decreasing the channel doping concentration
25. A source follower using an FET usually has a voltage gain which is [     ]
- greater than +100
  - slightly less than unity but positive
  - exactly unity but negative
  - about -10

26. The MOSFET if designed to operate as an "electronic switch", in its own state may be considered equivalent to [     ]
- Resistor
  - Inductor
  - Capacitor
  - Battery
27. A properly biased JFET will act as a [     ]
- Current controlled current source
  - Voltage controlled voltage source
  - Voltage controlled current source
  - Current controlled voltage source
28. When source terminal is not connected to the body terminal of a FET, the expression for body transconductance  $g_{mb}$ , involves a parameter " $\chi$ ". Employing it,  $g_m$  and  $g_{mb}$  are related as \_\_\_\_\_ . The Expression for " $\chi$ " = \_\_\_\_\_ and typically it varies in the range from \_\_\_\_\_ to \_\_\_\_\_ .
29. The figure of merit of an amplifier " $f_T$ " of an FET can be expressed as :

$$f_T =$$

The physical significance of  $f_T$  of an FET w.r.t. its use in the \_\_\_\_\_ FET model in designing of amplifiers is: \_\_\_\_\_

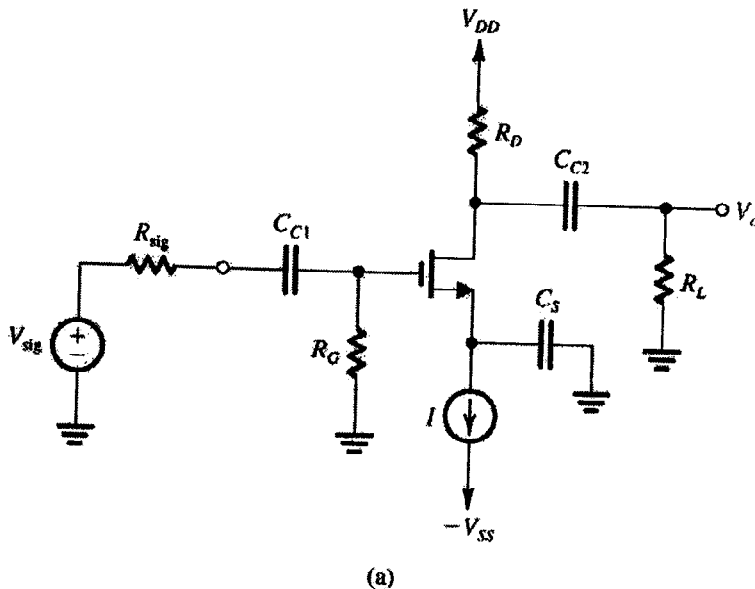30. The mid band voltage gain of the amplifier shown below is \_\_\_\_\_ if  $R_{sig} = 100 \text{ k}\Omega$ ;  $R_G = 4.7 \text{ M}\Omega$ ;  $R_D = R_L = 15 \text{ k}\Omega$ ;  $g_m = 1 \text{ mA/V}$  and  $r_o = 150 \text{ k}\Omega$ ;



\*\*\*\*\* ) ALL THE BEST (\*\*\*\*\*

**BJTS, Pilani – Dubai Campus, Knowledge Village, Dubai**  
 Academic Year 2006-2007 III B.E.(Hons.) I Semester – EEE & EIE  
 Course No. EEE UC 424 / INSTR UC 313 Microelectronic Circuits

Test-1 (Make-up) – Closed Book

Date : 12-10-2006  
 Duration : 50 mts.

Max. Marks : 20  
 Weightage : 20%

**Note** :- 1. Answer ALL Questions  
 2. Indicate explicitly the assumptions, if any, made by you.

1)

Consider a transistor amplifier with its transfer characteristics defined as:  $v_o = 10 \cdot 10^{-11} e^{40v_i}$  which applies for  $v_i > 0V$  and  $v_o > 0.3V$ . Find the value of the dc bias voltage  $V_i$  that results in  $V_o = 5V$  and the voltage gain at the corresponding that operating point. Assuming that, to this amplifier a positive input signal of 1mV superimposed on the dc bias voltage ( $v_i$ ) has been applied, find the corresponding signal at the output for the following two situations, assuming:


- A. the amplifier is linear around the operating point;
- B. the applied input signal is (i) 5 mV and (ii) 10 mV

(1+1+1+2= 5 Marks)

2)

Model the 3-stage amplifier shown below (without the source and load) using the voltage amplifier model. What are the values of the input resistance ( $R_i$ ), open circuit voltage gain ( $A_{vo}$ ) and the output resistance ( $R_o$ ). If  $R_L$  varies in the range  $10\Omega$  to  $1000\Omega$ , find the corresponding range of overall voltage gain ( $v_o/v_s$ ).

(1+1+1+2 =5 Marks)

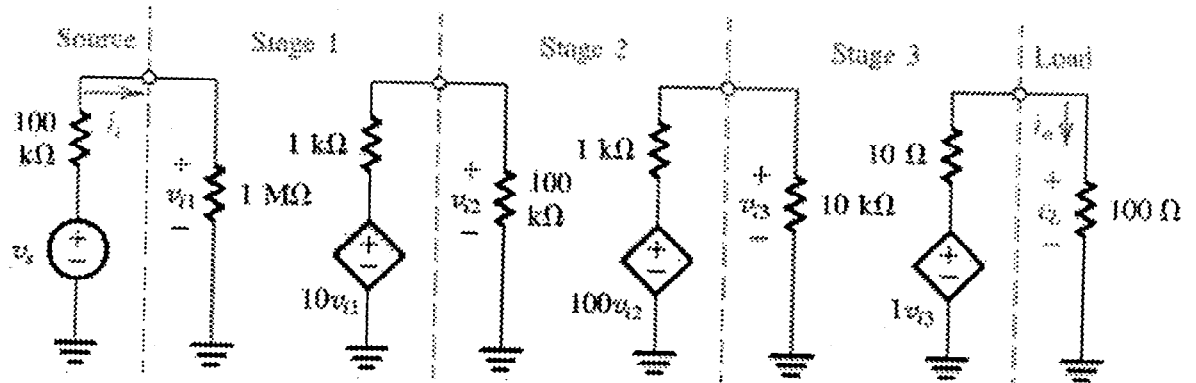

3) A pnp BJT is biased to operate at  $I_C = 2.0\text{mA}$ . What is the associated value of  $g_m$ ? If  $\beta = 50$ , what is the value of the small signal resistance seen looking into the emitter ( $r_e$ )? Into the base ( $r_\pi$ )? If the collector is connected to  $5\text{k}\Omega$  load with a signal of 5-mV peak applied between base and emitter, what output signal voltage results?

(1+1+1+1 = 4 Marks)

4) An amplifier is measured to have  $R_i = 10\text{K}\Omega$ ,  $A_{vo} = 100$ , and  $R_o = 100\Omega$ . Also, when a load resistance  $R_L$  of  $1\text{K}\Omega$  is connected between the output terminals, the input resistance is found to decrease to  $8\text{K}\Omega$ . If the amplifier is fed with a signal source having an internal resistance of  $2\text{k}\Omega$ , find Short circuit transconductance ( $G_m$ ), Voltage Gain ( $A_v$ ), Open circuit-overall voltage gain ( $G_{vo}$ ), Overall Voltage gain ( $G_v$ ), Output Resistance ( $R_{out}$ ) and Current gain ( $A_i$ )

(1+1+1+1+1+1=6Marks)


=====) B E S T O F L U C K (=====

**BITS, PILANI – DUBAI CAMPUS, KNOWLEDGE VILLAGE, DUBAI**  
**FIRST SEMESTER 2006 – 2007**  
**EEEUC424 MICRO ELECTRONIC CIRCUITS**  
**TEST 1(CLOSED BOOK)**

**MAXIMUM MARKS: 20**  
**DATE: 01/10/06**

**WEIGHTAGE: 20%**  
**DURATION: 50 MINUTES**

 1. Evaluate the overall gain, current gain and power gain of the amplifier shown below. [5 marks]



2. (a) Draw the equivalent circuit of a common emitter amplifier with a resistance in the emitter. [1 mark]  
 (b) Derive the expressions for  $R_i$ ,  $A_v$ ,  $R_o$  and  $A_i$ . [4 marks]
3. A common base amplifier biased at an emitter current of 3mA employs a base resistor  $R_B=2K\Omega$  ohm with  $R_C= 3K\Omega$ ,  $R_E=3K\Omega$  and  $R_L = 1K\Omega$ . For  $\beta=150$ , what is the input resistance. What is the voltage gain from a 100  $\Omega$  source? [5 marks]
4. Analyze the circuit shown below to find all node voltages and branch currents. Assume that  $\beta$  is specified to be 50. [5 marks]

