

BITS PILANI DUBAI CAMPUS
DUBAI INTERNATIONAL ACADEMIC CITY, DUBAI
I SEMESTER 2012-2013


COMPREHENSIVE EXAMINATION

COURSE : **CS C391 Digital Electronics and Computer Organization**
 DURATION : **3 HOURS III YEAR**
 WEIGHTAGE : **40% (80 Marks)**
 Date : **08-01-2013 FN**


Calculators are not allowed

- 1a) Subtract 176 from 204. Do the work in binary using 2's complement notation.
- 1b) Express the hexadecimal number B73D as an equivalent octal number.
- 1c) Give the Gray-coded equivalent of the hex number 3A7. [3+3+3] M

 - 2a) Draw the truth table for the following logic diagram. [2+4]M



 - 2b) In the logic circuit given below, find the redundant gate, by using K'MAP



3a) Show the circuit of a 5 X 32 decoder constructed with four 3 X 8 decoders and one 2 X 4 decoder. [4 M]

3b) Design a logic circuit for “sum” output of a full adder using only inverters and 2 X 1 MUX [5 M]

4a) A sequential circuit with two D flip-flops A and B, two inputs x and y, and one output z is specified by the following next-state and output equations. [9 M]


$$A(t+1) = x^1y + xB$$

$$B(t+1) = x^1A + xB$$

$$Z = A$$

- Draw the logic diagram of the circuit.
- List the state table for the sequential circuit.
- Draw the corresponding state diagram.

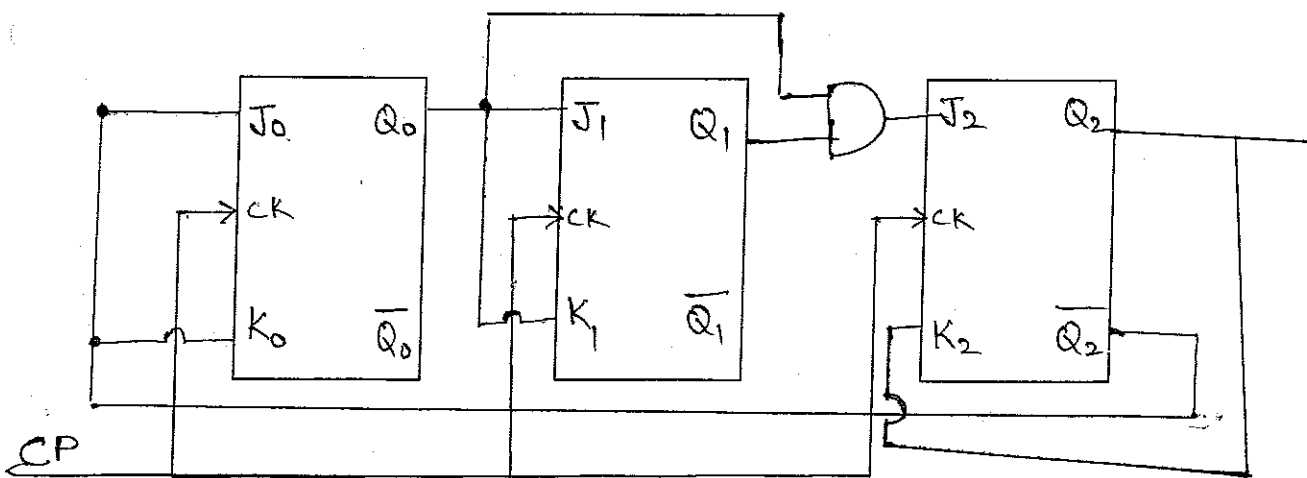4b) For the divide by ‘n’ counter circuit shown below, $J_0=K_0=\overline{Q_2}$; $J_1=K_1=Q_0$; $J_2=Q_0Q_1$; $K_2=Q_2$ write the truth table of the Q_0 , Q_1 and Q_2 after each pulse and find the value of ‘n’. (Assume the initial state of the counter as 000) [5 M]



5a) Draw and explain the design of a 4 bit serial adder. And compare serial adder and parallel adder. [6 + 2 M]

5b) Assuming unused states are driven to don't care states, design a counter with D flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 4, 6, 7. what are self correcting circuits? And how will you make sure the circuit you have designed as self correcting circuit. [6 M]

6a) specify the size of a ROM (number of words and number of bits per word) that will accommodate the truth table for the following combinational circuit components: [4 M]

- 1) A binary multiplier that multiplies two four-bit words
- 2) A 4 bit adder-subtractor.
- 3) A quadruple two to-one-line multiplexer with common select and enable inputs, and
- 4) A BCD-to-seven-segment decoder with an enable input.


6b) It is desired to generate the following three Boolean functions: [5 M]

$$F1 = ab^1c + a^1bc^1 + bc$$

$$F2 = ab^1c + ab + a^1bc^1$$

$$F3 = a^1b^1c^1 + abc + a^1c$$

 By using an OR gate array as shown in figure, where P_1, P_2, P_3, P_4 and P_5 are product terms in one or more of the variables a, a^1, b, b^1, c and c^1 . Find terms P_1, P_2, P_3, P_4 and P_5 .



7a) A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are equal to 1, equal to 0 otherwise. Write a Verilog user-defined primitive for a three bit majority function. [4 M]

7b) Draw the logic diagram of the digital circuit specified by the following Verilog description: [5 M]

```
module Compre_circuit(A,B,C,D,F);  
input A,B,C,D;  
output F;  
wire w, x, y, z, a, d;  
/ and (x, B, C, d);  
/ and (y, a, C);  
/ and (w, z, B);  
/ or (z, y, A);  
or (F, x, w);  
/ not (a, A);  
/ not (d, D);  
endmodule
```

8a) Construct Inverter, NAND gate and NOR gate with n-channel MOS logic circuit. [6 M]

8b) Perform the signed number multiplication for the data -7×11 , using Booth's algorithm. Give the comments on each step. [4 M]

BITS PILANI DUBAI CAMPUS

Dubai International Academic City, Dubai

Year III – Semester I 2012– 2013

Test II (Open Book)

Course No.: CS C391


Course Title: Digital Electronics and Computer Organization

Date: December 13, 2012

Time: 50 Minutes

Max. Marks = 25

 1. For the modified ring counter shown, taking $Q_0=0$, $Q_1=0$ and $Q_2=1$. Make a table of readings Q_0 , Q_1 , Q_2 , J_2 and K_2 after each clock pulse. How many pulses are required before the system begins to operate as a divide-by N counter [5M]



2. Implement the function

$$F(A, B, C, D) = \sum (1,4,5,7,9,12,13) \text{ using } 4 \times 1 \text{ MUX. Choose}$$


Case 1) AB as selection line and

Case 2) CD as selection line

and find which design gives less hardware

[8 M]

 3. The fig. shown below is a Serial in and Parallel out 4 bit **shift right** register, which is initially loaded with 1000 show all the sequence of pattern that will be generated in this circuit. [4 M]



4. Design a counter using T flip flop with the following repeated binary sequence: 0,1,2,3,4,5,6. And check whether the circuit is self correcting. [8 M]

ALL THE BEST

BITS PILANI DUBAI CAMPUS

Dubai International Academic City, Dubai

Year III – Semester I 2012– 2013

Test I (closed Book)

Course No.: CS C391


Course Title: Digital Electronics and Computer Organization

Date: October 21, 2012

Time: 50 Minutes

Max. Marks = 25

 1. Draw a logic circuit which will convert the given 4 bit GRAY code into its equivalent Binary code. [4M]
2. In a digital circuit, output is 1 if and only if the majority of the inputs are 1. The output is zero otherwise, obtain the truth table of a 3 input majority function and implement the function obtained using only 4 NAND gates. [4M]
3. Design a 4 bit parallel full adder without any initial carry using only half adders and OR gates. [4M]
4. Implement the Boolean function $f = AB + C$ using only 2-input NOR gates and what is the minimum number of NOR gates required. [4M]
5. Write the Boolean expression for the shaded area. [4M]



6. Formulate a weighted binary code for the decimal digits using weights 6,4,2,1. [2M]
7. The state of a 12-bit register is 100010010111. What is its content if it represents
 - a) three decimal digits in BCD
 - b) three decimal digits in excess three code
 - c) a binary number. [3M]

.....
ALL THE BEST

NAME:-----ID NO:-----

BITS PILANI DUBAI CAMPUS

SET B

Dubai International Academic city, Dubai

Year III – Semester I 2012 – 2013

Quiz II (Closed Book)

Course No: CS C391

Course Title: Digital Electronics and Computer Organization


Date: 27-11-12

Time: 20 Minutes


Max. Marks = 10

1. Consider the following J-K flip flop, $J = \bar{Q}$ and $K=1$. Assume that the flip flop was initially set and then clocked for 6 pulses. What is the sequence at the output?

[3 M]

 

 2. Find the function $F(A, B, C)$ implemented using the following circuit. [3 M]



3. Given the following state table of a Mealy model sequential circuit with one input x , one output z and four states A, B, C and D, draw the state diagram. [2 M]

S(t)	S(t+1), z	
	X=0	X=1
A	B,0	A,1
B	B,1	C,0
C	D,0	A,0
D	B,0	C,1

4. Construct a JK flip-flop, using D flip-flop, a 2 X 1 MUX, and an inverter. [3 M]

NAME:-----ID NO:-----

BITS PILANI DUBAI CAMPUS

SET A

Dubai International Academic city, Dubai

Year III – Semester I 2012 – 2013

Quiz I (Closed Book)

Course No: CS C391

Course Title: Digital Electronics and Computer Organization

Date: 09-10-12

Time: 20 Minutes

Max. Marks = 10

1. Convert the gray code 101011 into its binary equivalent. **1M**

2. Minimized expression for the K-Map shown below is **2M**

CD \ AB

1	1	1	1
0	0	0	0
1	0	0	1
1	0	0	1

3. Perform the subtraction $(9)_{10} - (4)_{10}$ in BCD using 10's complement method. **2M**

4. The output of a logic gate is '1' when all its inputs are at logic '0'. The gate is either

----- or -----

1M

5. When signed numbers are used in binary arithmetic, then ----- notation, would have unique representation for zero. **1M**

6. Simplify following $\overline{A + AB + ABC + \overline{BC} + \overline{C}}$ **2M**

7. Define the term fanout in IC family. **1M**