

BITS, PILANI - DUBAI CAMPUS

KNOWLEDGE VILLAGE, DUBAI

III-Year II- Semester 2006- 2007

COMPREHENSIVE EXAMINATION (Closed Book)

COURSE TITLE: ANALOG ELECTRONICS

COURSE NO: INSTR UC364

DURATION: 3 Hours

Date: 21-05-07


MARKS: 60

Weightage: 30%

NOTE:

- i. Answer all Questions.
- ii. Assume any missing data suitably and mention it explicitly
- iii. Answer all parts of question in continuation. Do not leave any blank page in between the answers

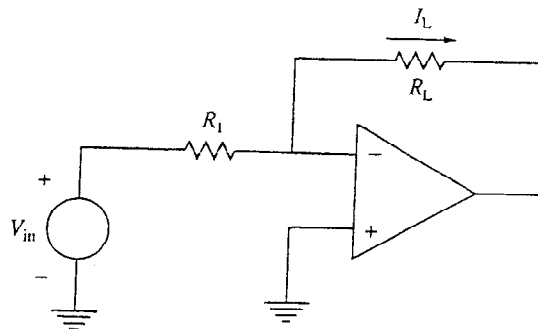- 1) (a) Draw a neat sketch of an isolation amplifier using optical isolation. Explain its working. (4 marks)
- (b) Figure shows a voltage-to-current converter. Given $V_{in} = 2\text{ V}$, $R_1 = 1\text{ k}\Omega$, maximum output voltage of the op-amp, $V_{omax} = \pm 15\text{ V}$, and maximum output current through the op-amp, $I_{omax} = \pm 10\text{ mA}$. Determine
 - (i) maximum value of R_L that can be used and
 - (ii) maximum value of V_{in} that can be used given $R_1 = 1\text{ k}\Omega$ and $R_L = 0\ \Omega$(4 marks)




- 2) (a) Explain the working of a successive approximation register A/D converter with a neat sketch. Take analog input as 10.6 V . Find what is the digital output. Show the full table. (5 marks)
- (b) What is the output of the $R - 2R$ ladder for the input pattern 1010 ? Take $R_F = 3R$ (3 marks)
- 3) What is RTD? Explain with a neat sketch. (3 marks)
- Design a basic temperature sensor using LM335, given dc supply voltage of 5 V . (3 marks)
- 4) Design a second order low pass filter at a high cutoff frequency of 1 kHz . Take

$C_2 = 0.0047 \mu\text{F}$, $R_1 = 27 \text{ k}\Omega$

Draw the frequency response of the network in your answer book (Take $f = 10\text{Hz}$, 200 Hz , 700 Hz , 1 kHz , 3kHz , 10kHz , 100kHz). No need to use semi log sheet or graph sheet. (8 marks)

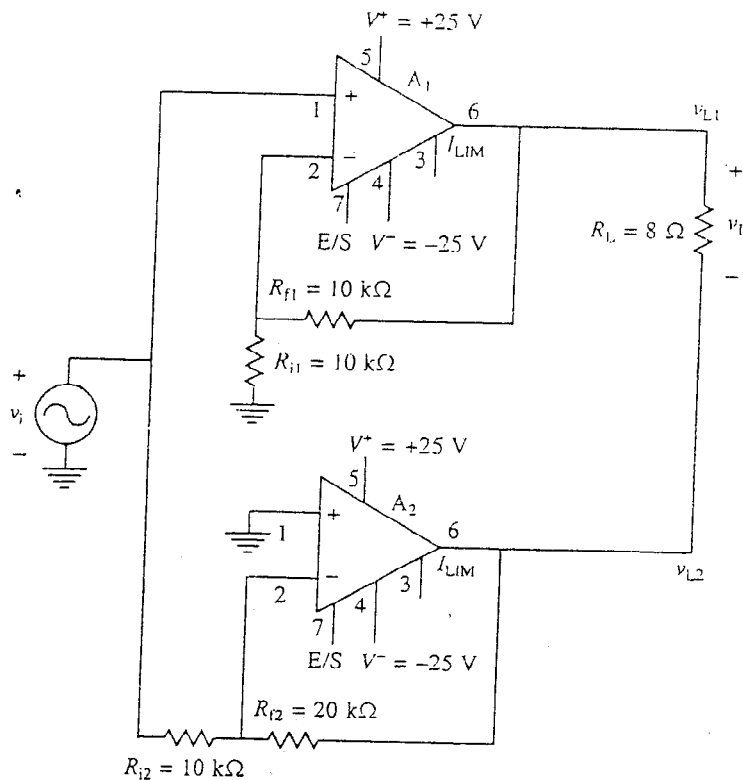- 5) (a) Calculate the values of R_1 and R_3 (given $R_2 = 2.2\text{k}\Omega$) for a high voltage IC723 regulator so as to get an output voltage of 28 V . (4 marks)
 (b) Design a current limit circuit for IC723 regulator to limit the current to 60 mA . (4 marks)
- 6) An inductance of $36 \mu\text{H}$ is resonated with a 1000 pF capacitor. Find f_0 and Q of the resonator if $R_p = 9\text{k}\Omega$ (6 marks)
- 7) The following bridge power amplifier uses OPA 548 op -amp. For a peak sinusoidal input of 10 V peak, find the output voltage, power delivered to the load and peak current drawn from each amplifier. (8 marks)



- 8) Draw a Schmitt trigger circuit. (2 marks)
 (a) If $R_1 = 22 \Omega$, $R_2 = 10 \text{ k}\Omega$ and $V_i = 50(\sin 2\pi * 100t) \text{ mV}$ and op-amp used is 741 op-amp calculate hysteresis voltage. Take $V_{\text{sat}} = \pm 15\text{V}$. (3 marks)
 (b) Explain how this circuit responds to $V_i = 30(\sin 2\pi * 100t) \text{ mV}$ (3 marks)

BITS, PILANI - DUBAI CAMPUS
KNOWLEDGE VILLAGE, DUBAI
 III-Year II- Semester 2006- 2007
 TEST – II (Open Book)


COURSE NO: INSTR UC364
 TIME: 50 minutes

COURSE TITLE: ANALOG ELECTRONICS
 MARKS: 20 WEIGHTAGE:(10%)

ONLY TEXT BOOK AND CLASS NOTES (NOTE BOOK) ALLOWED


NOTE: (Answer all Questions, Data provided are complete)

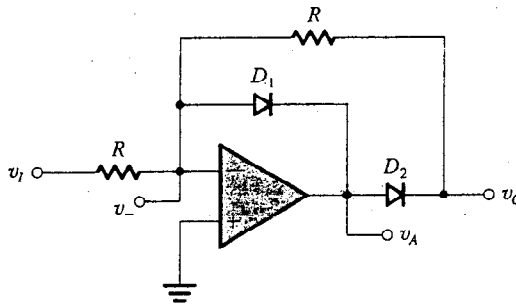- 1) The op-amp in the following diagram is ideal with output saturation levels of $\pm 12V$. The diodes exhibit a constant $0.7V$ drop when conducting. Draw the transfer characteristics for this circuit. Find V_- , V_A and V_0 for:
- (a) $V_I = +1V$
 (b) $V_I = -2V$ Explain. [6 marks]




- 2) In a monostable multivibrator circuit(using 555) charging capacitor = $1nF$
- (a) Find the value of R that result in an output pulse of $10\mu s$ duration.
 (b) If the 555 timer used in (a) is powered with $V_{cc} = 15V$ and assuming that V_{TH} can be varied externally (i.e., it need not remain equal to $2/3 V_{cc}$) find it's required value so that the pulse width is increased to $20 \mu s$, with other conditions the same as in (a) [4 marks]
- 3) Design a triangular waveform generator using comparator and integrator so that $f_0 = 2KHz$ and $V_0 = 7V(p-p)$. Supply voltage is $\pm 15V$ and $V_{sat} = 14V$. Take $R_2 = 10K\Omega$, $C_1 = 0.05\mu F$ [3 marks]

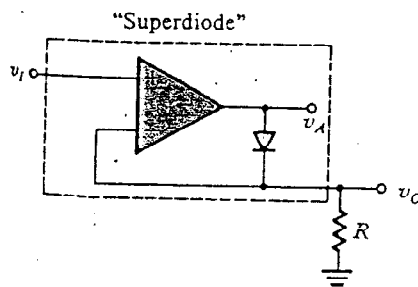- 4) The following circuit can be made to have gain by connecting a resistor R_2 in place of the short circuit between the cathode of the diode and the negative input terminal of the op-amp, and a resistor R_1 between the negative input terminal of the op-amp and ground. Design the circuit for a gain of 2. For a 10V peak -to-peak input sine wave, what is the average output voltage resulting? Draw the output waveform. Mark amplitude and time. [5 marks]



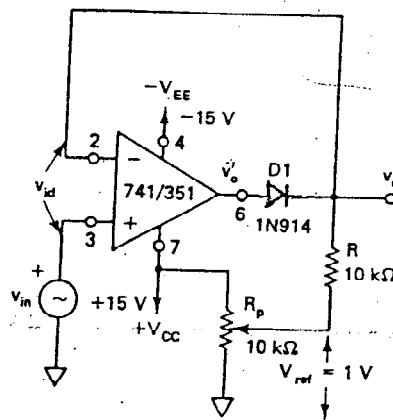- 5) In the following circuit $V_{in} = 2V(\text{peak})$. Draw both input and output waveforms. [2 marks]



BITS, PILANI - DUBAI CAMPUS
KNOWLEDGE VILLAGE, DUBAI
III-Year II- Semester 2006- 2007
TEST – I (Closed Book)


COURSE NO: INSTR UC364
TIME: 50 minutes

COURSE TITLE: ANALOG ELECTRONICS
MARKS: 20 WEIGHTAGE:(10%)

NOTE: (Answer all Questions, Data provided are complete)


- 1) Consider a symmetrical square wave of 20V peak- to - peak, 0 average, and 2ms period applied to an integrator. Find the value of time constant RC such that the triangular waveform at the output has a 20V peak- to – peak amplitude. Sketch input and output waveforms with all voltages marked. [4 marks]

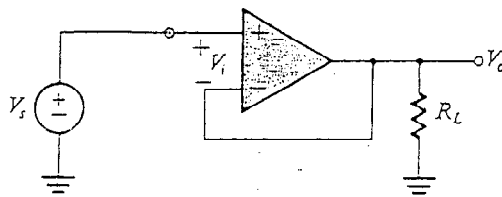- 2) A non - inverting op-amp configuration is shown in figure. Assume that the op-amp has infinite input resistance and zero output resistance. If $A=100$, what is the closed loop voltage gain? What is the amount of feedback in dB? If A decreases by 10%, what is the corresponding decrease in A_f ? (Express it in percentage.) [4 marks]



- 3) Design an inverting op-amp circuit to form the weighted sum V_o of two inputs V_1 and V_2 . It is required that $V_o = -(V_1 + 5V_2)$. Choose values for R_1 , R_2 and R_f so that for a maximum output voltage of 10V the current in the feedback resistor will not exceed 1mA. [4 marks]

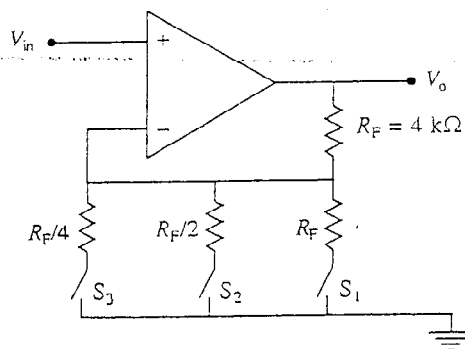- 4) In the following circuit $V_{in} = .1V$. Calculate the gain of the amplifier for all the combinations of the switch. [4 marks]



- 5) A 1V battery with an internal resistance of 5 ohms is to be connected to a load of 20 ohms. Calculate the voltage across the load. Connect a voltage follower in between the load and battery and again calculate the load voltage. [4 marks]