

*BITS-Pilani Dubai, International Academic City, Dubai*

II sem : Year:2007-2008

Evaluation Component : Comprehensive examination (Closed Book)

III Year EIE

EEE UC 364 ANALOG ELECTRONICS

Date: 22<sup>ND</sup> May. 2008

Duration: 3hrs

Max. Marks: 60

Weightage: 30%

Instructions:


Assume suitable data if required

I Answer All Questions (5x2=10)


- 1 Design an OPAMP inverting amplifier with gain 1000.
- 2 Design an active OPAMP filter for passing frequency upto 5Khz.
- 3 Design OPAMP logarithmic amplifier.
- 4 Design an OPAMP circuit to convert square wave into spike.s
5. What is staggered tuned amplifier? Write its advantage.

II Answer All Questions (5x4=20)

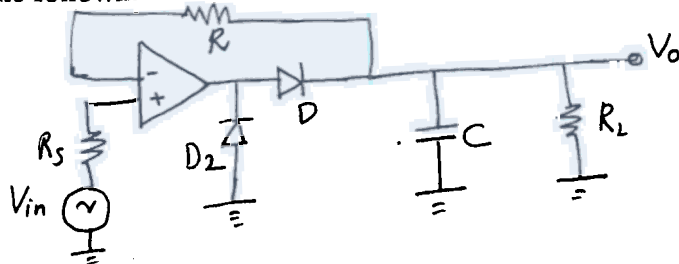6. Design an OPAMP circuit for  $V_o = V_x \cdot V_y \cdot \sin^2 wt$
7. Explain the operation of the following circuit



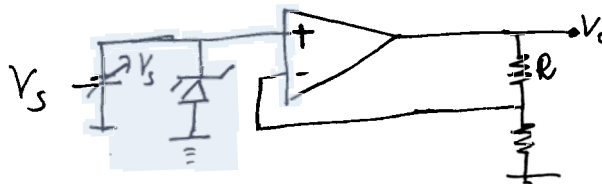8. Explain the operation of circuit given below




9. Design a Zener diode tester circuit using opamp
10. Explain in detail about successive approximation method of converting analog to digital signal

P.T.O

III Answer All Questions (5x6=30)

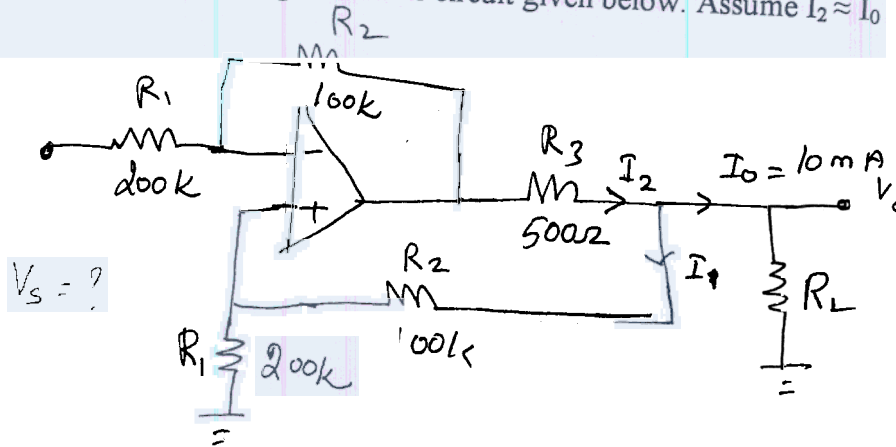11. Find out input voltage  $V_s$  in the circuit given below. Assume  $I_2 \approx I_0$




12. Design an analog circuit using 741 ICs to solve the following differential equation by integrator and summation. Assume all initial conditions to be zero

$$A \frac{d^2 V_o}{dt^2} + B \frac{dV_o}{dt} + CV_o = V_i$$

13. Design an OPAMP RC phase shift oscillator for generating 100 Hz sinusoidal signal. Assume the capacitor value to be  $0.1\mu F$

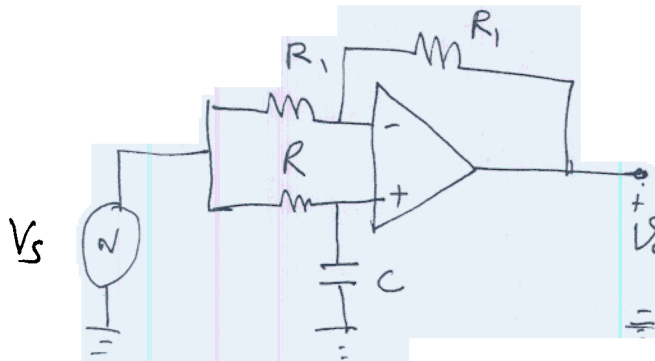14. Design the given opamp circuit to produce the phase shift of  $-135^\circ$  at frequency of 2 kHz. Assume the capacitor value to be  $0.1\mu F$ .



15. Propose your own IC sensor for measuring current passing in the network without any changes in the connection of the circuit.

**BITS-Pilani Dubai, International Academic City, Dubai**  
**III YEAR EIE**

Evaluation Component : **TEST-II(Open Book)**  
**INSTR UC 364 ANALOG ELECTRONICS**


Date : 10<sup>th</sup> Apr. 2008  
 Duration: 50 mts

Max. Marks: 20  
 Weightage: 10%


- Note:-
1. ANSWER ALL QUESTIONS
  2. Make assumptions, if any, but explicitly indicate the assumptions made
  3. **TEXT BOOK ONLY ALLOWED**

Combine low pass and high pass filter to construct band pass filter. Analyze the condition required for it [3 M]

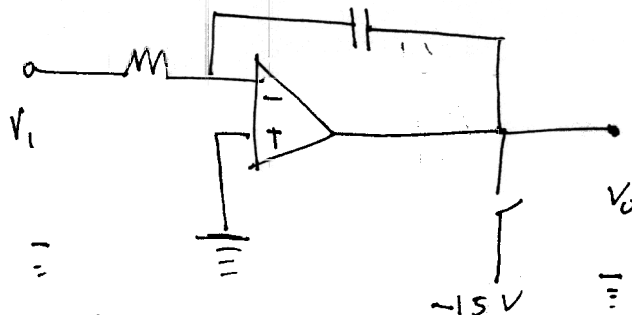2. The operational amplifier shown is used as an integrator. Assume that the capacitor is charged to +15V. It is to be changed to -15 V by closing the switch 'S'. This blows out the opamp. Explain Why and give the way to avoid this. [3M]



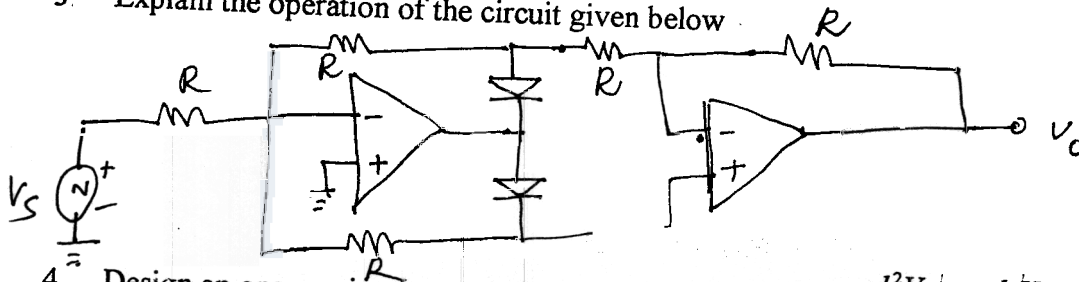3. Explain the operation of the circuit given below



4. Design an opamp circuit to solve the differential equation  $A \frac{d^2V}{dt^2} + B \frac{dV}{dt} + CV_0 = V_i$ , where A B and C are the constants. Use only integrator and summing amplifier. [4M]

5. Design an operational amplifier circuit to find the cube root of give signal

6. The inputs  $V_x = 4.47 \sin(2\pi \times 1000t)$  and  $V_y = 4.47 \sin(2\pi \times 1000t + \theta)$  S are given to multiplier. If a dc voltmeter pf (0-1)V is connected to the output, find the meter readings at  $\theta = 30^\circ, 60^\circ, 90^\circ$ . [3M]


**INSTR UC 364 ANALOG ELECTRONICS**

**Date : 24<sup>th</sup> Feb. 2008**  
**Duration: 50 mts**


**Max. Marks: 30**  
**Weightage: 10%**

- Note:-
1. ANSWER any 6 QUESTIONS
  2. Make assumptions, if any, but explicitly indicate the assumptions made
  3. Write all necessary s-teps for solving problems

- 1 a) Prove that  $|V_o| = (V_s/2)(\Delta R/R)$  in the following bridge circuit having changes in resistance due to strain gauge (2.5 M)

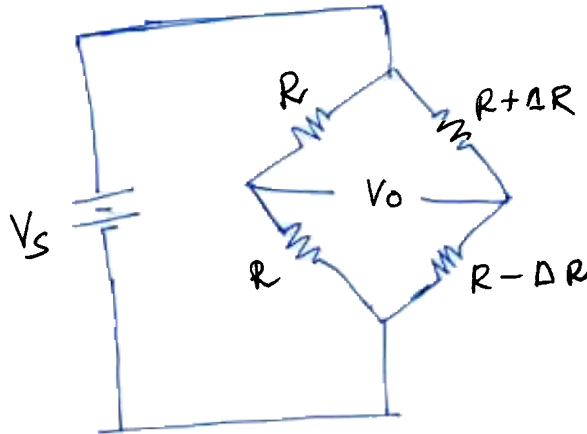

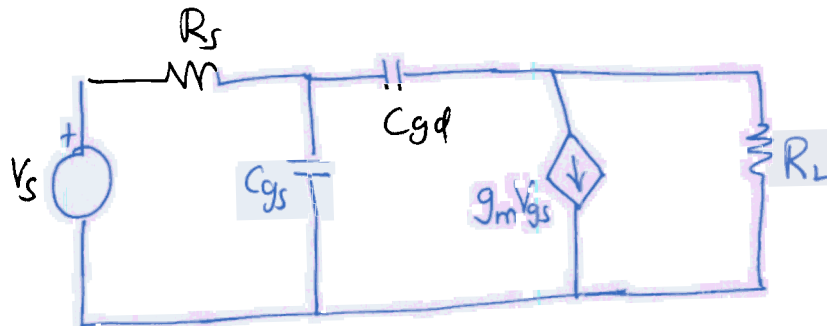
- b) Consider FET amplifier equivalent circuit as shown in figure. Given  $C_{gs} = C_{gd} = 1$  pF,  $g_m = 4$  mA/V,  $R_f = 10$  kΩ. Find the values of the effective input and output capacitances, using miller's theorem (2.5M)




2. Consider a CS amplifier circuit with feedback biasing arrangement as shown in figure. Given  $V_{DD} = 15$  V,  $R_f = 1$  MΩ,  $R_d = 4$  KΩ,  $k'n = 20$  μA/V,  $L = 10$  μ meter,  $W = 400$  μ meter,  $V_a = 100$  V and  $V_t = 2$  V. Assume all capacitors as short at the given signal frequency. Determine the dc operating point and the performance parameters of the voltage amplifier .

(5.0 M)


(PTO)

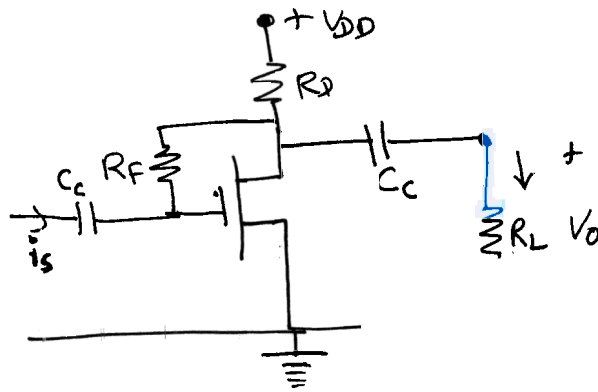

- 3 a) Draw operational amplifier internal block diagram and write their function (2.5M)  
 b) Write the characteristics of an ideal OPAMP (2.5M)
- 4 a) Draw the transfer characteristics of operational amplifier under open loop condition.  
 When does operational amplifier operate in linear mode (2.5M)  
 b) Write the significance of CMRR in operational amplifier (2.5M)
- 5 Find  $V_o$  for the circuit given (5.0M)

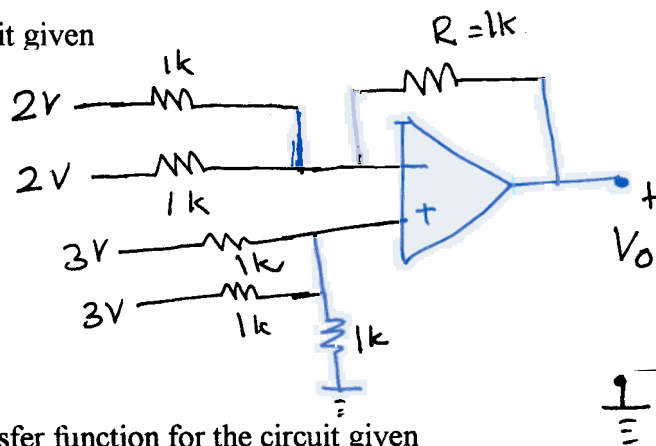

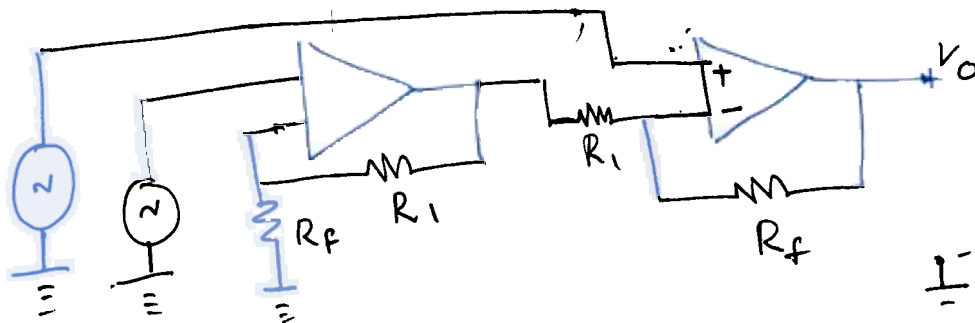- 6 Find the voltage transfer function for the circuit given (5.0M)



- 7 Write all conditions to make inverting amplifier as a summer  
 Write how to convert a summer into an inverting amplifier having gain N (5.0M)