

**BITS PILANI, DUBAI CAMPUS**  
**II SEMESTER 2011 – 2012**

Course Code: EEE C391  
 Course Title: DECO  
 Duration: 50 minutes

TEST-2 (Open Book)


Date: 06.05.2012  
 Max.Marks:25  
 Weightage: 12.5%

**Instructions:** 1. ANSWER all questions in sequence of their order.  
 2. Make assumptions, if any, but explicitly indicate the assumptions made

1. A sequential circuit has two JK flip flops and one input x and one output S. The circuit is described by following flip flop input equations  $J_A = x$ ,  $K_A = B'$ ,  $J_B = x$  and  $K_B = A$  and the output  $S = A'B$
- i) Draw the circuit diagram. 2 + 2  
 ii) Derive the state equations  $A(t+1)$  and  $B(t+1)$ . + 3  
 iii) Draw the state diagram.
2. Design an universal 4 bit shift register using D flip flops whose function table is as shown below. 4

Mode control		Function
0	0	Clear the register
0	1	Load new data
1	0	Shift right
1	1	No Change in data

 3. A three bit up counter is as given below. Modify the circuit to 4
- (i) A down counter with no additional logic gate  
 (ii) An up/down counter using additional EX-OR gates only



4. How many address lines are required to address a 4K x 8 memory? What would be the starting and ending addresses of the Memory? What would be the maximum value of data which can be stored in a memory location. 4
5. Design a full adder using PLA and develop its programming table 6

\*\*\*\*\*

# BITS PILANI, DUBAI CAMPUS

II SEMESTER 2011 – 2012

Course Code: EEE C391/ECE C391

TEST-1

Date: 18.03.2012

Course Title: DECO

Max.Marks:25

Duration: 50 minutes

Weightage: 12.5%

- Instructions:**
1. ANSWER all questions in sequence of their order.
  2. Make assumptions, if any, but explicitly indicate the assumptions made
  3. Calculators are not allowed

1. Find the following by direct conversion 2+1+2
  - a)  $(132 \frac{37}{64})_{10} = (\text{_____})_2$
  - b)  $(11100.010101)_2 = (\text{_____})_H$
  - c) Compute  $(783)_H - (78)_H$  using 16's complement
  
2. Implement the following function 2+2  
 $F(A, B, C) = AB'C' + A'BC' + ABC + A'B'C + A(B'C' + BC)$  using two level EX- OR logic gates only.
  
3. Draw and explain a 4-bit binary word adder circuit using full adders. Modify the circuit to perform addition or subtraction using additional external logic gates. Explain the logic of your design. 2+1+1
  
4. Simplify the following function  $F(A, B, C, D)$  along with the don't care condition  $d(A, B, C, D)$  2+1+1+2  
 $F(A, B, C, D) = \sum(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$ .  
Identify prime implicants and essential prime implicants.  
Implement the function using minimum no. of NOR gates alone.
  
5. Develop the truth table of the function given below and realize it using only 2 to 4 line active high decoder with active low enable pin and external two input OR gates 2+2+2  
 $f(x, y, z) = xy + xz' + y'z$

\*\*\*\*\*

NAME:

ID NO:

**BITS, PILANI – DUBAI CAMPUS**  
I SEMESTER 2011 – 2012  
III Yr ECE/EEE

Version B

Course Code: **EEE C391/ECE 391**

Quiz-1

Date: **28.02.2012**

Course Title: **Digital Electronics and Computer Organization**

Max Marks: 10

Duration: **20 minutes**

Weightage: 5%

- Instructions:**
1. ANSWER all questions at the space provided.
  2. Make assumptions, if any, but explicitly indicate the assumptions made
  3. All questions except Q2 carry one marks each.
  4. Write on back side if the space is insufficient.

1. Find out the base of number system if  $(101)_b = (37)_{10}$

2. Write SOP expression for the following truth table and prove that  $\bar{Y} = A \oplus B$  (2M)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

3. Prove that  $\overline{AB + BC + AB + BC} = 0$

4. Implement the following function <sup>using</sup> only NAND gates  $Y = AB + \bar{A}\bar{B}$

