

BITS, Pilani – Dubai

International Academic City – Dubai

III year EEE/ EIE, II Semester 2011-12 / Comprehensive Exam.

**Course Title –Power Electronics(EEE C 461/ INSTR C461) Full Marks--
80(Weightage 40%) Duration—3 Hrs. Date-14/06/2012**

(1) In context to “TURN-ON Control of BJT Base Drive”, derive the expression for $i_B(t)$ using Laplace Transform method (with the relevant circuit diagram), starting from fundamentals. Also calculate the time instant at which the base current ($i_B(t)$) becomes 90% of its initial value.

Given data are: (i) $R_1 = 4.0$ ohm (ii) $C_1 = 1.0$ micro farad (iii) Final value of base current is 60% of its initial value ----- [7+5 marks]

(2) (a) In context to the Resonant Commutation of Thyristor(see Fig.1), following conditions are given: (i) Initial voltage across capacitor = V_s volts (ii) Initial current through the inductor = I_1 amps. Applying Laplace Transform method, prove that current through the inductor is given as, $i_L(t) = I_1 \cos(\omega_0 t) - C V_s \omega_0 \sin(\omega_0 t)$ -----where ω_0 represents the resonant frequency in rad./sec. The switch(S) is closed at $t=0$.

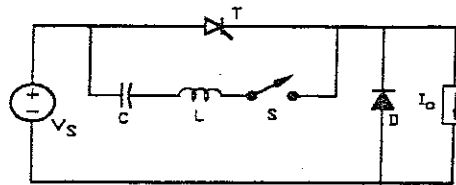


Fig.-1

(b) In connection with Question2(a), calculate the value of the inductor(L) if the Thyristor has a turn-off time of $20 \mu\text{-sec}$. The given data are: $V_s = 215$ volts, Resonant frequency = 18 KHz . and $I_1 = 0$ -----[7+5 marks]

(3) A voltage pulse of height of V_{DD} volts and pulse width of “a” seconds, is injected into the gate of a MOSFET in context to its **“Turn-on” phenomenon**. Following assumptions (changes) and symbols are to be incorporated:

(i) Gate to drain capacitance is realistic and it is equivalent to the parallel combination of ideal capacitor(C_{gd}) and resistor(R_{gd})

(ii) Gate to source capacitance is realistic and it is equivalent to the parallel combination of ideal capacitor(C_{gs}) and resistor(R_{gs})

(iii) $\frac{1}{R} = \frac{1}{R_g} + \frac{1}{R_{gs}} + \frac{1}{R_{gd}}$ (iv) $C = C_{gs} + C_{gd} = \frac{\tau}{R}$

Prove that in Mode-1(using Laplace Transform method),

$$v_{gs}(t) = \frac{RV_{DD}}{R_g} \left\{ \left(1 - e^{-\frac{t}{\tau}}\right) u(t) \right\} - \frac{RV_{DD}}{R_g} \left\{ \left(1 - e^{-\frac{t-a}{\tau}}\right) u(t-a) \right\},$$

where, $u(t)$ and $u(t-a)$ are the Unit Step Function and Shifted Unit Step Function, respectively and $v_{gs}(0) = 0$. -----[12 marks]

(4) A chopper fed D.C series motor is working under regenerative mode. The machine is having following data:

$V_s = 600$ volts; $R_a = 0.02$ ohm; ---

[P.T.O]

$R_f = 0.03 \text{ ohm}$; $K_v = 16.27 \text{ mv/A-rad./sec.}$; $I_a = 265 \text{ A(average)}$
 Duty cycle of the chopper=60% and armature current---continuous.

After deriving the relevant formulae and drawing a suitable circuit diagram for the above said drive system, calculate:

- (i) Average voltage across chopper(V_{ch})
- (ii) Power regenerated to the D.C supply (P_g)
- (iii) Equivalent load resistance of the motor acting as generator
- (iv) The minimum and maximum permissible braking speeds of the motor(in r.p.m)
- (v) Motor speed (in r.p.m)----- [3+1+9 marks]

(5)(a) Draw the labeled circuit diagram and all relevant waveforms of a single phase full converter (controlled rectifier) with a large inductor as load. What is the purpose of using large inductor as load----explain.----- [2+2+1 marks]

(b) In context to question 5(a),calculate b_1, b_3, b_5 (Harmonic coefficients) of input current[$i_s(t)$] after deriving the expression for b_n . Given data are: $I_a = 1.2 \text{ amp}$ ---fixed value ; Firing angle of Thyristor (α)= 20° .----- [3+4 marks]

(6) (a) Draw the labeled circuit diagram of a single phase bridge inverter (V.S.I) and draw the waveform of output voltages (v_{ao}, v_{bo} and v_{ab})-- [1+2 marks]

(b) Develop the "**Switching State Table**" of the inverter in question6(a), with conventions given as: upper switch on--- STATE=1; lower switch on--- STATE=0--[3 marks]

(c) Derive the expression for the harmonic coefficient (b_n) of the output voltage (=voltage across load= v_{ab}) of the above-said inverter, starting from fundamentals.-- [4 marks]

(7) (a) Draw the basic circuit diagram(labeled) of a Buck Converter or Boost Converter-----[2 marks]

(b) Draw the equivalent circuits of Mode-1 and Mode-2 of the above-said converter (corresponding to any one of them) and draw the corresponding relevant waveforms.----- [3 marks]

(c) Prove that $\Delta I = \frac{(V_s - V_a)k}{fL}$ -----for Buck Converter----[4 marks]

OR

Prove that $\Delta I = \frac{(V_s - V_a)(k-1)}{fL}$ -----for Boost Converter

BITS, Pilani – Dubai

International Academic City – Dubai

III year EEE/ EIE, II Semester 2011-12 / Test-2 (OPEN BOOK)

Course Title –Power Electronics(EEE C 461/ INSTR C461)

Full Marks – 20(Weightage 20%) Duration—50 min

Date: 20---05---2012(Only Text book and hand written class notes allowed)

(1) In context to the Antisaturation Control Circuit of BJT Base Drive System , calculate: (i) “ β ” (answer should be in nearest integer value) and (ii) Hence, the collector current magnitude, without clamping. Assume that “ β ” remains same in the cases of “ Without clamping” and “ With clamping”.

The given data are: $V_{CC} = 100.0$ volts , $V_{d1} = 2.1$ volts , $V_{d2} = 0.9$ volts, $V_{BE} = 0.7$ volts, $V_B = 15.0$ volts, $R_B = 2.5$ ohm, $R_C = 1.5$ ohm, Collector current(with clamping) = 67 amps-----[5 marks]

(2) Consider a n-channel MOSFET (TURN ON, Modes 1&2) having the following data:

$V_{DD} = 15.0$ volts, $I_o = 40.0$ amps, $V_T = 3.0$ volts, $C_{gs} = 2600$ picofarad , $C_{gd} = 350$ picofarad, $g_m = 25.0$ siemens, $R_g = 9.0$ ohm . Calculate the following: (a) The time instant at which the current through the clamping diode will be 40% of the load current (b) Duration of Mode-1 (c) Duration of Mode-2 [3+3+2 marks]

(3) In context to the Impulse Commutation of a Thyristor(Fig.1), the capacitor is precharged with a voltage of “ $-V_c$ ” volts. “ $t=0$ ” is counted when the switch(S) is closed. Initial value of current through the inductor is zero. Reverse recovery time (of junction J_2) within the Thyristor structure may be ignored. Prove that the “ Turn-off time(t_{off})” of the Thyristor may be expressed as :

$$t_{off} = \sqrt{LC} \tan^{-1} \left(\frac{V_c \cdot \sqrt{C/L}}{I_0} \right)$$

[7M]

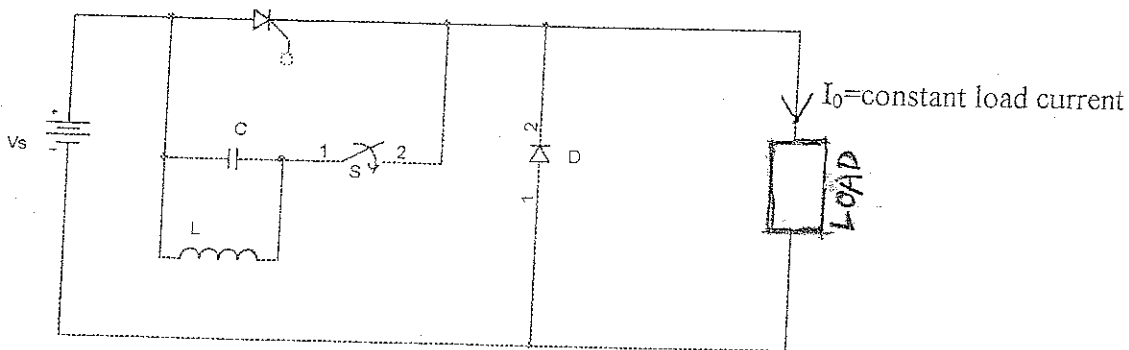


Fig. 1

BITS, Pilani – Dubai
International Academic City – Dubai
III year EEE/ EIE, II Semester 2011-12 / Test-1
Course Title –Power Electronics(EEE C 461/ INSTR C461)
Full Marks – 25 (Weightage 25%) Duration—50 min
Date: 01--04—2012

- (1) (a) Draw the circuit diagram (labeled) of a three phase full-converter using Thyristors, with highly inductive load. Draw also the waveforms of output voltage and input current (phase “a”) of this circuit.---[1+2 marks]
- (b) With reference to Question 1(a), prove that the r.m.s output voltage(V_{rms}) can be expressed as: $(V_{rms})^2 = 3 (V_m)^2 [(1/2) + \{(3\sqrt{3})/(4\pi)\} \cos(2\alpha)]$.
Hence calculate the value of “ α ” when following data are given:
 $V_{rms} = 150$ volts and $v_{an} =$ Input phase “a” voltage = $170 \sin(\omega t)$ —[4+2 marks]
- (2) (a) Draw the circuit diagram (labeled) of a single phase semi-converter using Thyristors, with highly inductive load. Also explain why free-wheeling diode is necessary to be included in such circuit.
- (b) Draw the wave form of the current through the free-wheeling diode of the circuit in Question 2(a) and hence derive the expression for the Harmonic Coefficient, “ b_n ” and “dc component” of this current.-- [1+2+1+4+2]
- (3) The output voltage of a single phase full wave bridge rectifier circuit has been expressed as $v_o(t) = (2V_m/\pi) + (4V_m/\pi) \sum [\{(-1)/(n+1) (n-1)\} \cos(n\omega t)]$ -----for $n=2,4,6,8$ -----. The input to the rectifier is a 120 volts(rms), 50 Hz. source. Load resistance is 500 ohms. Design a series inductor, “L” that limits the RMS ripple current, I_{ac} to less than 5% of I_{dc}
-----[6 marks]

#-----#-----END-----#-----

BITS, Pilani – Dubai **[Set—A]**
International Academic City – Dubai
III year EEE/ EIE, II Semester 2011-12 / Quiz-2/ Set--A
Course Title –Power Electronics(EEE C 461/ INSTR C461)
Full Marks – 14 (Weightage 07%) Duration—20 min
Date: 02--05—2012/ Name----- Id No.-----

(1) Draw a labeled Two-Transistor Model Diagram of a Thyristor. [3 marks]

(2) Draw a labeled circuit diagram of “ANTISATURATION CONTROL” of BJT Base Drive System.-----[3 marks]

(3) “ In context to a Thyristor, Latching Current is of lesser value as compared to that of Holding Current”---Statement—FALSE/TRUE?---[1 mark]

(4) What are the differences between “Resonant Commutation” and “ Impulse Commutation” methods of Thyristor?---Mention any two points.-- [3 marks]

[P.T.O]

Name-----Id No.-----

[Set-A]

(5) In the case of Impulse Commutation of Thyristor, given data are :
Device Turn-off time = 20 μ -sec; Constant load current = 50 amp., Initial voltage across Capacitor = -169 volts. Calculate the value of the capacitor (assuming linear charging)--- [2 marks]

(6) In the case of "Turn-On Control of BJT Base Drive System (given circuit diagram in Fig.1)", given data are: $V_1 = 15$ volts, $V_{BE} = 0.7$ volts, $R_1 = 2.5$ ohms , $R_2 = 2.0$ ohms. Calculate final value of Base Current.--- [2 marks]

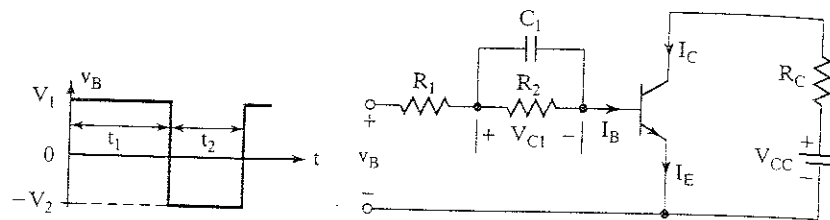


FIGURE 1

-----END-----

-----END-----

BITS, Pilani – Dubai

[Part—A]

International Academic City – Dubai


III year EEE/ EIE, II Semester 2011-12 / Quiz-1/ Part--A

Course Title –Power Electronics(EEE C 461/ INSTR C461)

Full Marks – 08 (Weightage 08%) Duration—20 min

Date: 13--03—2012/ Name----- Id No.-----

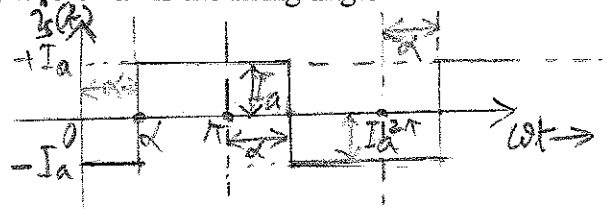- (1) One Harmonic (Fourier) Coefficient is given as $a_n = (4V_m / \pi) [(-1)/(n+1)(n-1)]$ The corresponding Power Electronic hardware will be:
- (a) A full wave bridge rectifier using Thyristor (b) A half-wave rectifier using Thyristor (c) A full bridge rectifier using Diode----[1 mark]
- (2) With reference to the following waveform for an input current of a power electronic circuit , prove that (after doing Harmonic Analysis) :
- $b_n = (4I_a / n\pi) \cos(n\alpha)$ ----for $n=1,3,5,7$ ----, where “ α ” is the firing angle of the Thyristor.-----[4 marks]



[P.T.O]

Part-A

Name-----Id No.-----

(3) The output voltage of a particular power electronic converter circuit (with R-L load) has been expressed as $v_o(t) = (2V_m/\pi) + (4V_m/\pi) \sum [(-1)^{n+1} / (n-1)] \cos(n\omega t)$ -----for $n=2,4,6,8$ ----. Prove that the R.M.S value expression of the dominant A.C Component (Harmonic) of the output current will be :

$$I_{a.c, dominant} = [(4V_m/\pi)(1/\sqrt{2})(1/3)] [1/\{R^2 + 4\omega^2 L^2\}^{0.5}] \text{-----}[2 \text{ marks}]$$

(4) Out of the following, is which expression correct?---for a power electronic system:-----[1 mark]

(a) $PF = (I_{s1}/I_s) [1/(DPF)]$ (b) $PF = (I_{s1}/I_s) (DPF)$ (c) $PF = (I_s/I_{s1}) [1/(DPF)]$

-----*-----*