

**BITS, PILANI - DUBAI CAMPUS**  
**KNOWLEDGE VILLAGE, DUBAI**  
 III-Year II- Semester 2003- 2004  
**COMPREHENSIVE EXAMINATION(Closed Book)**  
 COURSE TITLE: ANALOG ELECTRONICS (EEE UC364/ INSTR UC364)

TIME: 3 Hours


Date : 08-06-2004

MARKS: 60

NOTE:

- i. Answer all Questions.
- ii. Assume any missing data suitably
- iii. Answer all parts of question in continuation
- iv. Do not leave any blank page in between the answers

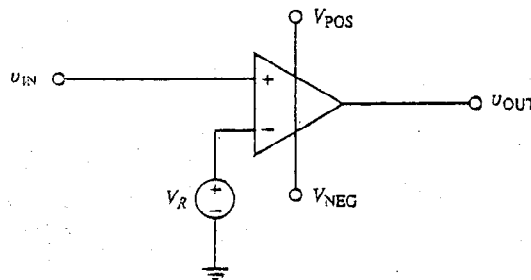- 1) The 741op-amp is connected as an inverting amplifier. The input and feedback resistors values are  $10K\Omega$ , and  $20K\Omega$  respectively. It's input signal is a  $\pm 10V$  peak-to-peak triangular wave and  $V_{sat} = \pm 13V$ . Sketch and label the input( $V_s$ ), the voltage at the inverting terminal( $V_n$ ) and the output voltage( $V_o$ )  $V_s$  time. [6 marks]
  
- 2) A 6-V peak triangular wave is applied to the circuit shown in figure. If the op-amps are powered by  $\pm 12V$  supplies, plot the resulting output for the following cases:
  - (a)  $V_R = 0$
  - (b)  $V_R = +3V$
  - (c)  $V_R = -5V$
 [6 marks]




- 3) A singing group has a lead vocalist and two background musicians. Each sings into one of three microphones, producing an electrical signal with  $10mV$  maximum magnitude. Using the summation amplifier configuration, design an op-amp circuit that mixes the three microphone signals and feeds them to a common output. The lead vocalist's signal is to be amplified by twice the amplification factor of the other two singers. The circuit should be designed so that the op-amp does not saturate even if the maximum peak signal is received simultaneously from all three microphones. The magnetic coil winding


in each microphone contributes a series resistance of  $500\Omega$  and negligible inductance. The available power supply voltages are  $\pm 15V$ . The gain of any one input should not exceed 100 in magnitude. Choose  $R_F$  as  $100K\Omega$  [6 marks]

- 4) Design a wide band-pass filter with  $f_L = 200Hz$ ,  $f_H = 1KHz$  and a pass band gain = 4.  
 (a) Calculate  $R_1$ ,  $R_F$ ,  $R$ ,  $R'$ ,  $R_1'$  and  $R_F'$ .  
 (b) Calculate the value of Q for the filter.  
 (c) Calculate voltage gain in dB for frequencies of input signal (i) 10 Hz (ii) 100 Hz (iii) 200Hz (iv) 447.2 Hz (v) 1000 Hz  
 Take capacitor in LPF section =  $0.01\mu F$  and in HPF section =  $0.05\mu F$ . [6 marks]

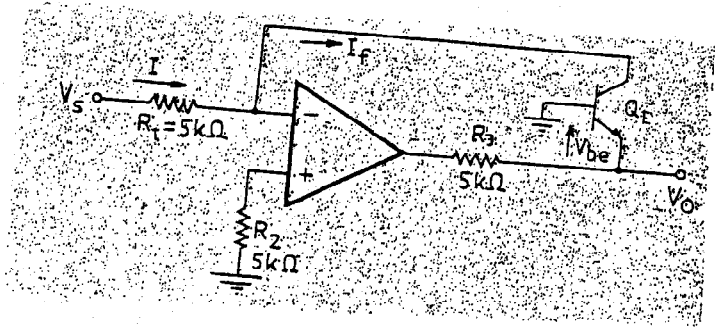- 5) In the circuit shown determine  $V_o$  (in terms of log). Given  $R_1 = 5K\Omega$ , Boltzmann's constant =  $1.38 \times 10^{-23} J/K$ ,  $T = +298^\circ K$  (room temperature) and electron charge =  $1.6 \times 10^{-19} C$ . Neglect reverse saturation current of the transistor. [5 marks]



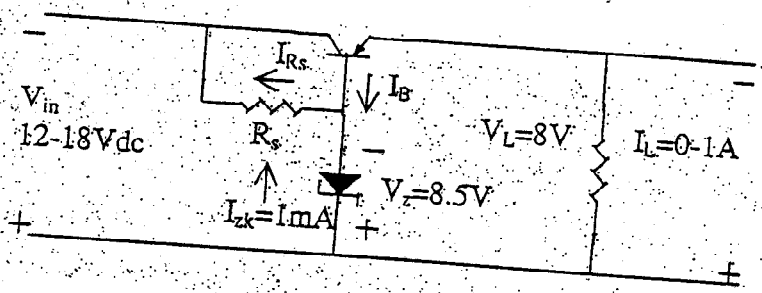- 6) Provide a design of precision rectifier in which the gain is -2 for negative inputs and zero otherwise and the input resistance is  $100K\Omega$ . Draw the circuit with all component values. [5 marks]
- 7) Design a negative voltage regulator as shown in figure.




The load current varies between 0-1mA, and the unregulated dc input varies from 12-18V for all line and load changes. The 8.5V zener diode requires at least 1mA of current to stay in its regulating region ( $I_{zk} = 1\text{mA}$ ). Assume  $h_{FE} = 50$


- (a) Determine the value of  $R_s$  to ensure proper circuit operation
- (b) Determine worst case power dissipation of  $R_s$  & Q1 [6 marks]

8) Design an astable multivibrator using 555, to obtain a square wave with a 50KHz frequency and a 75% duty cycle. Specify the values of  $R_A$  and  $R_B$ . Take value of timing capacitor as 680pF. [5 marks]

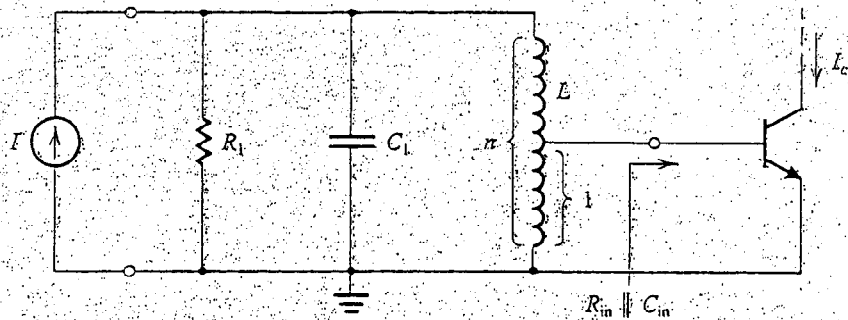9) Consider the circuit shown first without tapping the coil. Let  $L = 5\mu\text{H}$  and assume that  $R_1$  is fixed at  $1\text{K}\Omega$ . Design a tuned amplifier with  $f_o = 455\text{KHz}$  and a 3dB BW of 10KHz. If the BJT has  $R_{in} = 1\text{K}\Omega$  and  $C_{in} = 200\text{pF}$ , find the actual bandwidth obtained and the required value of  $C_1$ . [5 marks]



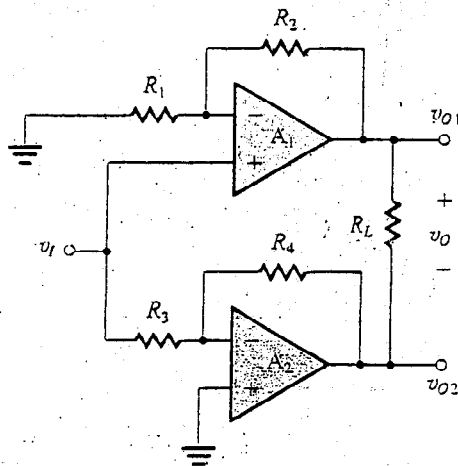10) Consider the circuit shown in figure where  $R_1 = R_3 = 10\text{K}\Omega$ ,  $R_2 = 5\text{K}\Omega$ ,  $R_4 = 15\text{K}\Omega$  and  $R_L = 8\Omega$ . Find the voltage gain and input resistance. The power supply used is  $\pm 18\text{V}$ . If  $V_1$  is a 20V peak-to-peak sine wave, what is the peak-to-peak o/p voltage? What is the peak load current? [5 marks]



- 11) An amplifier operating from a single 15V supply provides a 12V peak - to - peak sine wave signal to a  $1\text{K}\Omega$  load and draws negligible current from the signal source. The DC current drawn from 15V supply is 8mA. What is the power dissipated in the amplifier and what is the amplifier efficiency?

[5 marks]

---

**BITS, PILANI - DUBAI CAMPUS**

**KNOWLEDGE VILLAGE, DUBAI**

**III-Year II- Semester 2003- 2004**

**QUIZ-I (Closed Book)**

**COURSE TITLE: ANALOG ELECTRONICS (EEE UC364/ INSTR UC364)**

**TIME: 30 minutes**  
**NAME:**

**Date : 24-05-2004**

**MARKS: 15**

**ID:**


- 
- 1) Since the closed loop gain is smaller than the open loop gain in a negative feedback circuit, the closed loop cut-off frequency is \_\_\_\_\_ the open loop cut-off frequency
- a) <
  - b) >
  - c) =
  - d) >=
- 2) When a PLL is locked what is the relation between VCO frequency and the input frequency?
- a) <
  - b) >
  - c) =
  - d) >=
- 3) In a wein bridge oscillator the lead-lag network provides \_\_\_\_\_ feedback and the voltage divider provides \_\_\_\_\_ feedback.
- a) +, +
  - b) +, -
  - c) -, +
  - d) -, -
- 4) Negative feedback increases the \_\_\_\_\_ impedance of a non-inverting amplifier.
- a) Input
  - b) Output
  - c) Both input & output
- 5) In the inductor simulation experiment, the op-amp is connected as

- a) An inverting amplifier
- b) A non-inverting amplifier
- c) A voltage follower
- d) Open loop comparator

- 6) The type of feedback in non-inverting op-amp circuits is
- a) Voltage shunt
  - b) Current shunt
  - c) Voltage series
  - d) Current series

7) In 555 timer if  $V_{cc} = +15V$ , trigger voltage must be slightly less than \_\_\_\_\_ V to reset the RS flip-flop.

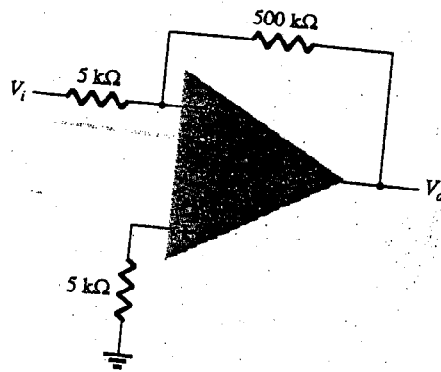
8) What is the total offset voltage for the following circuit for an op-amp with specified values of input offset voltage,  $V_{IO} = 4mV$  and input offset current  $I_{IO} = 150nA$



- a)  $429\mu V$
- b)  $429mV$
- c)  $329mV$
- d)  $479mV$

9) The input \_\_\_\_\_ current is the difference of the two input base currents.

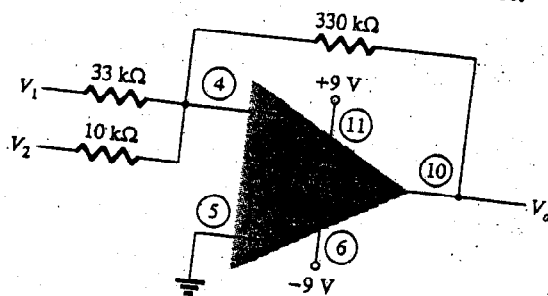10) Calculate the output voltage for the given circuit.



The inputs are

$$V_1 = 50\text{mv} \sin(1000t) \text{ and}$$

$$V_2 = 10\text{mv} \sin(3000t)$$

- 11) If the diode offset voltage is 0.7V and an op-amp has a voltage gain of 100,000 the effective offset voltage is \_\_\_\_\_
- 12) Well above cut-off a second order active low pass filter has voltage gain that decreases \_\_\_\_\_ dB/octave, equivalent to \_\_\_\_\_ dB/decade.
- 13) What is the cause of slew rate?
- 14) What is the physical significance of an input offset current of 15nA?
- 15) An amplifier with a gain of 10 gives 2vp-p sine wave output. If the input is lifted up by adding 2v DC to it what will be the output?

**BITS, PILANI - DUBAI CAMPUS**  
**KNOWLEDGE VILLAGE, DUBAI**

III-Year II- Semester 2003- 2004

TEST II(Open Book)

COURSE TITLE: ANALOG ELECTRONICS (EEE UC364/ INSTR UC364)

TIME: 50 minutes

Date : 02-05-2004


MARKS: 30(=10%)

NOTE:

- i. Only Class notes and EDD notes are allowed
- ii. Answer all Questions.
- iii. Assume any missing data suitably
- iv. Answer all parts of question in continuation
- v. Do not leave any blank page in between the answers


1) A zener shunt regulator utilizes a zener diode whose voltage is 5.1 at a current of 100mA and whose incremental resistance is  $7\Omega$ . The diode is fed from a supply of 15V nominal voltage through a  $100\Omega$  resistor. What is the output voltage at no load? Find the line regulation and load regulation. [5 marks]

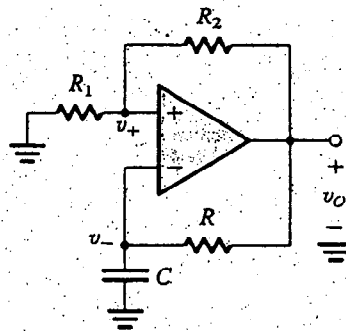2) In the circuit shown  $R_1$  is replaced by a pair of diodes connected in parallel in opposite directions.



For  $V_{sat} = 12V$ ,  $R_2 = R = 10K\Omega$ ,  $C = 1\mu F$  and the diode voltage a constant denoted  $V_D$ , find an expression for frequency as a function of  $V_D$ . If  $V_D = 0.7V$  at  $25^\circ C$  with a temperature coefficient(TC) of  $-2mv/^\circ C$ , find the frequency at  $25^\circ C$ . [4 marks]

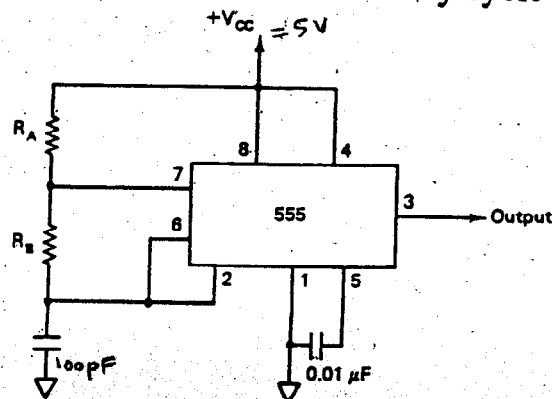
3) In the following circuit find the values of  $R_A$  and  $R_B$  that result in an oscillation frequency of 100KHz and a duty cycle of 75%. [5 marks]





- 4) In the circuit shown  $R_1 = 1K\Omega$ ,  $R_2 = 10K\Omega$ . Find  $V_o$  and the voltage at the amplifier output for  $V_i = +1V$  &  $-10mV$ . Explain the working for both cases. Assume the op-amp to be ideal with saturation voltages of  $\pm 12V$ . The diodes have  $0.7V$  voltage drop at  $1mA$  and the voltage drop changes by  $0.1V$  per decade of current change.

[5 marks]

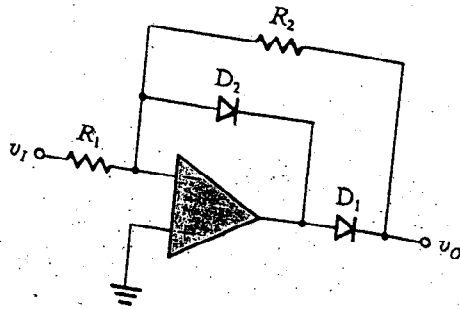


- 5) What is the maximum resistor ratio required by a 12-bit D/A converter utilizing a binary weighted ladder.

[2 marks]

- 6) Design a timer circuit using 555 device that operates with a  $15V$  supply and turns on an LED (Light Emitting Diode) for a duration of approximately  $10ms$  every time it receives a negative trigger pulse. The LED requires about  $20mA$  of operating current and forward voltage drop  $V_f$  of  $1.4V$ . The high output of timer is  $[V_{CC} - 2V_{BE}]$ . Take  $C$  (timing capacitor) =  $.22\mu F$ . Draw the circuit with all component values.

- 7) Refer to the circuit shown below.

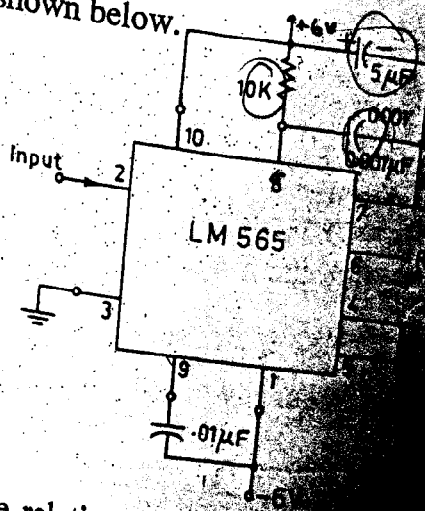

Calculate & show the relationship between  $f$  and  $R$  indicating all boundary values.

**BITS, PILANI - DUBAI CAMPUS**  
**KNOWLEDGE VILLAGE, DUBAI**  
III-Year II- Semester 2003- 2004


COURSE NO: EEE UC364/ INSTR UC364  
TIME: 50 minutes

COURSE TITLE: ANALOG ELECTRONICS  
MARKS: 25


*Text-I*

NOTE: (Answer all Questions, Data provided are complete)

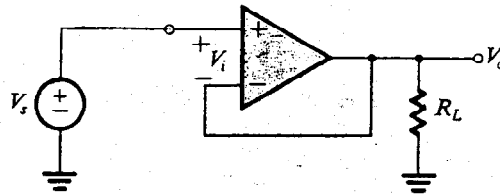
- 1) A non - inverting op-amp configuration is shown in figure. Assume that the op-amp has infinite input resistance and zero output resistance. If  $A=100$ , what is the closed loop voltage gain? What is the amount of feedback in dB? If  $A$  decreases by 10%, what is the corresponding decrease in  $A_f$ ? (Express it in percentage.) [5 marks]



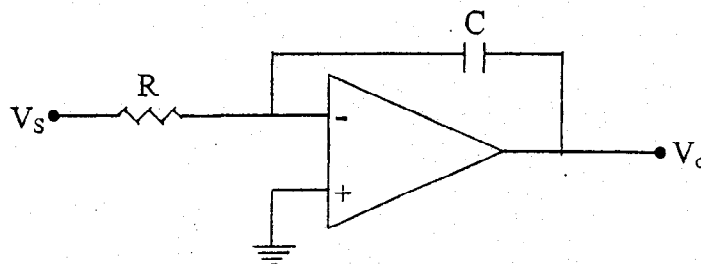- 2) Design an inverting op-amp circuit to form the weighted sum  $V_o$  of two inputs  $V_1$  and  $V_2$ . It is required that  $V_o = -(V_1 + 5V_2)$ . Choose values for  $R_1$ ,  $R_2$  and  $R_f$  so that for a maximum output voltage of 10V the current in the feedback resistor will not exceed 1mA. [4 marks]
- 3) Design an integrator (shown in figure) with a resistance of  $100K\Omega$  and a time constant of 1 second. For a dc input of  $-1V$  applied at the input at time 0,  $V_o = -10v$
- (a) How long does it take the output to reach 0 volt?  
(b) How long does it take the output to reach 10 volt? [5 marks]



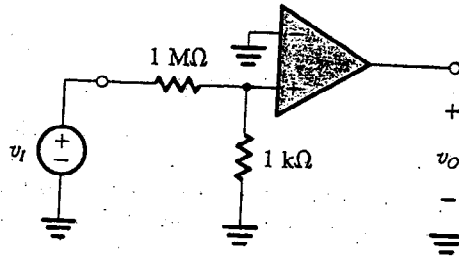- 4) The circuit shown uses an op-amp, that is ideal, except for having a finite gain  $A$ . Measurements indicate  $V_o = 3.5V$ . When  $V_i = 3.5V$ , what is the op-amp gain  $A$ ? [3 marks]



- 5) The following specifications are given for a certain wide band pass filter.  $f_l=400\text{Hz}$ ,  $f_h=1\text{KHz}$ , and pass band gain=1. Calculate the value of  $Q$  for the filter. Mention one application of All pass filter. [4 marks]
- 6) Design a non - inverting amplifier (shown in figure) with a gain of 2. At the maximum output voltage of 10V, the current in the voltage divider is to be  $10\mu\text{A}$ . [4 marks]

